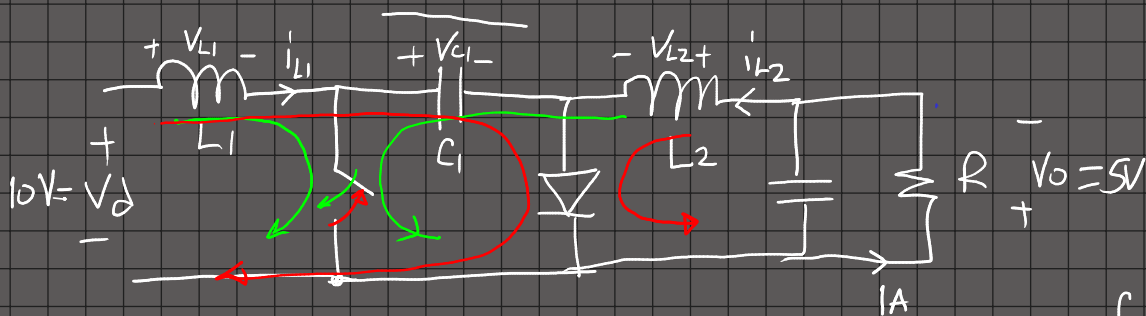


■ **Example 7-3** In a Cúk converter operating at 50 kHz, $L_1 = L_2 = 1$ mH and $C_1 = 5$ μ F. The output capacitor is sufficiently large to yield an essentially constant output voltage. Here $V_d = 10$ V and the output V_o is regulated to be constant at 5 V. It is supplying 5 W to a load. Assume ideal components.

Calculate the percentage errors in assuming a constant voltage across C_1 or in assuming constant currents i_{L1} and i_{L2} .



$$f_s = 50 \text{ kHz}$$

$$T_s = \frac{1}{f_s} = 20 \mu\text{se.}$$

$$V_o = V_d \cdot \frac{D}{(1-D)} \Rightarrow \frac{V_o}{V_d} = \frac{5}{10} = \frac{D}{1-D} \Rightarrow D = \frac{1}{3} = 0.33 \dots$$

Assume C.C.M

$$\Delta i_{L1} = \frac{V_d \cdot D \cdot T_s}{L_1} = \frac{(V_{C1} - V_d) (1-D) T_s}{L_1}$$

$$= \frac{10 \cdot \frac{1}{3} \cdot 20 \mu\text{s}}{1 \text{ mH}} = 0.067 \text{ A} = 67 \text{ mA}$$

$V_{C1} = V_o + V_d = 15 \text{ V (average)}$

$$\Delta i_{L2} = \frac{V_o (1-D) \cdot T_s}{L_2} = \frac{5 \left(\frac{2}{3}\right) \cdot 20 \mu\text{s}}{1 \text{ m}} = 0.067 = 67 \text{ mA}$$

$\Delta i_{L1} = \Delta i_{L2}$
because $L_1 = L_2$

$i_{L1}(\text{average}) = 0.5 \text{ A}$
 $i_{L2}(\text{average}) = 1 \text{ A}$

$\Delta i_{L1} \ll i_{L1(\text{av})}$
 $\Delta i_{L2} \ll i_{L2(\text{av})}$ } CCM is verified!

inductor currents

$$\frac{\Delta i_{L1}}{i_{L1(\text{av})}} = \frac{0.067}{0.5} \Rightarrow 13.4\% \text{ ripple}$$


$$\frac{\Delta i_{L2}}{i_{L2(\text{av})}} = \frac{0.067}{1} = 6.7\% \text{ ripple}$$

Capacitor $i_{L1} \Rightarrow$ Assume constant 0.5A

$$\Delta V_{C1} = \frac{0.5 (1 - \frac{1}{3}) \cdot 20 \mu\text{s}}{5 \mu\text{F}} = 1.33 \text{ V}$$

$$V_{C1(\text{av})} = 15 \text{ V}$$

$$V_{C1(t)} = 15 \pm \frac{1.33}{2}$$

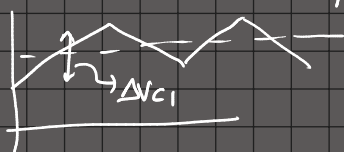

$$\frac{\Delta V_{C1}}{V_{C1(\text{av})}} = \frac{1.33}{15} \Rightarrow 8.9\% \text{ ripple}$$