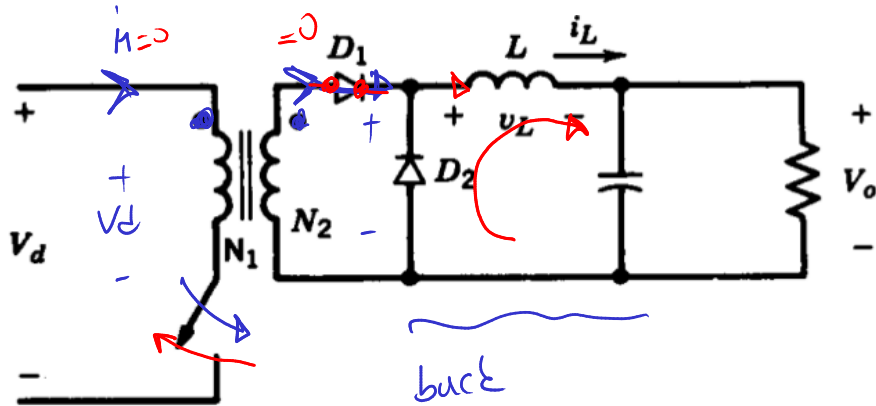


Forward Converter


Derived from the Buck Converter



Forward Converter


Let's obtain the output voltage characteristics

Switch is ON


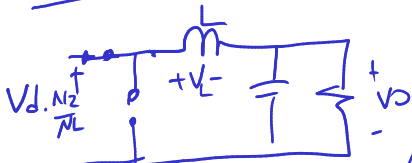


$$V_L = V_d \left(\frac{N_2}{N_1} \right) - V_o$$

Switch is OFF

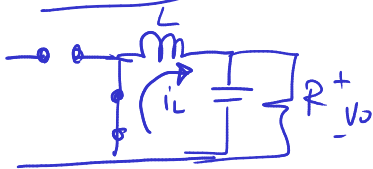

$$V_L = -V_o$$

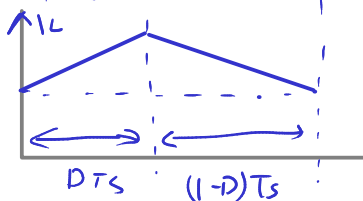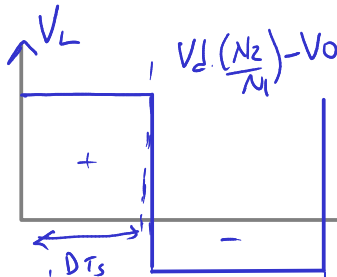

$$V_o = V_d \cdot \frac{N_2}{N_1} \cdot D$$

$$V_d \cdot \frac{N_2}{N_1} \cdot D - V_o D = V_o - V_o D$$

$$\left(V_d \left(\frac{N_2}{N_1} \right) - V_o \right) \cdot D = V_o (1 - D)$$

Forward Converter


A buck converter with added turns ratio

$$\frac{V_o}{V_d} = \frac{N_2}{N_1} D$$

↳ transformer ratio


↳ buck part

Forward Converter

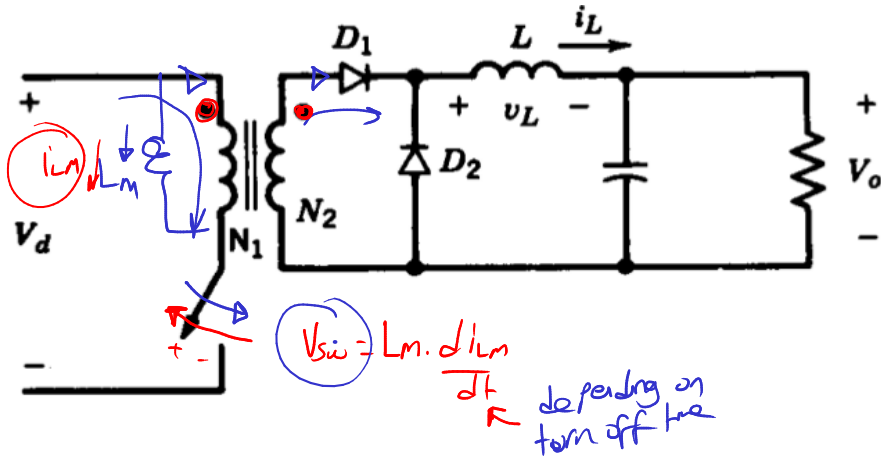

What happens at the instant when the switch is turned-off, if the transformer is not ideal?


Forward Converter

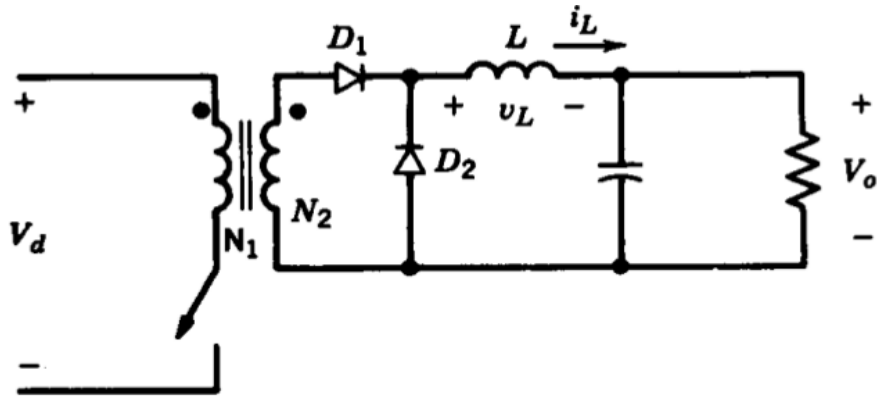

A discharging path for L_m should be added.


Simple Solution: RCD Reset Circuit

↳ Snubber Circuit

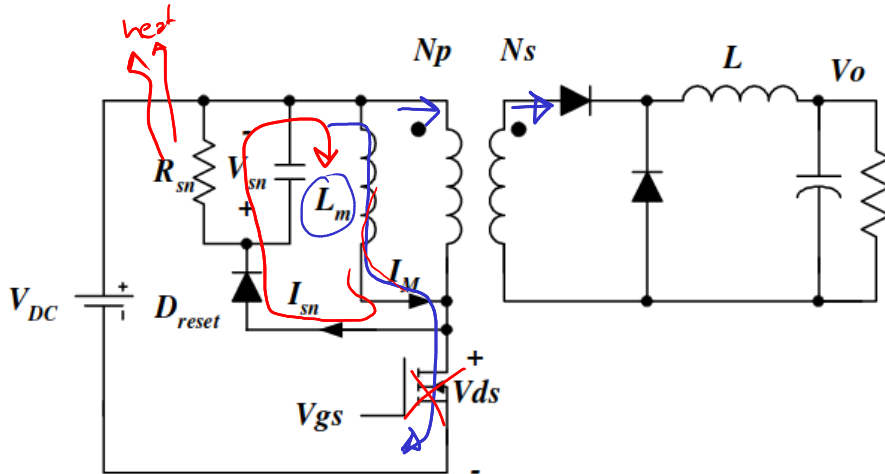

Magnetizing current dissipates through RCD circuit


Simple Solution: RCD Reset Circuit

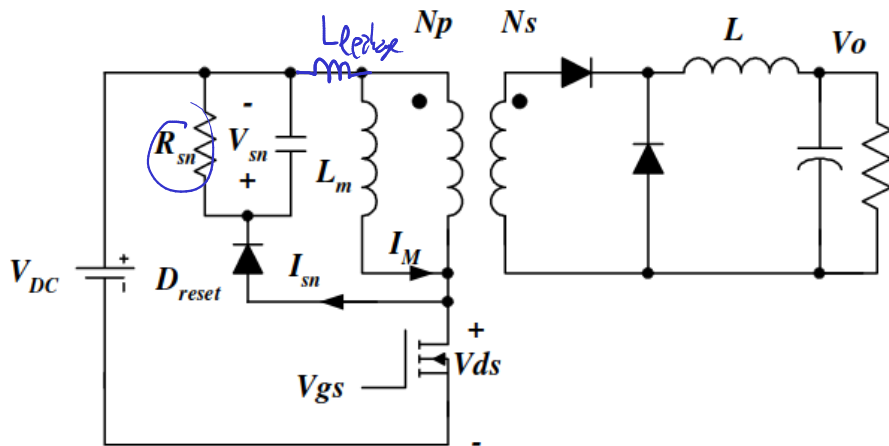

Cheap but inefficient


RCD Snubber

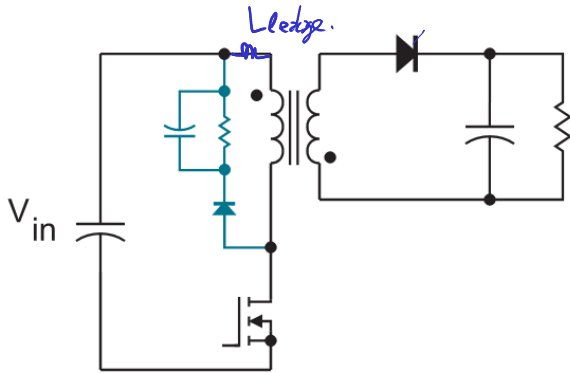Note a similar circuit can be used for the Flyback converter (to reduce inductance leakage ringing)




Suggested Reading: [Flyback Converter Snubber Design](#)

Practical Forward Converter

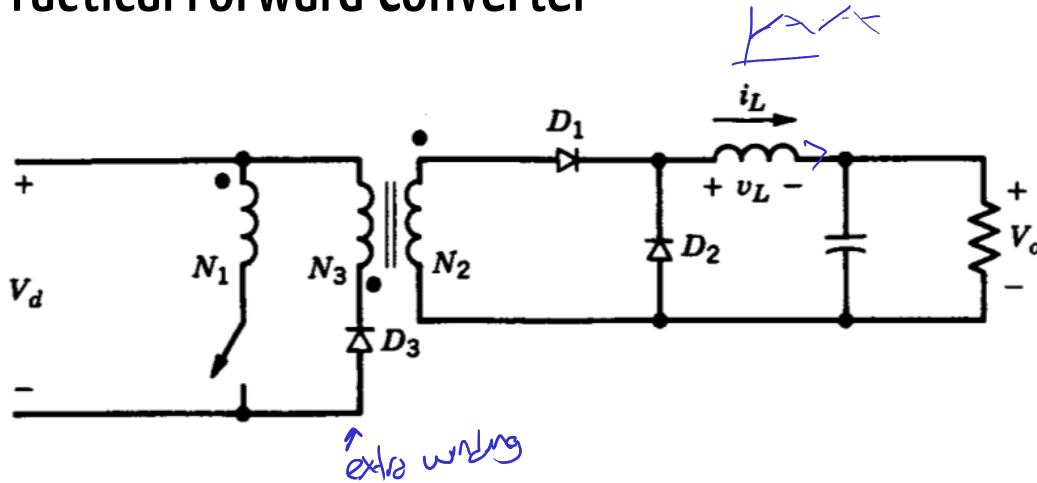


A transformer with two-primary windings

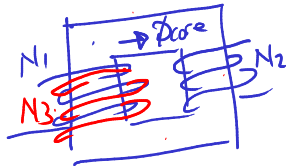Third winding is added to discharge the energy stored in L_m




Practical Forward Converter

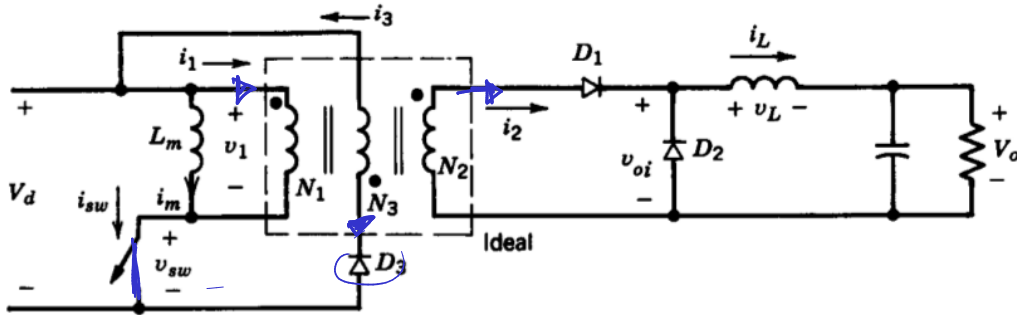



A transformer with two-primary windings

Third winding is added to discharge the energy store

Forward Converter

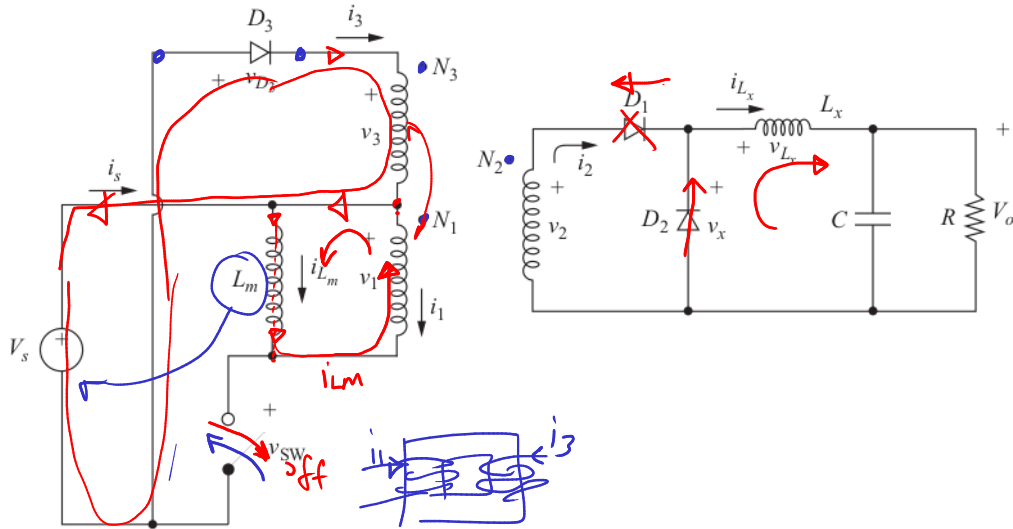

Forward Converter: Switch is ON

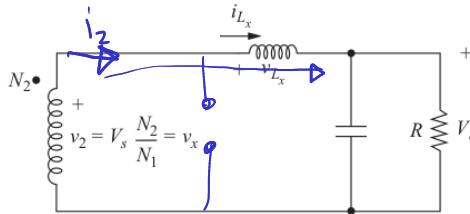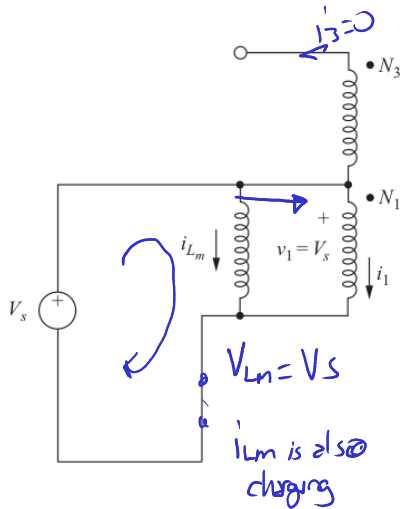


$$V_{Lx} = V_s \frac{N_2}{N_1} - V_o$$

i_{Lx} is increasing linearly

Lm is charged by input voltage, Lx is also charging

D1 On, D2 Off, D3 Off

Forward Converter: Switch is OFF

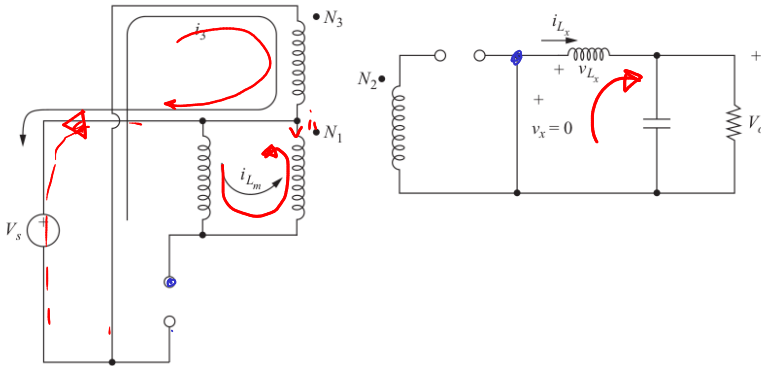

L_x feeds the load, L_m is discharged to the source: $i_1 = -i_{L_m}$

$$\text{KCL: } N_1 i_1 = N_2 i_2 - N_3 i_3$$

For proper operation the transformer should be "reset" before next ON period ✓

Forward Converter: Switch is OFF

$$\text{Switch ON} \Rightarrow V_1 = V_s$$

$$V_2 = V_1 \cdot \frac{N_2}{N_1} = V_s \cdot \frac{N_2}{N_1}$$

$$V_3 = V_1 \cdot \frac{N_3}{N_1} = V_s \cdot \frac{N_3}{N_1}$$

$$V_{D3} = -V_s - V_3 < 0 \Rightarrow D_3 \text{ is off}$$

$$V_{Lm} = V_s \text{ (for DTs)}$$

$$\Delta i_{Lm} = \frac{V_s \cdot DT_s}{L_m}$$

$$i_{sw} = i_1 + i_{Lm}$$

Switch off

$$i_{Lm} = -i_1 \quad V_3 = -V_s$$

$$V_1 = V_3 \cdot \left(\frac{N_1}{N_3}\right) = -V_s \cdot \frac{N_1}{N_3}$$

$$V_2 = V_3 \cdot \left(\frac{N_2}{N_3}\right) = -V_s \cdot \frac{N_2}{N_3}$$

$$V_{Lm} = V_1 = -V_s \cdot \frac{N_1}{N_3} = L_m \cdot \frac{di_{Lm}}{dt}$$

$$\frac{di_{Lm}}{dt} = \frac{-V_s}{L_m} \cdot \left(\frac{N_1}{N_3}\right) \checkmark$$



$$N_1 \cdot i_1 = N_2 \cdot i_2 - N_3 \cdot i_3$$

$i_2 = 0$

$$N_1 i_1 = N_3 i_3$$

$$i_3 = \frac{N_1}{N_3} i_1$$

Forward Converter

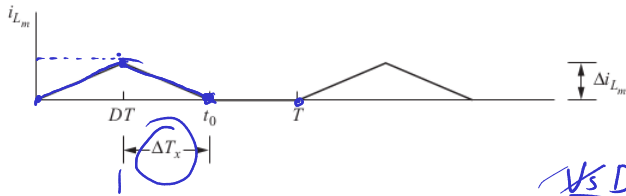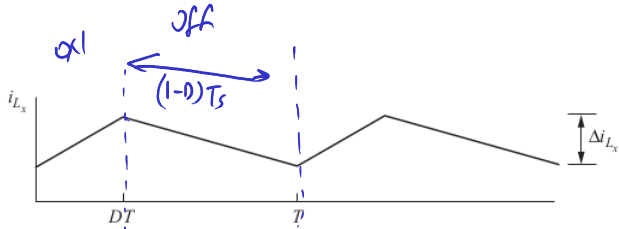

$$i_{L_m(\max)} = \frac{V_s \cdot DT_s}{L_m}$$

$$\Delta T_x < (1-D) T_s$$

$$\Delta T_x = \frac{V_s \cdot DT_s}{L_m \left(\frac{N_1}{N_3} \right)} = DT_s \left(\frac{N_3}{N_1} \right)$$


$$\Delta T_x = DT_s \left(\frac{N_3}{N_1} \right) < (1-D) T_s$$

$$D \left(1 + \frac{N_3}{N_1} \right) < 1$$

$N_1 = N_3$ (common practice)

$$\underline{\underline{D < 0,5}}$$

Forward Converter

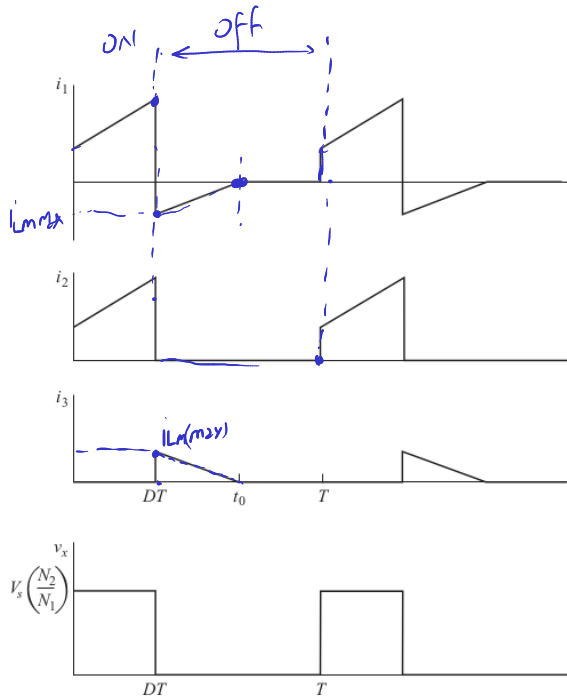

Practical Forward Converter




For proper operation the transformer should be "reset" before next ON period

$$t_m < (1 - D)T_s$$

$$D_{max} = \frac{1}{1 + (N_3/N_1)}$$

if $N_3 = N_1 \Rightarrow D < \underline{\underline{0,5}}$

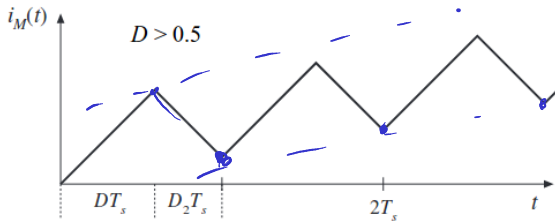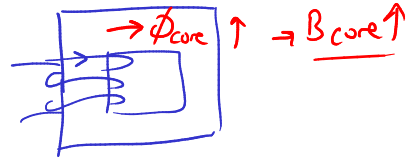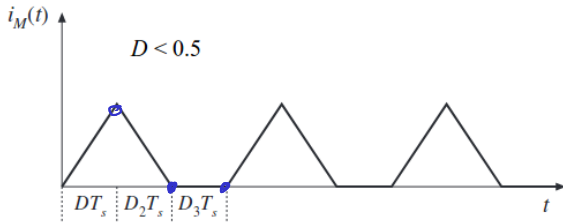What happens if D is large, and transformer does not reset completely?



In the figure $D_{\text{max}}=0.5$

Saturation, increased core losses, reduced L_m , problem in power transfer

Advantages over Flyback


- . Better utilization of transformer (direct power transfer, higher)
- . A gapless core can be used (higher L_m , less ripple)
- . Output inductor and diode ensures continuous output current

Drawbacks compared to Flyback

- Increased cost (extra diode and inductor)
- Gain changes a lot in DCM
- Higher voltage requirement for MOSFET


Forward Converter Alternatives

Two-switch forward converter

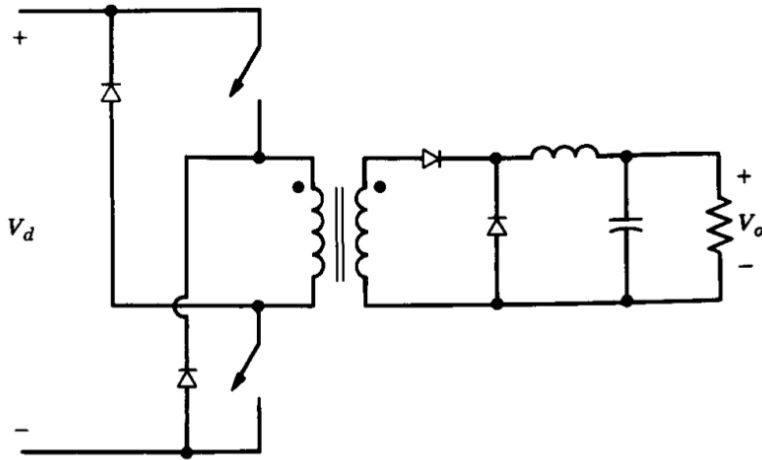


Forward Converter Alternatives

Two-switch forward converter

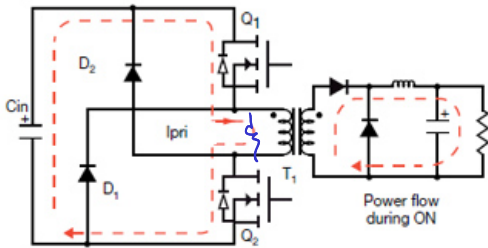

ON state

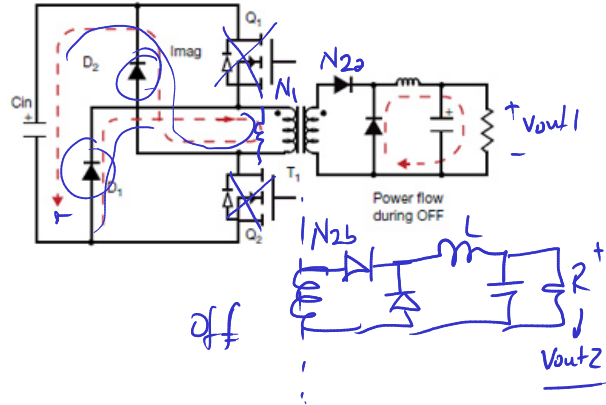

off

Two-switch forward converter

Advantages:

- Does not require a snubber circuit
- Less voltage stress on MOSFETs
- Can supply multiple isolated outputs
- Low power losses and noise

Two-switch forward converter

Disadvantages:

- Slightly more expensive
- Larger component count

Interleaved forward converter

