

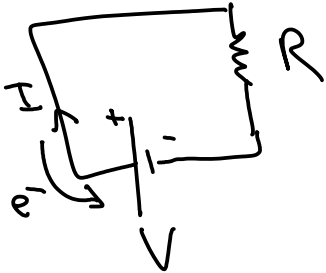



April 2, 2015

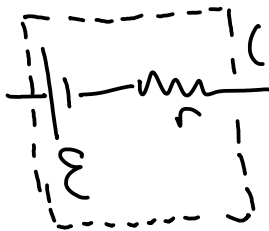

$$V = IR$$

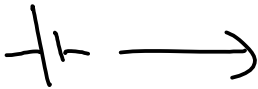$\mathcal{E}$ ; emf = electro  
motive  
force  
(it is not a force)



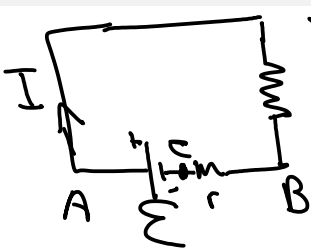

$$V_A - V_B \equiv V_{AB} = IR$$

$$= \mathcal{E} - Ir$$

$$V_A - V_B = (V_A - V_C) + (V_C - V_B)$$

$$= \mathcal{E} + (-Ir)$$

$$V_{AB} = \mathcal{E} - Ir = IR$$

$$I = \frac{\mathcal{E}}{R + r}$$

$$\Delta W = \Delta q (IR)$$


$$\frac{\Delta W}{\Delta t} = \frac{\Delta q}{\Delta t} IR = IR^2$$

$\Delta W$  by an emf source

$$\frac{\Delta W}{\Delta t} = \frac{\Delta q \mathcal{E}}{\Delta t} \Rightarrow \boxed{P = I \mathcal{E}}$$


# Connecting Resistors

## Series Connection

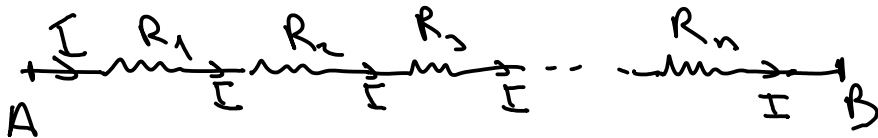

$$\begin{aligned} V_A - V_B &\equiv V = V_1 + V_2 + \dots + V_n \\ &= IR_1 + IR_2 + \dots + IR_n \\ R_{eq} &= R_1 + R_2 + \dots + R_n \end{aligned}$$

# Parallel Connection

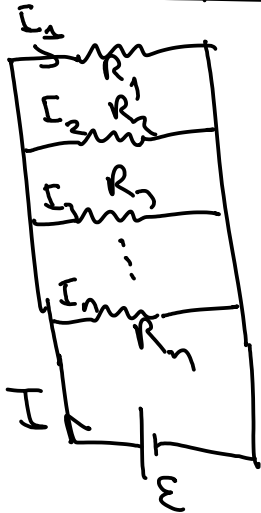

$$I = I_1 + I_2 + I_3 + \dots + I_n$$
$$= \frac{\mathcal{E}}{R_1} + \frac{\mathcal{E}}{R_2} + \dots + \frac{\mathcal{E}}{R_n}$$

$$I = \mathcal{E} \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$


Example 60W, 100W  
at 240 Volts.

$$P = IV = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P}$$

$$R_{60} = \frac{(240V)^2}{60W}$$


$$R_{100} = \frac{(240V)^2}{100W}$$

$$R_{60} > R_{100}$$

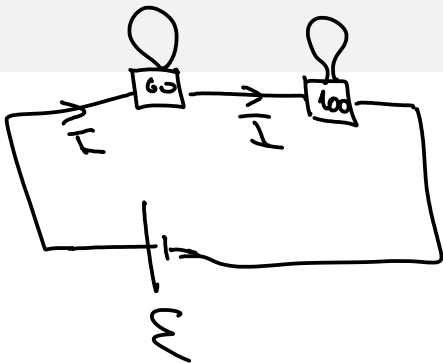

$$P = VI = \frac{V^2}{R} = I^2 R$$

$$P_{60} > P_{60}$$

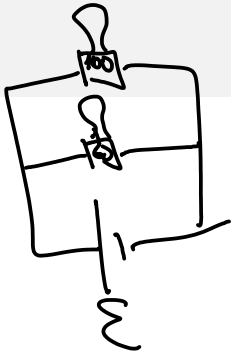

$$P = I^2 R$$


$$P_{60} = I^2 R_{60}$$

$$P_{100} = I^2 R_{100}$$

$$P_{100} > P_{60}$$




# QUIZ 3

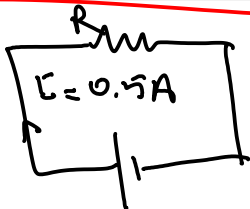


$R$  is how many ohms?

# Example

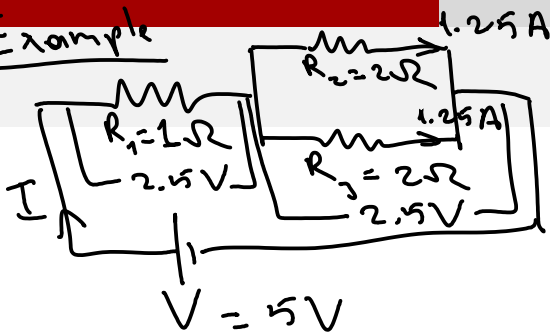


$$I = ?$$



$$I = \frac{5V}{2\Omega} = 2.5A$$

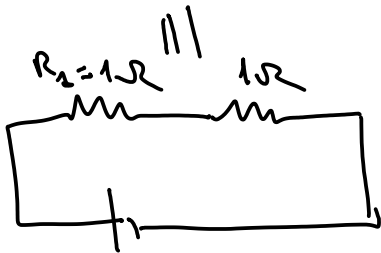


$\equiv$

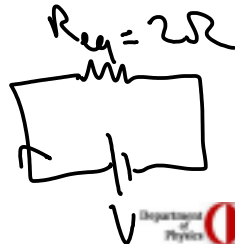

# Example - Kirchoff's Laws

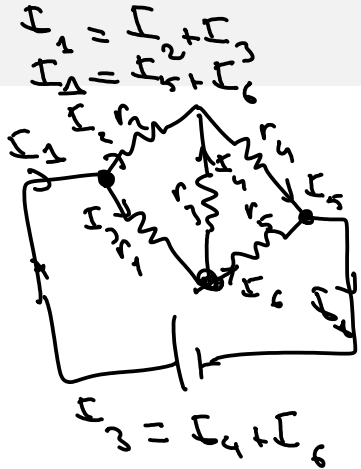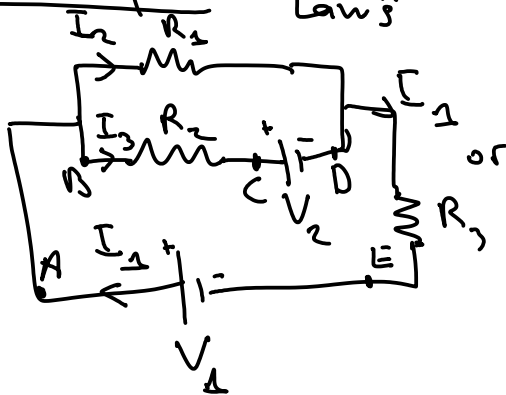

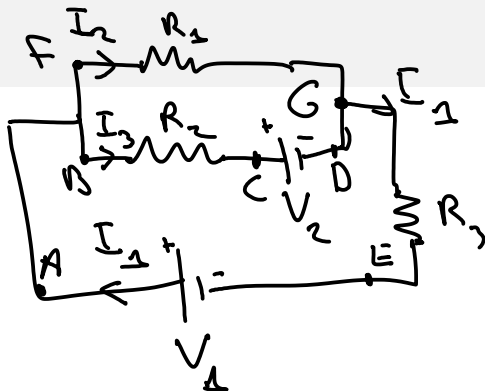
$$\begin{aligned}
 V_{AA} = 0 &= -V_{AB} + V_{BC} + V_{CD} + V_{DE} + V_{EA} \\
 &= 0 + I_3 R_2 + V_2 + I_1 R_3 - V_A \quad (1)
 \end{aligned}$$



$$I_1 = I_2 + I_3 \quad (3)$$


$$\begin{aligned}
 V_{AA} = 0 &= V_{AF} + I_2 R_1 + V_{GE} + V_{EA} \\
 &= 0 + I_2 R_1 + I_1 R_3 - V_1 \quad (2)
 \end{aligned}$$

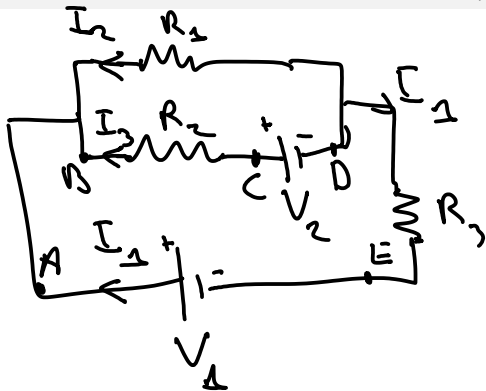Alternative choice of directions of currents.


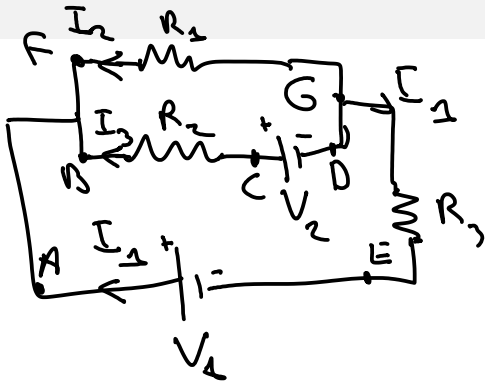
$$\begin{aligned}
 V_{NA} &= V_{AB} + V_{BC} + V_{CD} + V_{DE} + V_{EA} \\
 &= 0 - I_3 R_2 + V_2 + I_1 R_3 - V_A \quad (1')
 \end{aligned}$$






$$I_1 + I_2 + I_3 = 0 \quad (1)$$

$$\begin{aligned} V_{AA} = 0 &= V_{AF} + V_{FG} + V_{GE} + V_{EA} \\ &= 0 - I_2 R_2 + I_1 R_2 - V_A \quad (2) \end{aligned}$$

# Certain Limits

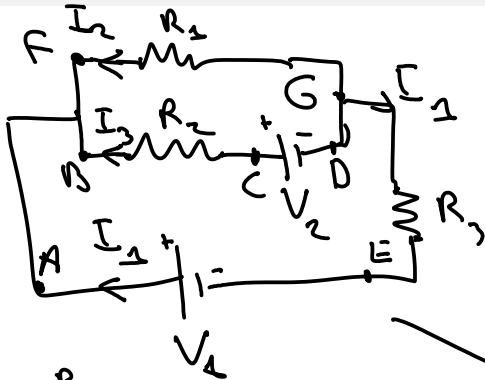

$$R_1 \rightarrow \infty \Rightarrow I_2 = 0$$

$$\text{if } V_2 > V_1 \\ I_3 > 0, I_1 < 0$$


$$\text{if } V_2 < V_1 \\ I_3 < 0, I_1 > 0$$

$$\text{if } R_2 \rightarrow \infty \Rightarrow I_3 = 0$$

$$I_1 = -I_2 > 0$$

$$I_1 = \frac{V_1}{R_1 + R_3}$$

# Capacitors In a Circuit

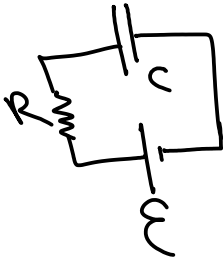


$Q_{\text{max}} = C \mathcal{E}$   
reached  $t \rightarrow \infty$   
at this time  $I = 0$

at  $t = 0$ ,  $Q = 0$

$$I = \frac{\mathcal{E}}{R}$$



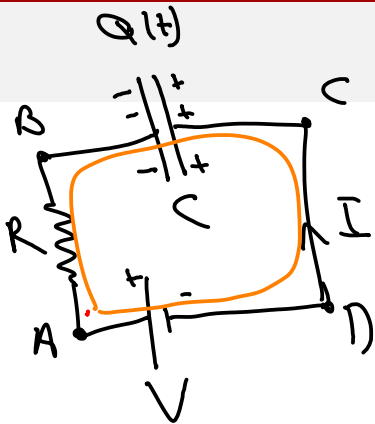

$$Q = CV$$

$$\begin{aligned} V_{AA} &= V_{AB} + V_{BC} + V_{CD} + V_{DA} \\ &= -IR - \frac{Q}{C} - 0 - V \end{aligned}$$

$I$  runs for a duration  $dt$

$$dQ = I dt \quad \Rightarrow \quad I = \frac{dQ}{dt}$$

$$-\frac{dQ}{dt} R - \frac{Q}{C} - V = 0$$

$$-\frac{dQ}{dt}R - \frac{Q}{C} - V = 0$$

$$\frac{dQ}{dt} + \frac{Q}{RC} = -\frac{V}{R}$$


$$Q(t) = A e^{-t/RC} - VC$$

$$Q(t=0) = A - VC = 0 \quad (\text{initial cond.})$$

$$Q(t) = -VC (1 - e^{-t/RC})$$

$$Q(t) = -VC(1 - e^{-t/RC})$$

$$\ln e = 1$$
$$e \approx 2.718...$$

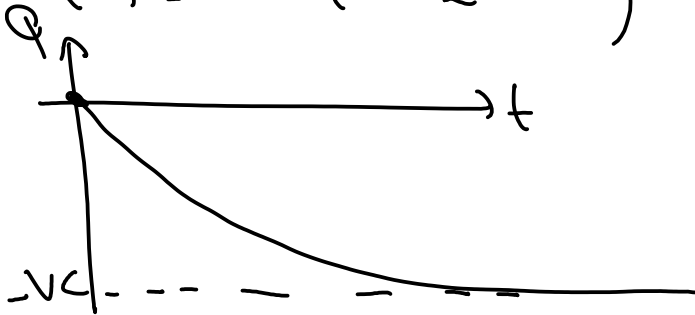


$t \rightarrow \infty \Rightarrow t \gg RC$


$$I = \frac{dQ}{dt} = \frac{d}{dt} (VC) (1 - e^{-t/RC})$$

$$= (-V \Delta) \left( \frac{1}{RC} \right) e^{-t/RC}$$

$$I(t) = \frac{V}{R} e^{-t/RC}$$

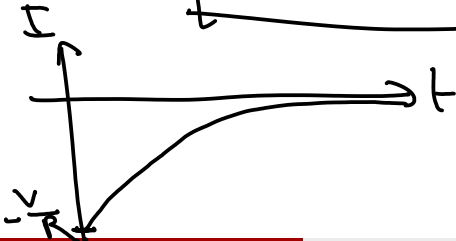

# Example

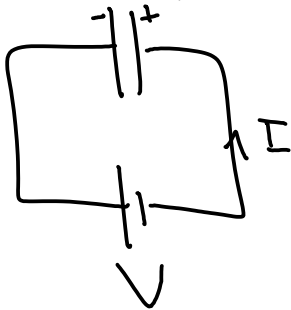

$$Q(t=0) = VC$$