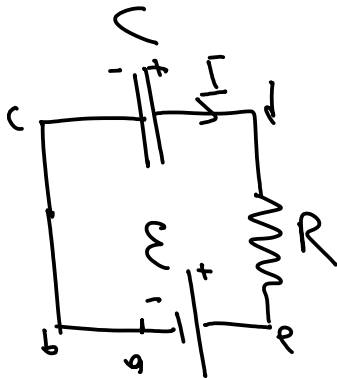


April 7, 2015

$$\oint \vec{E} \cdot d\vec{r} = 0 \Rightarrow \Delta V = - \int_{r_1}^{r_2} \vec{E} \cdot d\vec{r}$$



$$\oint \vec{E} \cdot d\vec{r} = 0$$

a → b → c → d → e

→ a

∴ sum of all pot drops.

$$0 + 0 - \mathcal{E} + IR + \mathcal{E} = 0$$

$$I = \frac{\mathcal{E}}{R + r}$$

$$- \frac{Q}{C} - \frac{dQ}{dt} R + \mathcal{E} = 0$$

$$\frac{dQ}{dt} + \frac{Q}{RC} = \frac{\mathcal{E}}{R}$$

$$\frac{dQ}{dt} = - \frac{Q}{RC} + \frac{\mathcal{E}}{R}$$

$$Q = A e^{\alpha t} + B$$

$$\frac{dQ}{dt} = \alpha A e^{\alpha t} = \alpha (Q - B) = \alpha Q - \alpha B$$

$$\frac{d}{dx} \ln x = \frac{1}{x}$$

$$\frac{d}{dx} x^n = nx^{n-1}$$

$$\frac{d}{dx} \sin x = \cos x$$

$$\frac{d}{dx} \cos x = -\sin x$$

$$\frac{d}{dx} e^x = e^x$$
$$\left[(\sin x)^{\cos x} \right] e^x$$

$$e^{ix} \equiv \cos x + i \sin x$$

Euler Formula

$$Q = A e^{\alpha t} + B$$


$$\frac{dQ}{dt} = \alpha A e^{\alpha t} = \alpha (Q - B) = \alpha Q - \alpha B$$

$$\frac{dQ}{dt} = -\frac{Q}{RC} + \frac{\mathcal{E}}{R}$$

$$\Rightarrow \alpha = -\frac{1}{RC} \quad -\alpha B = \frac{\mathcal{E}}{R} \Rightarrow B = \frac{-\mathcal{E}}{\alpha R} = \mathcal{E}C$$

$$Q(t) = A e^{-t/RC} + \mathcal{E}C$$

Example

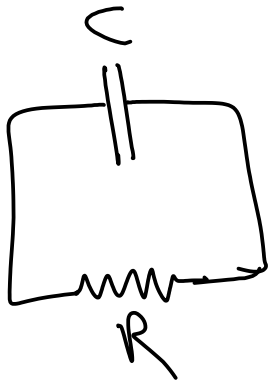


$$\mathcal{E} = 0$$

$$Q(t) = A e^{-t/RC}$$

$$Q(t=0) = Q_0 = A$$

$$Q(t) = Q_0 e^{-t/RC}$$

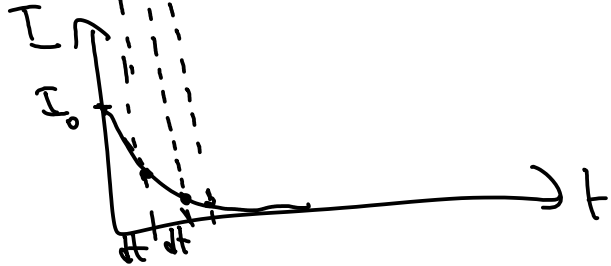

$$Q(t) = \Sigma C (1 - e^{-t/RC})$$



if $Q(t=0) = 0$

$$t = 5\tau = 5RC$$

$$e^{-5} \approx \frac{1}{2.7^5} \approx \frac{1}{3^5} \approx \frac{1}{250} \approx 0.004$$

$$Q(5\tau) = Q_{\max} 0.996$$

Example

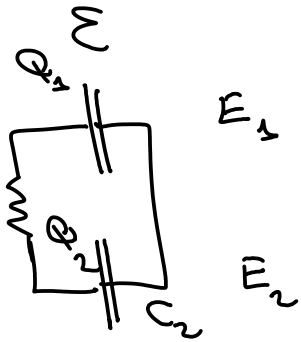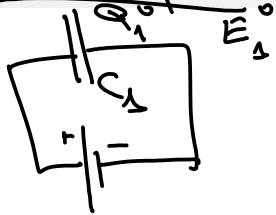


$$\Pi_1^0 \neq \Pi_1 + \Pi_2$$


$$\Pi_1^0 = \frac{1}{2} C_1 \mathcal{E}_1^2$$

$$\Pi_2 = \frac{1}{2} C_2 \mathcal{E}_2^2$$
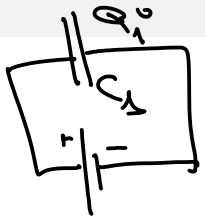
$$\Pi_1^0 = \frac{1}{2} C_1 \mathcal{E}_1^2$$




$$\mathcal{E}_1 = \frac{Q_1}{C_1}$$

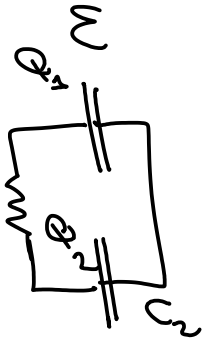

$$\mathcal{E}_2 = \frac{Q_2}{C_2} + IR$$


$$\mathcal{E}_2 = \frac{Q_2}{C_2}$$

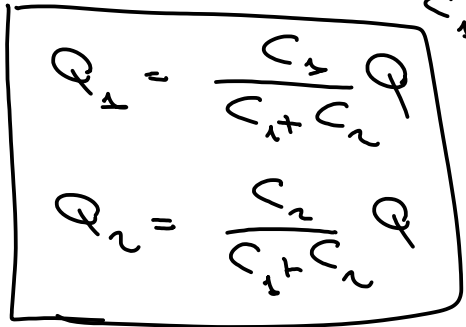

$$Q_1 = C_1 V_1$$

$$Q_2 = C_2 V_2$$

$$Q_1 + Q_2 = (C_1 + C_2) V$$

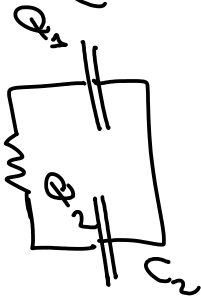


$$U_1$$

$$U_2 = \frac{C_2}{2(C_1 + C_2)} \mathcal{E}$$

$$U_2$$
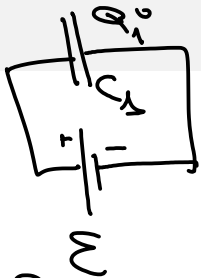
$$U_1 + U_2 = \frac{1}{2} \mathcal{E} \neq \frac{1}{2} \mathcal{E}$$




$$U_1 = \mathcal{E}$$

$$U_2 = \frac{C_1}{2(C_1 + C_2)} \mathcal{E}$$

$$U_2 = \frac{C_2}{2(C_1 + C_2)} \mathcal{E}$$

$$U_1 + U_2 = \frac{1}{2} \mathcal{E} \neq \frac{1}{2} \mathcal{E}$$
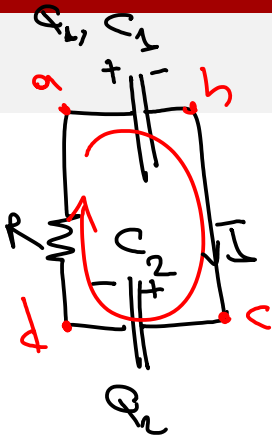
$$U_1 + U_2 = \frac{C_1}{2(C_1 + C_2)} \mathcal{E} + \frac{C_2}{2(C_1 + C_2)} \mathcal{E} = \frac{C_1 + C_2}{2(C_1 + C_2)} \mathcal{E} = \frac{1}{2} \mathcal{E}$$



$$q_1 = q_2$$

$$\frac{q_1}{C} + 0 + \frac{q_2}{C} + IR = 0$$

$$\frac{q_1}{R} + \frac{q_2}{R} = 0$$

$$IR - q_1 = -q_2$$

$$\frac{q_1}{R} + \frac{q_1}{R} = -\frac{q_1}{R}$$

$$Q_2 = Q_1 - Q$$

$$Q_1 + Q_2 + \Gamma R = 0$$

$$Q_1 + Q_2 + \Gamma R = 0$$

$$\frac{Q_1}{R C_{eq}} + \frac{Q_2}{R C_{eq}} + \Gamma R = 0$$

$$Q_1(t) = A e^{-\frac{t}{R C_{eq}}} + Q_2$$

$$Q_1(t) = A e^{-\frac{t}{RC_{eq}}} + Q \frac{C_1}{C_2} e^{-\frac{t}{RC_{eq}}}$$

$$Q_1(t=0) = A + Q \frac{C_1}{C_2} = Q$$

$$\Rightarrow A = Q \left(1 - \frac{C_1}{C_2} \right)$$

$$\Rightarrow Q_1(t) = Q \left[\left(1 - \frac{C_1}{C_2} \right) e^{-\frac{t}{RC_{eq}}} + \frac{C_1}{C_2} e^{-\frac{t}{RC_{eq}}} \right]$$

$$Q_1(t) = Q e^{-\frac{t}{RC_{eq}}} \left(1 - \frac{C_1}{C_2} + \frac{C_1}{C_2} \right)$$

$$Q_1(t) = Q e^{-t/RC} + \frac{C_2 \epsilon_0}{C_2} (1 - e^{-t/RC})$$

$$I = \frac{dQ_1}{dt} = -\frac{Q}{RC} e^{-t/RC}$$

$$I = -\frac{Q}{RC} e^{-t/RC}$$

$$I = -\frac{Q}{RC} e^{-t/RC} \left(\frac{1}{C_1} - \frac{1}{C_2} \right)$$


$$E = - \frac{Q}{R} e^{-\frac{t}{RC_{eq}}} \left(\frac{1}{C_{eq}} - \frac{1}{C_2} \right)$$


$$I = - \frac{Q}{R} e^{-\frac{t}{RC_{eq}}}$$

$$P = I^2 R = \frac{Q^2}{R} e^{-\frac{2t}{RC_{eq}}}$$

$$W = \int_0^{\infty} P dt = \frac{Q^2}{R} \int_0^{\infty} e^{-\frac{2t}{RC_{eq}}} dt = \frac{Q^2}{2C_1(C_1 + C_2)}$$


Ammeter, Voltmeters, Galvanometer, ...

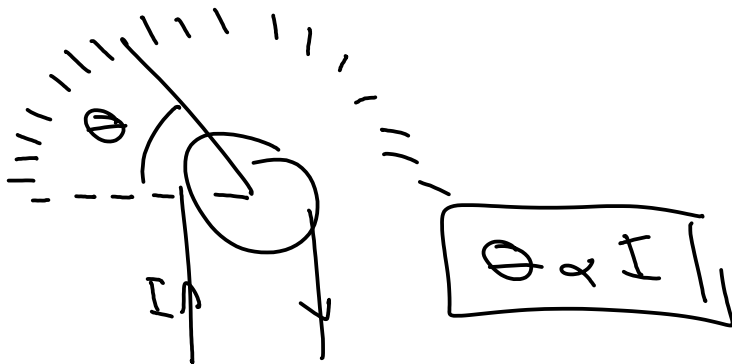

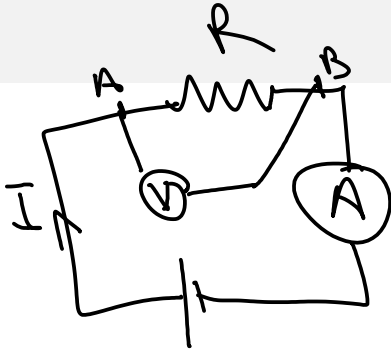

$R_{\text{ammeter}} \ll R$

$R_{\text{voltmeter}} \gg R$

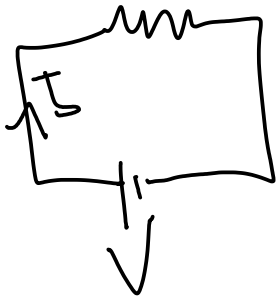

$$V = IR$$

$$I = \frac{V}{R}$$