

EE-362 ELECTROMECHANICAL ENERGY CONVERSION-II

Real & Reactive Power, V-Curves of Synchronous Machines


Ozan Keysan

ozan.keysan.me

Office: C-113 • Tel: 210 7586

Synchronous Machines Power:
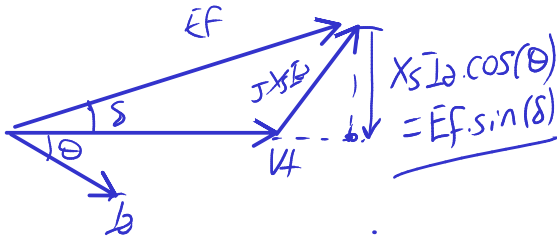
$$P = 3V_t I_a \cos(\theta) \text{ Watt}$$



Synchronous Machines Power:

$$P = 3V_t I_a \cos(\theta) \text{ Watt}$$


or

$$P = \frac{3V_t E_f \sin(\delta)}{X_s}$$

R_a is neglected

What about Q (Reactive power)?
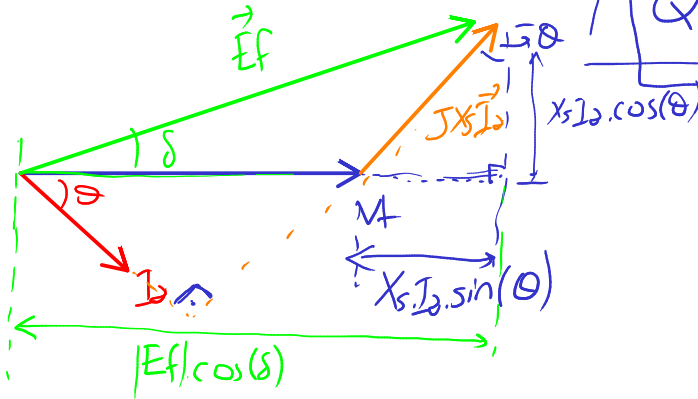
$$Q = 3V_t I_a \sin(\theta) \text{ VAR}$$



$$|E_f| \cos(\delta) - |V_t| = X_s I_a \sin(\theta)$$

$$I_a \sin(\theta) = \frac{|E_f| \cos(\delta) - |V_t|}{X_s}$$

$$Q = 3V_t \left(\frac{|E_f| \cos(\delta) - |V_t|}{X_s} \right)$$

What about Q (Reactive power)?


$$Q = 3V_t I_a \sin(\theta) \text{ VAR}$$

$$Q = \frac{3V_t (E_f \cos(\delta) - V_t)}{X_s}$$

If $|E_f \cos(\delta)| > |V_t| \Rightarrow Q > 0$


If $|E_f \cos(\delta)| < |V_t| \Rightarrow Q < 0$

leading pf

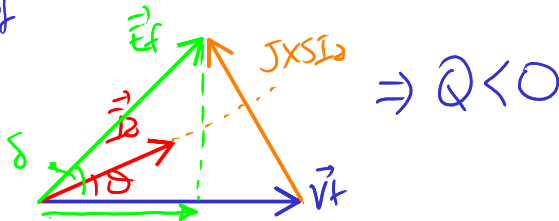


What about Q (Reactive power)?

Formal derivation

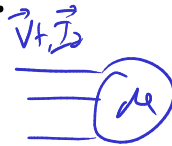

$$S = 3 \cdot V_t \cdot \vec{I}_0^*$$

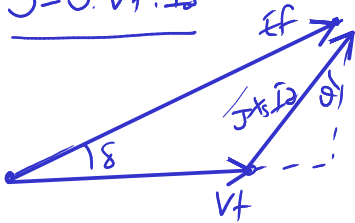

$$\vec{I}_0 = \frac{\vec{E}_f - \vec{V}_t}{jX_s}$$

$$\vec{I}_0 = \frac{E_f(\cos(\delta) + j\sin(\delta)) - V_t}{jX_s}$$

$$S = 3 V_t \cdot \left(\frac{E_f(\cos(\delta) + j\sin(\delta)) - V_t}{jX_s} \right)^*$$

$$= \underbrace{\frac{3 V_t \cdot E_f \cdot \sin(\delta)}{X_s}}_{\text{Real Power (P)}} + j \cdot \underbrace{\frac{3 V_t (E_f \cos(\delta) - V_t)}{X_s}}_{\text{Reactive Power (Q)}}$$

E_f gets larger with I_f (field current)

Real Power (P)

Reactive Power (Q)

Direction of P, Q?

Power (P) flows from leading side to lagging side

Reactive Power (Q) flows from over-excited to under-excited side.

If is large


Direction of P, Q?

Power (P) flows from leading side to lagging side


Reactive Power (Q) flows from over-excited to under-excited side.

Lagging pf generator supplies Q, lagging pf motor absorbs Q

Power-Reactive Power Directions

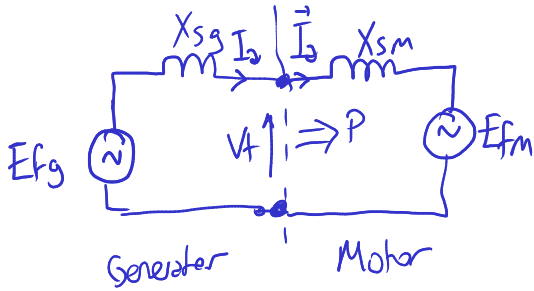


Unity pf
Generator

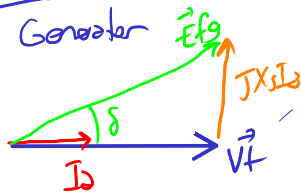

Generates

$\Rightarrow P$
 $Q=0$


Motor

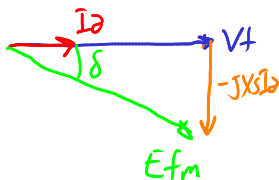

Consumes


$\Rightarrow P$
 $Q=0$

Lagging pf

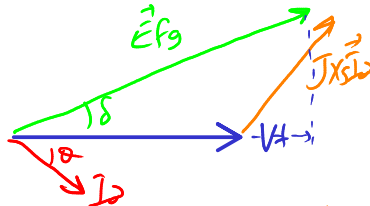

Generating P

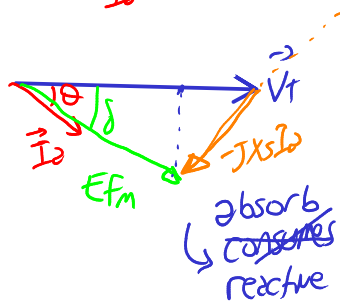$\Rightarrow P$
 $Q > 0$
supplies Q
reactive power




Consumes P
 $\Rightarrow P$

$Q < 0$

absorb
consumes
reactive power


Power-Reactive Power Directions

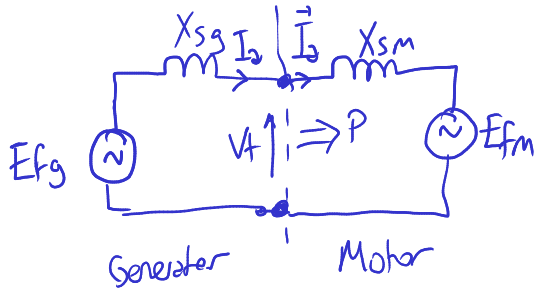


(P) Real power $G \Rightarrow M$
 (Q) Reactive power $G \Leftarrow M$

Leading pf

Generator

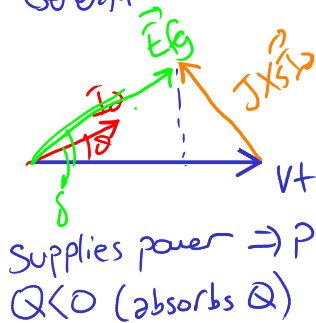

Motor

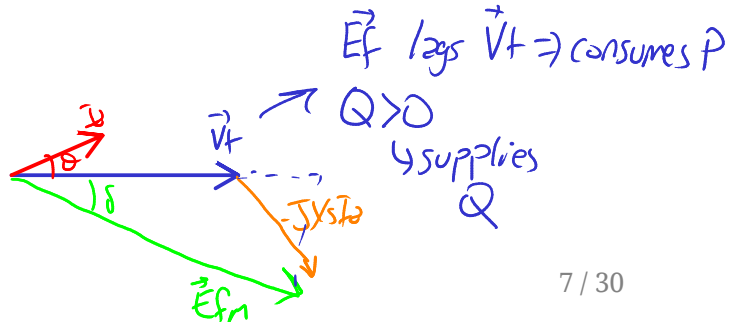

Direction of P, Q Summary

	Supply reactive power Q	$E_A \cos \delta > V_\phi$	Consume reactive power Q	$E_A \cos \delta < V_\phi$
Supply power P				
Generator				
E_A leads V_ϕ	Electro-mechanical system \xrightarrow{P} Electrical system \xrightarrow{Q}		Electro-mechanical system \xleftarrow{P} Electrical system \xleftarrow{Q}	
Consume power P				
Motor				
E_A lags V_ϕ	Electro-mechanical system \xleftarrow{P} Electrical system \xrightarrow{Q}		Electro-mechanical system \xleftarrow{P} Electrical system \xleftarrow{Q}	


Standalone Operation:

Let's draw output voltage vs. load



$I_f \ll I_m$



unity

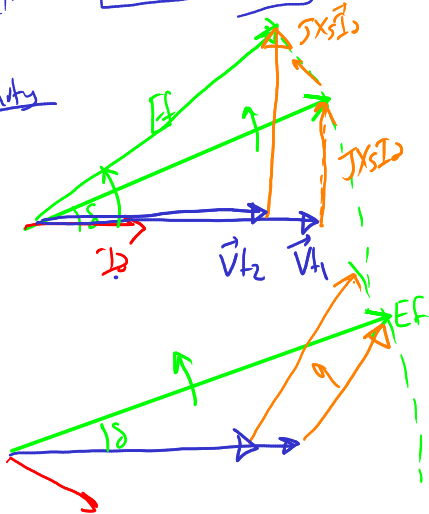

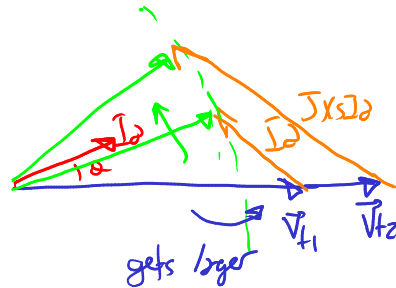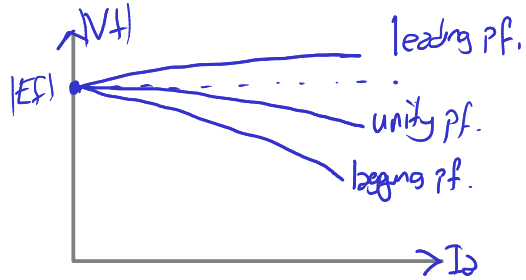$I_f, \text{ constant} \Rightarrow I_a \text{ keeps increasing}$




gets larger


Standalone Operation:

P_{mech} and I_f must be controlled for constant V_t and f .

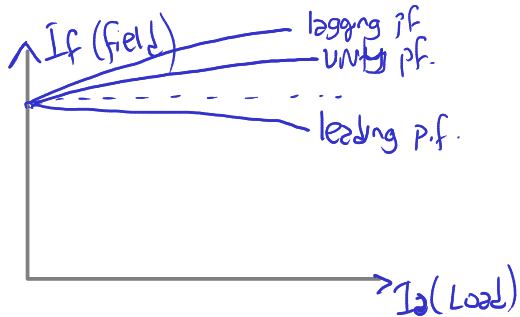Automatically done by the AVR (Automatic Voltage Regulator)



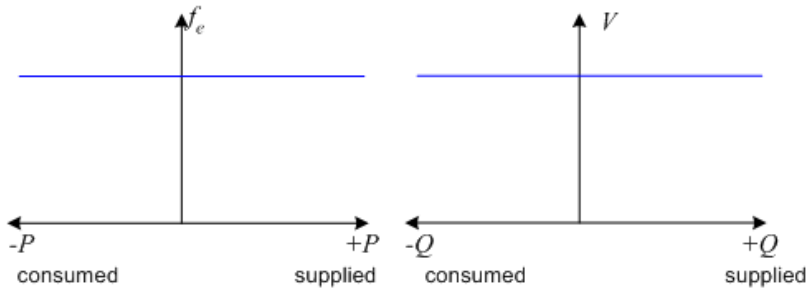
Synchronous Generator Connected to Infinite Bus



Constant terminal voltage and speed

Synchronous Generator Connected to Infinite Bus

$$\vec{E}_f = \vec{V}_t \pm (R_a + jX_s) \vec{I}_a$$


+: Generating

—: Motoring



V_t : Constant (when connected to infinite bus)

Synchronous Generator Connected to Infinite Bus

There exists two main operating modes:

- Constant Excitation, Variable Load (Circle Diagram)
- Constant Power, Variable Excitation

Animation

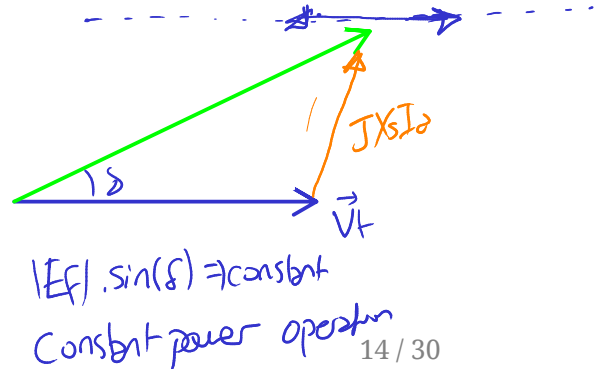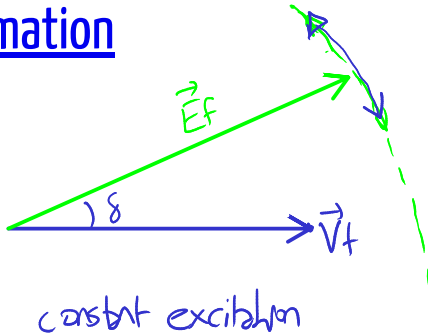


Constant Power, Variable Excitation

From geometry: $E_f \sin(\delta) = X_s I_a \cos(\theta) =$
Constant

E_f moves on horizontal line


For a generator connected to infinite bus:

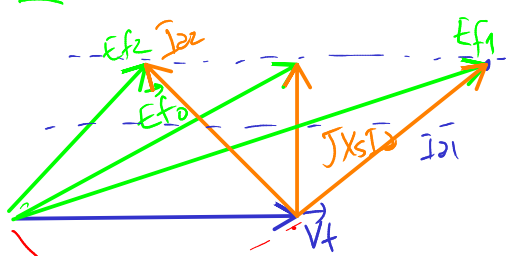Draw I_f vs I_a if the power kept constant (= constant $E_f \sin(\delta)$).




$|E_f| \propto |I_f|$
 $|X_s I_a| \propto |I_a|$

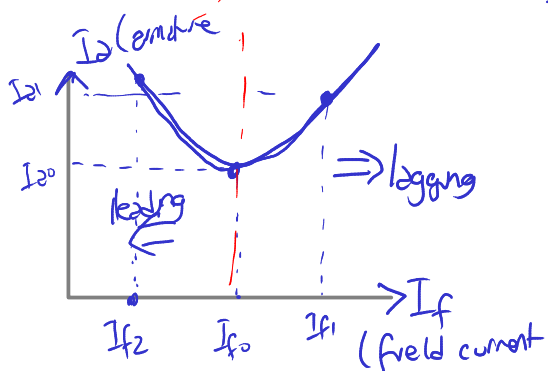field current $\uparrow \Rightarrow$ lagging
 field current $\downarrow \Rightarrow$ leading




For a generator connected to infinite bus:

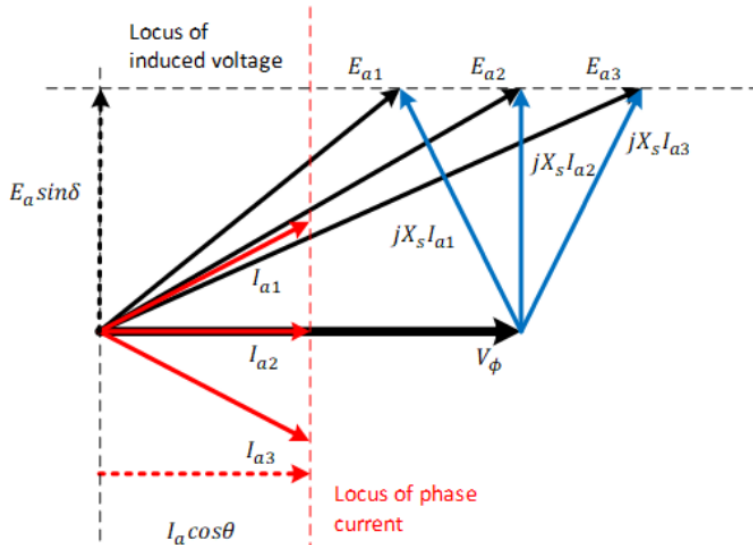Draw I_f vs I_a if the power kept constant (= constant $E_f \sin(\delta)$).




V-Curves: Generating Mode

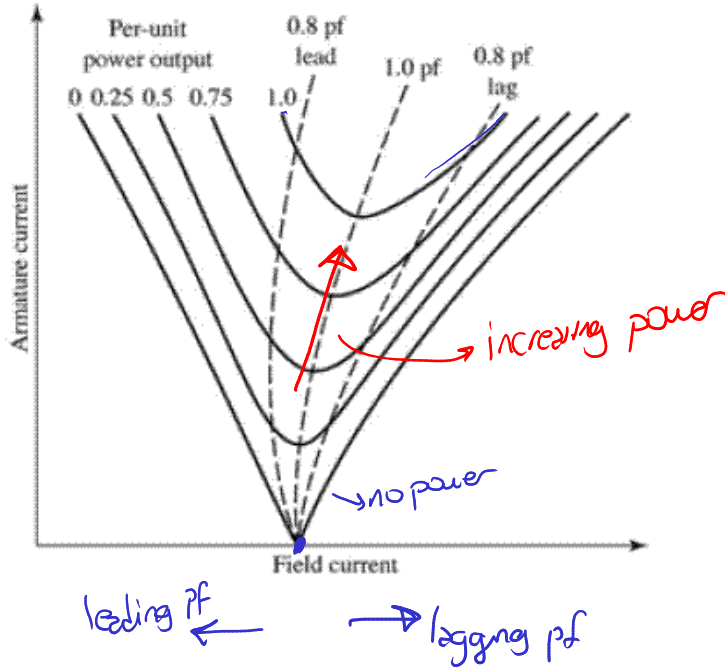


V-Curves: Motoring Mode

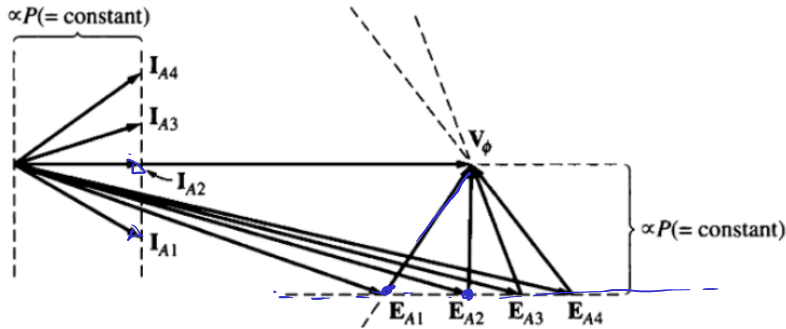Phasor under constant power for the motoring mode



V-Curves: Motoring Mode

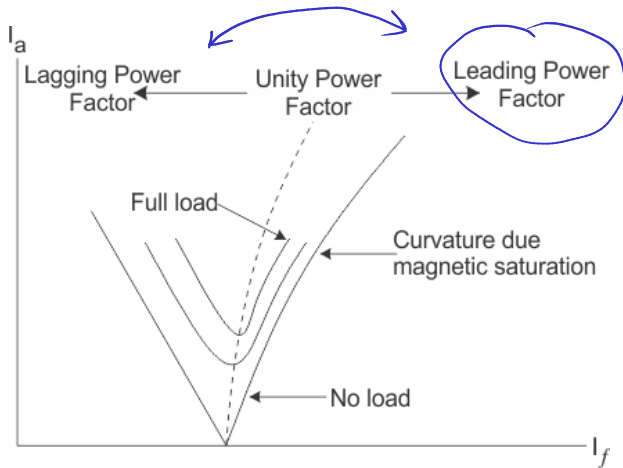Different characteristics for motoring and generating modes



V curves for a synchronous motor with variable excitation

In motoring mode, excess I_{field} makes pf. leading.

Some Useful Animations

[Infinite Bus Operation Animation](#)


[V-curves of a synchronous motor](#)

[Synchronous generator capability curves](#)

[Other Animations](#)

Synchronous Condenser

A Synchronous motor operating at no-load

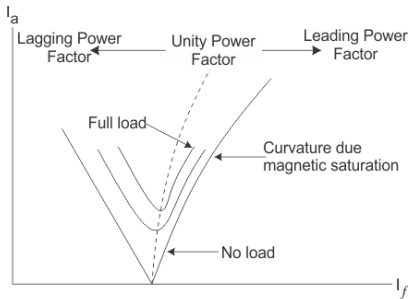

V curves for a synchronous motor with variable excitation

Used to deliver or to absorb VAR by controlling I_f

Can behave as a capacitor or an inductor!

Synchronous Condenser

Any difference compared to a motor?




Largest Synchronous Condenser



100 MVar, 300 tons, built in 2014 by [WEG](#) for the Brasil Grid.
[Manufacturing Video](#)

For curious students: [Rise of renewables leads to synchronous condenser revival, An old tool rediscovered to address new grid challenges](#)

Losses in Synchronous Machines

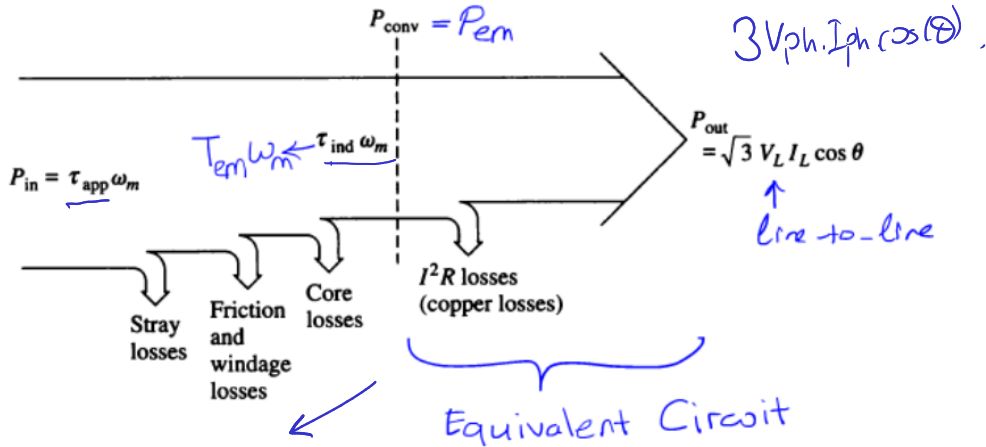


$$\frac{3 I_a^2 R_a}{\substack{\uparrow \\ \text{Armature} \\ \text{current}}} + I_f^2 R_f \substack{\downarrow \\ \text{Stator} \\ \text{losses}}$$

Operating Limits of Synchronous Machines


- Stator Heating: $\propto I_a^2$
- Rotor Heating: Limited $I_f = \text{Limited } E_f$
- Mechanical Power Input Limit ✓
- Stability Limit $\delta < 90$

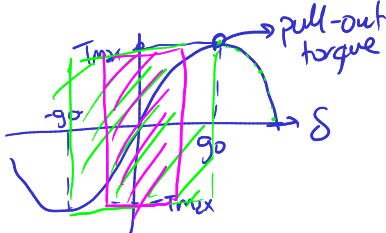Most cases it is much smaller for extra safety



Operating Limits of Synchronous Machines

art IB Electrical Engineering

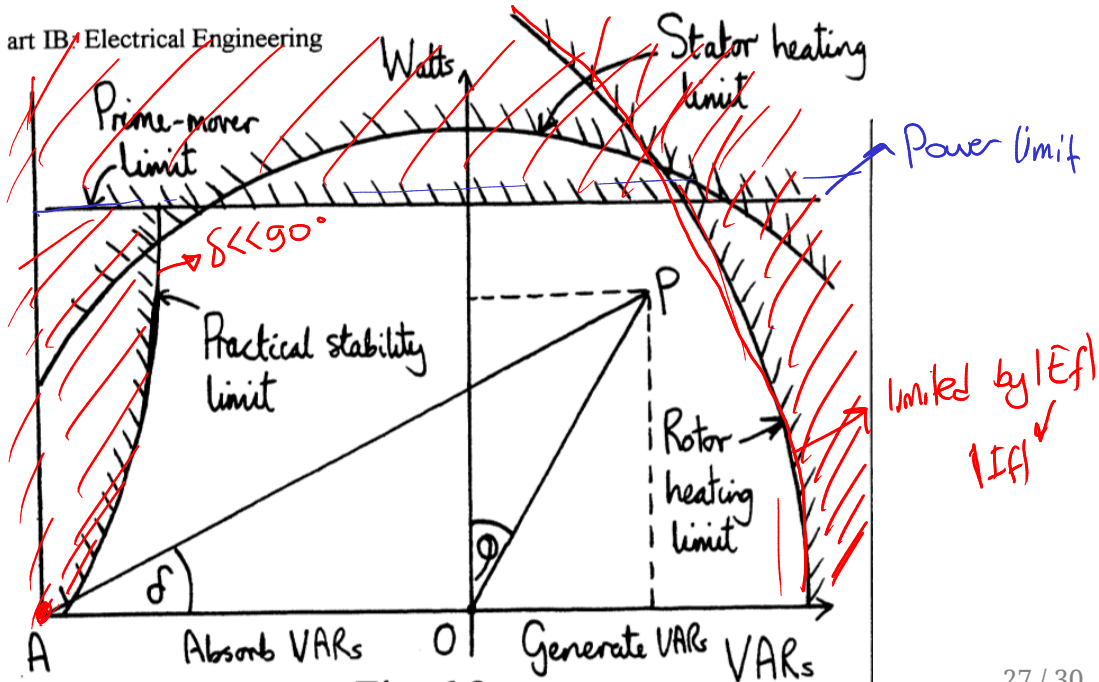

Real Data

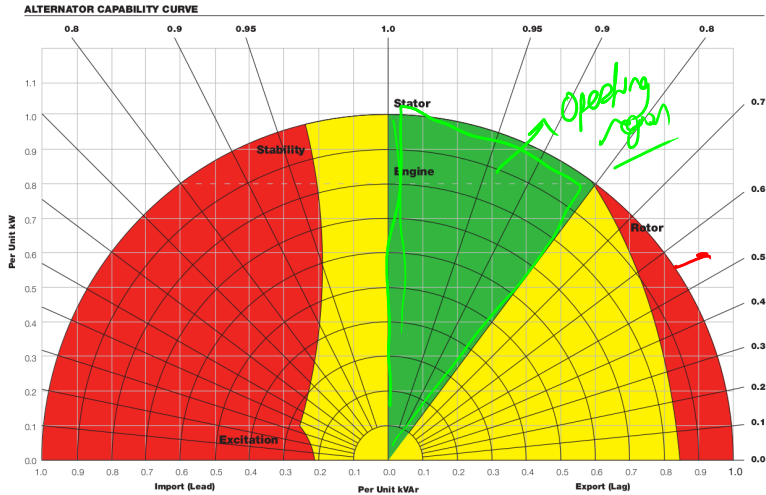


FIGURE 2 – Green area is normal operating range of a typical synchronous machine, yellow is abnormal but not damaging, and operating in red regional will cause damage or misoperation.

Our energy working for you.™
www.cumminspower.com
© 2009 Cummins Power Generation

