

500 MVA, 3-phase, 4-pole, Y-connected synchronous generator connected to 22 kV infinite bus (line-to-line)

Prime mover power (i.e. mechanical power) is set to 300 MW, $X_s = 1,2 \Omega$



- Find E and load angle for a power factor of 0.8 lagging.
- Double check the load angle from the power expression.
- The field current is changed, and the power factor is adjusted to unity at 300 MW. Calculate the new load angle and the E.

$$S_{rated} = 3 V_{ph} I_{ph} = 3 \frac{22 \text{ kV}}{\sqrt{3}} I_{ph} = 500 \text{ MVA} \Rightarrow I_{ph(rated)} = \underline{\underline{13,1 \text{ kA}}}$$

$$\omega_s = \frac{2\pi \cdot 50}{(4/2)} = 50\pi \text{ rad/s} \Rightarrow \underline{\underline{1500 \text{ rpm}}}$$

Mechanical synchronous speed


$$P_{mech} = T \cdot \omega_s$$

$$300 \text{ MW} = T \cdot 50\pi \Rightarrow T = \underline{\underline{1,91 \text{ M.Nm}}}$$

θ) $\text{pf} = 0,8$ lagging

$$P = 3 \cdot V_{ph} \cdot I_{ph} \cdot \cos(\theta) \Rightarrow 300 \text{ MW} = 3 \cdot \left(\frac{22 \text{ kV}}{\sqrt{3}} \right) \cdot I_{ph} \cdot 0,8$$
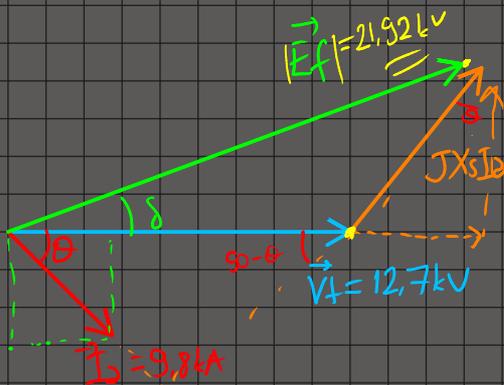
$$I_{ph} = \underline{\underline{9,8 \text{ kA}}}$$



$$|jX_s I_{ph}| = 1,2 \cdot 9,8 \text{ kA} = \underline{\underline{11,8 \text{ kV}}}$$

$$\vec{E}_f = \vec{V}_t + jX_s \vec{I}_{ph}$$


$$|E_f| =$$

$$\vec{E}_f = \left(12,7 \text{ kV} + 11,8 \text{ kV} \cdot \underbrace{\sin(\theta)}_{0,6} \right) + j \cdot 11,8 \text{ kV} \cdot \underbrace{\cos(\theta)}_{0,8}$$

$$|E_f| = \sqrt{(12,7 \text{ kV} + 11,8 \text{ kV} \cdot 0,6)^2 + (11,8 \cdot 0,8)^2} = \underline{\underline{21,92 \text{ kV}}}$$

$$\sin(\delta) = \frac{I_{ph} \cdot X_s \cdot \cos(\theta)}{|E_f|} = 0,43 \Rightarrow \boxed{\delta = 25,5^\circ} \checkmark$$

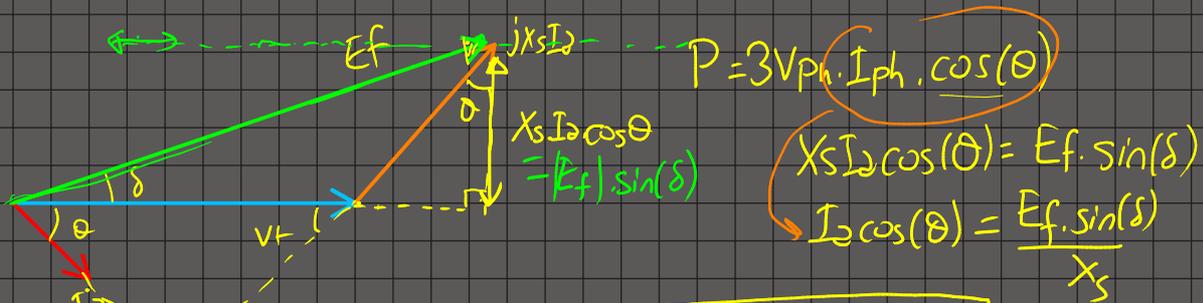
$$b) P = \frac{3 \cdot V_t \cdot E_f \cdot \sin(\delta)}{X_s} \Rightarrow \frac{3 \cdot 12,7 \text{ kV} \cdot 0,43}{1,2} = \underline{\underline{300 \text{ MW}}}$$



$$P = \frac{3 V_t \cdot E_f \cdot \sin(\delta)}{X_s}$$

$$P = T \cdot \omega$$

c) 300 MW \Rightarrow unity pf

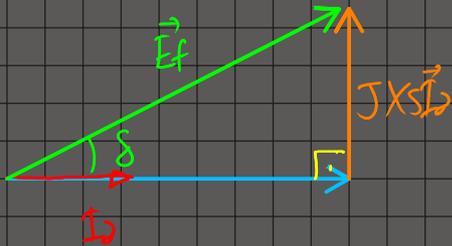

$$P = 3 V_p I_p \cdot \overbrace{\cos(\theta)}^1$$

$$300 \text{ MW} = 3 \cdot \frac{22 \text{ kV}}{\sqrt{3}} \cdot I_2$$

$$I_2 = \underline{\underline{7,84 \text{ kA}}}$$

$$|E_f| = \sqrt{(12,7 \text{ kV})^2 + (7,84 \cdot 1,2)^2}$$

$$\underline{\underline{|E_f| = 15,8 \text{ kV}}}$$

$$\sin(\delta) = \frac{7,84 \cdot 1,2}{15,8} \Rightarrow \underline{\underline{\delta = 36,7^\circ}}$$

double check

$$P = \frac{3 V_{ph} \cdot E_f \cdot \sin(\delta)}{X_s} = \frac{3 \cdot 12,7 \text{ k} \cdot 15,8 \text{ k} \cdot \sin(36,7^\circ)}{1,2} = \underline{\underline{300 \text{ MW}}}$$