

# EE-362 ELECTROMECHANICAL ENERGY CONVERSION-II


## Power and Torque in Induction Machines

Ozan Keysan

[keysan.me](http://keysan.me)


Office: C-113 • Tel: 210 7586

# Equivalent Circuit of Induction Motors

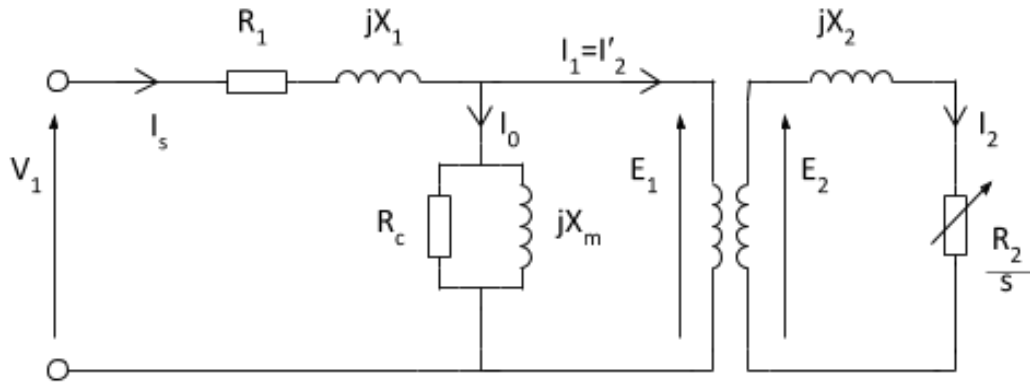

The rotor can be referred to the stator side

# Equivalent Circuit with Referred Rotor

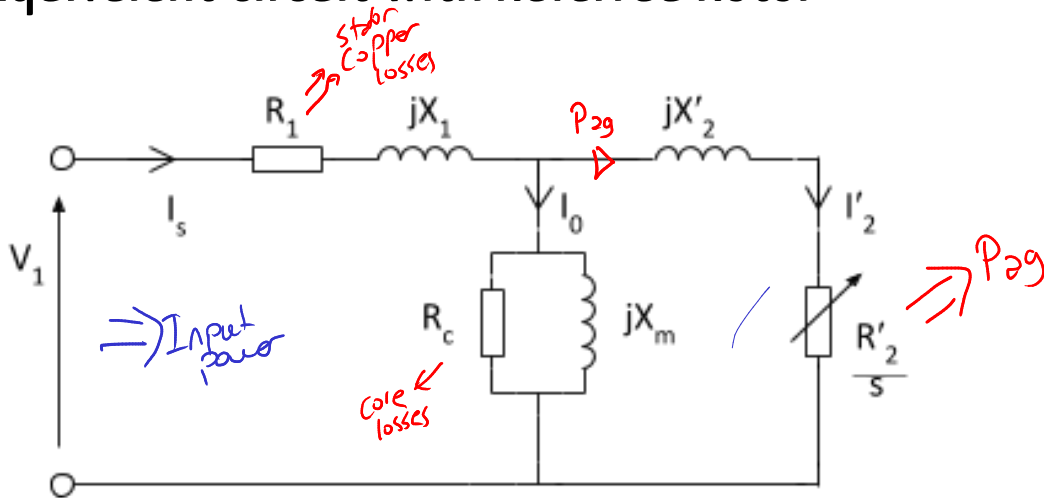

# Power Flow in Induction Motors

• Total Power:  $P_{in} = 3V_1 I_1 \cos(\theta)$

• Stator Copper Loss:  $P_{cu1} = 3I_1^2 r_1$

• Core Loss:  $P_c = 3 \frac{E_1^2}{R_c} \approx 3 \frac{V_1^2}{R_c}$

# Power Flow in Induction Motors

## Electrical Power Transferred to Rotor?

• Air-gap Power:

$$P_{ag} = P_{in} - P_{cu1} - P_c$$

or

$$P_{ag} = 3I_2'^2 \frac{r_2'}{s}$$

# Power Flow in Induction Motors

Not all the air-gap power dissipates as heat, most of it is converted to mechanical power

The equivalent circuit ( $\frac{r'_2}{s}$ ) can be separated into two components:

$$\frac{r'_2}{s} = r'_2 + \frac{1-s}{s} r'_2$$

*not a real resistance but a component to represent  $P_{mech}$ .*

$$P_{ag} = 3I_2'^2 \cdot \frac{r'_2}{s}$$

$$P_{ag} - P_{cu2} = P_{mech}$$


$$P_{ag} = P_{cu2} + P_{mech}$$

$\downarrow$   
 $3I_2'^2 \cdot r'_2$   
 rotor copper losses

$$3I_2'^2 \cdot \frac{r'_2}{s} - 3I_2'^2 \cdot r'_2$$

$$P_{mech} = 3I_2'^2 \left( r'_2 \frac{1-s}{s} \right)$$

# Rotor Side Equivalent Circuit

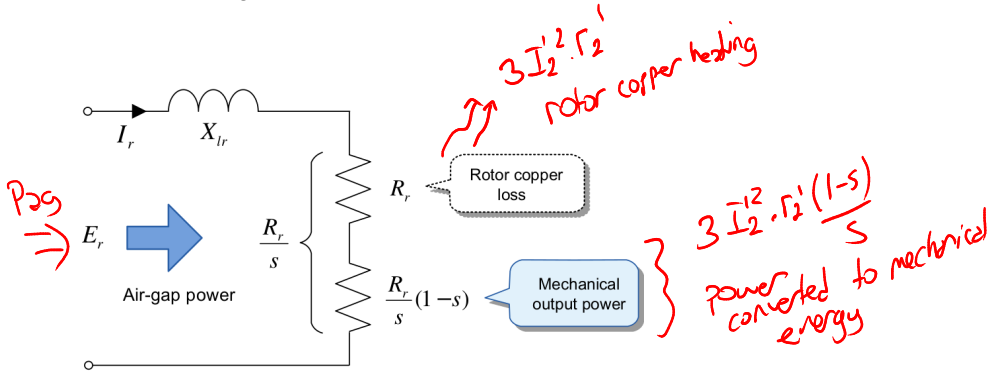

$\left(\frac{r_2'}{s}\right)$  is separated into two components

$$r_2' + \frac{(1-s)}{s} \cdot r_2' = \frac{r_2'}{s}$$

$s=1$  (rotor not rotating)


$r_2' \Rightarrow$  rotor heating  $\frac{r_2'(1-s)}{s} = 0$

$s=0$  (rotor at synch. speed)

$r_2' \Rightarrow \frac{r_2'(1-s)}{s} = \infty$  (open circuit)

$P_{ag}=0$


# Equivalent Circuit of Induction Motors

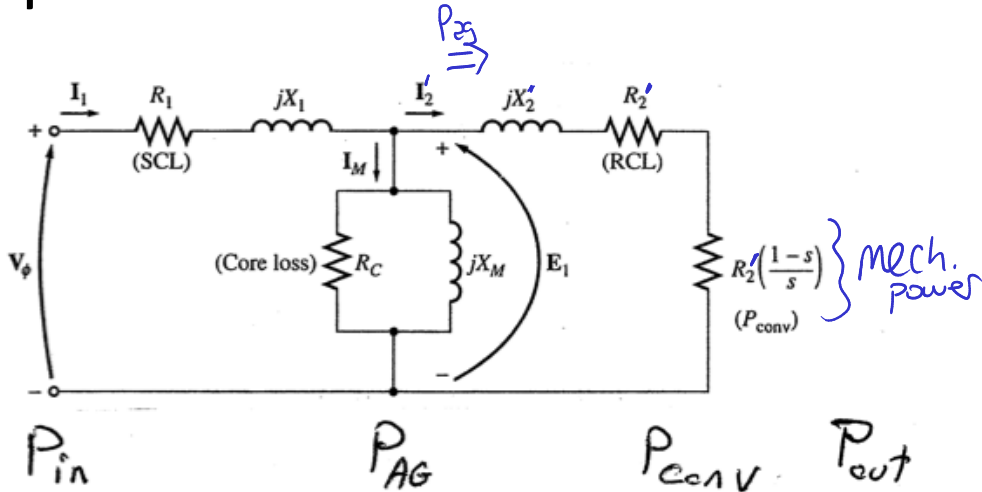



# Mechanical Power

Gap Power:  $P_{ag} = 3I_2'^2 \frac{r_2'}{s}$



Rotor Copper Loss:  $P_{cu2} = 3I_1^2 r_2'$

$P_{cu2}$  can also be expressed in terms of  $P_{ag}$

$$P_{cu2} = sP_{ag}$$


 slip.

# Mechanical Power

Gross Mech. Power = Gap Power - Rotor Copper Loss

Gap Power:  $P_{ag} = 3I_2'^2 \frac{r_2'}{s}$

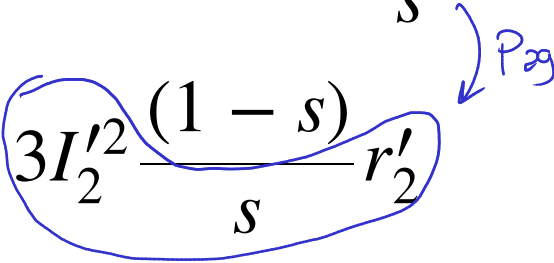$P_{mech} = 3I_2'^2 \frac{(1-s)}{s} r_2'$



$P_{mech} = (1-s)P_{ag}$

# Mechanical Power


Gross mechanical power is the power converted into mechanical form

Net power is the useful mechanical energy to drive the mechanical load

Net Power = Gross Power - Rotational Losses

$$\underline{P_{net}} = P_{mech} - P_{rot}$$

# Power Flow in Induction Motors

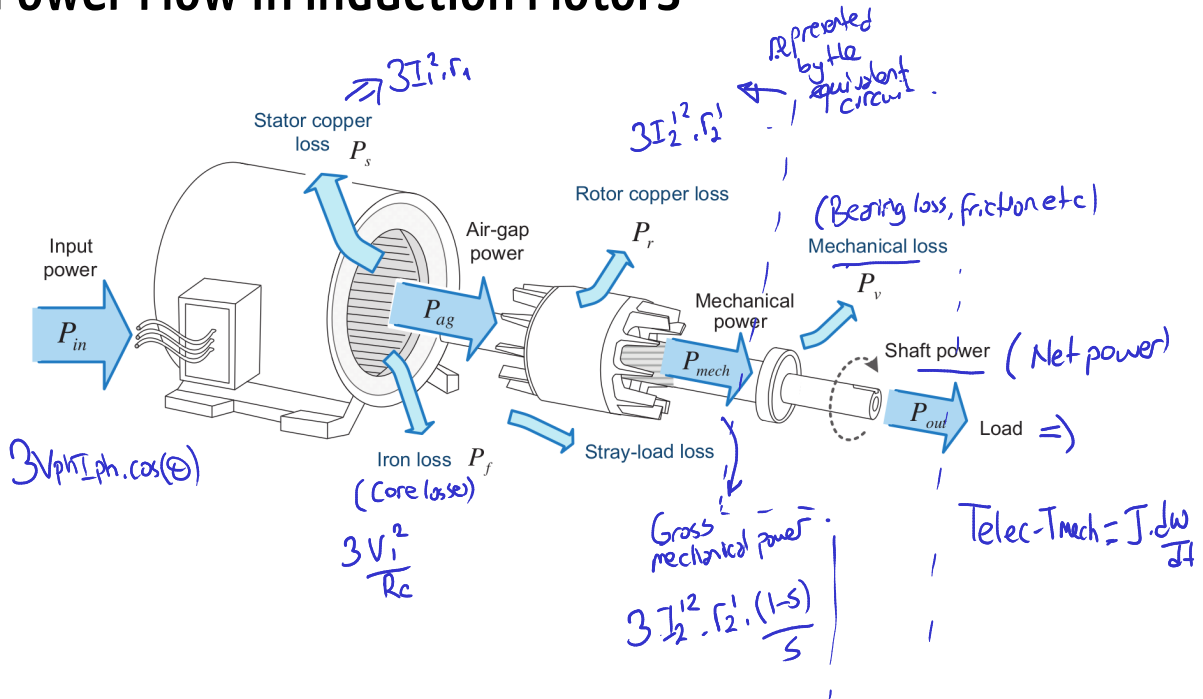

# Efficiency

Output Power / Input Power

$$\eta = \frac{P_{out}}{P_{in}}$$

Don't forget the rotational losses!