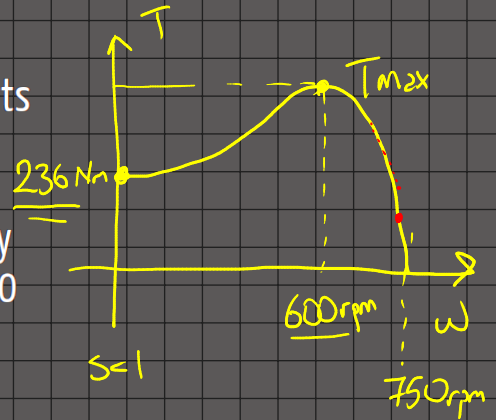


The following observations are made on a 3-phase, 50-Hz, Y-connected, 380 V rms line-to-line induction motor with negligible stator winding resistance and core loss.

i) At no-load the motor is rotating at 745 rpm.  $\Rightarrow N_{syn} = 750 \text{ rpm}$

ii) The stator can not be started with a heavy load, but it only starts when the load torque is reduced to 236 Nm

iii) When the motor is running at rated speed, the load is gradually increased and it is found that the rotor speed reduced down to 600 rpm, but after it decelerates and stops.




b-c) Calculate the referred rotor resistance and total leakage reactance (stator+rotor)?

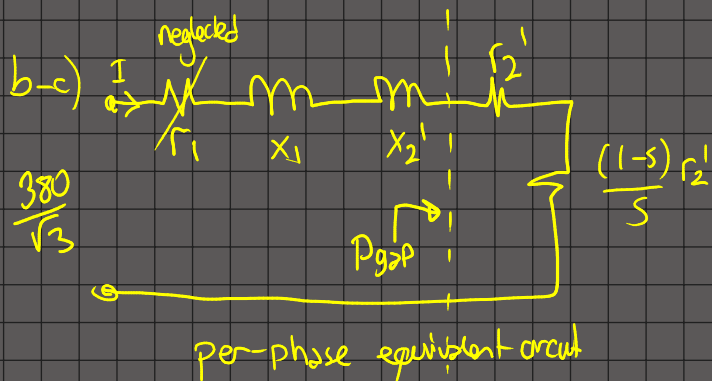2) Number of poles = ?  
 $s \approx 0$   $N_r = 745 \text{ rpm}$

50 Hz  $\rightarrow$  2 pole  $\Rightarrow \frac{120 \cdot f}{p} \Rightarrow 3000 \text{ rpm}$

4 pole  $\Rightarrow 1500 \text{ rpm}$   
 8 pole  $\Rightarrow 750 \text{ rpm}$



At max torque  
 $\rightarrow P_{gap}$  should be max.

$$s_{max-T} = \frac{750 - 600}{750} = 0,2$$

Torque is max. when  $P_{gap}$  is max

$\hookrightarrow P_{gap}$  is max when max. power transfer is satisfied.

$P_{gap}$  is max  $\Rightarrow$

$$\hookrightarrow (X_1 + X_2') = (r_2' + \frac{(1-s)r_2'}{s}) = \frac{r_2'}{s}$$

$$(X_1 + X_2') = \frac{r_2'}{0,2} \Rightarrow \boxed{5r_2' = (X_1 + X_2')}$$

$$T_{start} = 236 \text{ Nm} \quad (N_r = 0) \Rightarrow s = 1$$

$$T = \frac{3 V_1^2}{\left(\frac{r_1}{s} + \frac{r_2'}{s}\right)^2 + (X_1 + X_2')^2} \cdot \frac{r_2'}{s} \cdot \frac{1}{\omega_s}$$

mech. synchronous speed

$\leftarrow s = 1$



$$T = \frac{3V_1^2}{r_2'^2 + 25r_2'^2} \cdot \frac{r_2'}{1} \cdot \frac{1}{\omega_s}$$

$$\omega_s = \frac{2\pi f_e}{(P/2)} = \frac{2\pi \cdot 50}{4}$$

mech. synch. speed

$$V_1 = 380/\sqrt{3}$$


$$T = \frac{3 \left(\frac{380}{\sqrt{3}}\right)^2}{26r_2'^2} \cdot \frac{r_2'}{\frac{2\pi \cdot 50}{4}} \Rightarrow \boxed{r_2' = 0,3 \Omega} \quad \boxed{(X_1 + X_2') = 1,5 \Omega}$$

d) If the rotational power is 1518 W, find the air-gap power, rotor copper loss, internal mechanical power and the net output power when the rotor is rotating at 712.5 rpm


$$N_r = 712,5 \text{ rpm}$$

$$N_s = 750 \text{ rpm}$$

$$s = \frac{750 - 712,5}{750} = 0,05$$

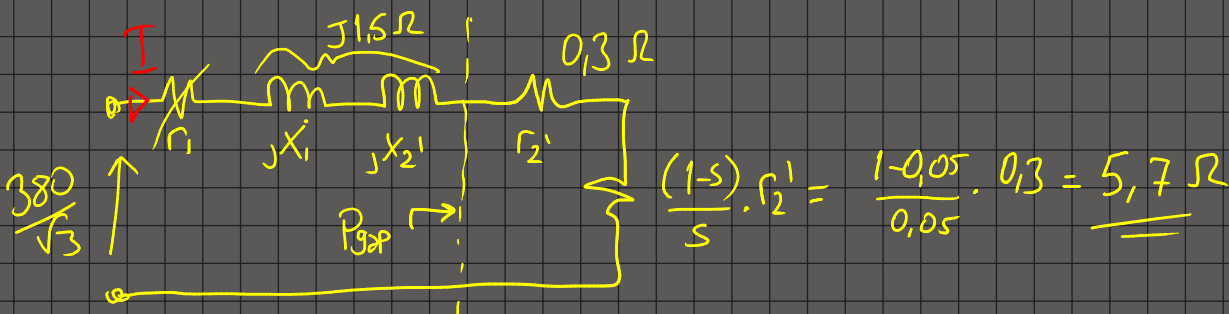
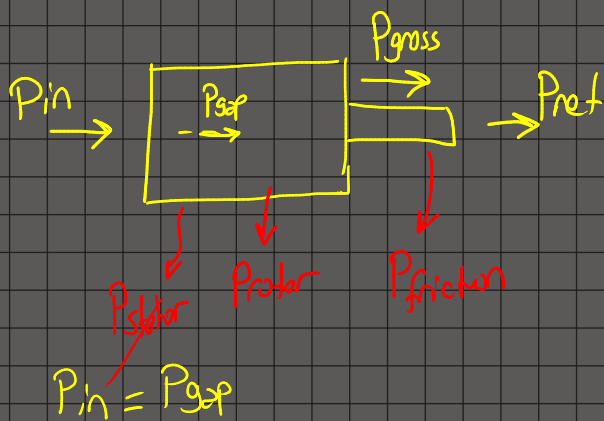
$$I = \frac{380/\sqrt{3}}{\sqrt{6^2 + 1,5^2}} = 35,47 \text{ A}$$



$$P_{gap} = 3I^2 \cdot \frac{r_2'}{s}$$

$$= 3(35,47)^2 \cdot 6 = 22,65 \text{ kW}$$

$$P_{\text{copper(rotor)}} = 3I^2 \cdot r_2'$$

$$= 3(35,47)^2 \cdot 0,3 = 1,13 \text{ kW}$$

$$P_{\text{gross mech}} = 22,65 - 1,13 \text{ kW}$$

$$= 21,52 \text{ kW}$$

$$P_{\text{net}} = P_{\text{gross}} - P_{\text{friction}}$$

$$= 21,52 - 1,52 = 20 \text{ kW}$$

Efficiency

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{20 \text{ kW}}{22,65 \text{ kW}} = 88,3\%$$