

EE-463 STATIC POWER CONVERSION-I

Diode Rectifiers


Ozan Keysan

keysan.me

Office: C-113 • Tel: 210 7586

Line Frequency Diode Rectifiers

Line Frequency Diode Rectifiers

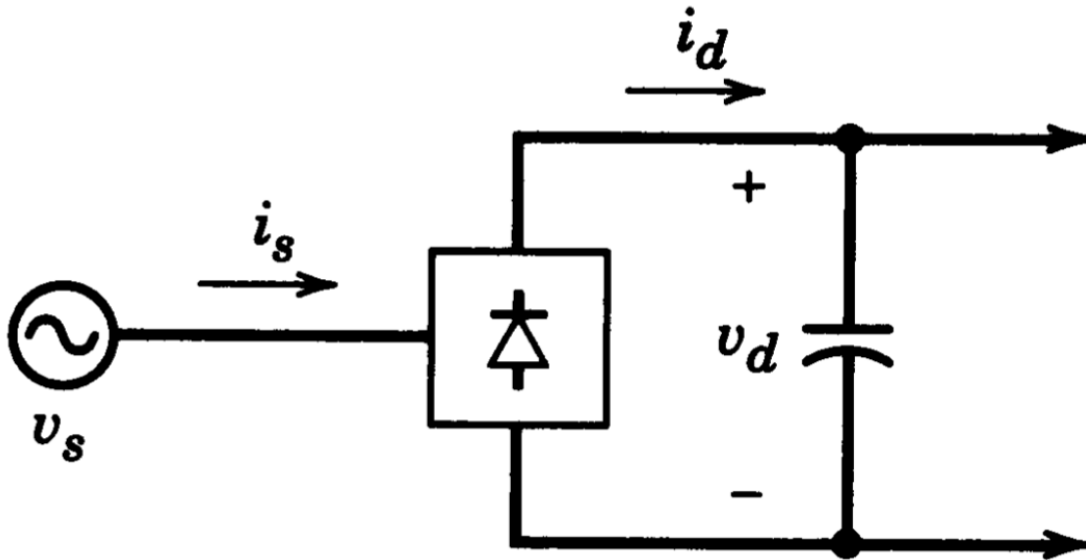

Line Frequency Diode Rectifiers

Ideal Rectifier

Line Frequency Diode Rectifiers

Ideal Rectifier

- Ripple free DC output

Line Frequency Diode Rectifiers

Ideal Rectifier

- Ripple free DC output
- Sinusoidal (THD=0) input current

Line Frequency Diode Rectifiers

Ideal Rectifier

- Ripple free DC output
- Sinusoidal (THD=0) input current
- High Efficiency


Line Frequency Diode Rectifiers

Ideal Rectifier

- Ripple free DC output
- Sinusoidal (THD=0) input current
- High Efficiency
- Small Size (High Power Density)


Simplest Case: One diode with resistive load

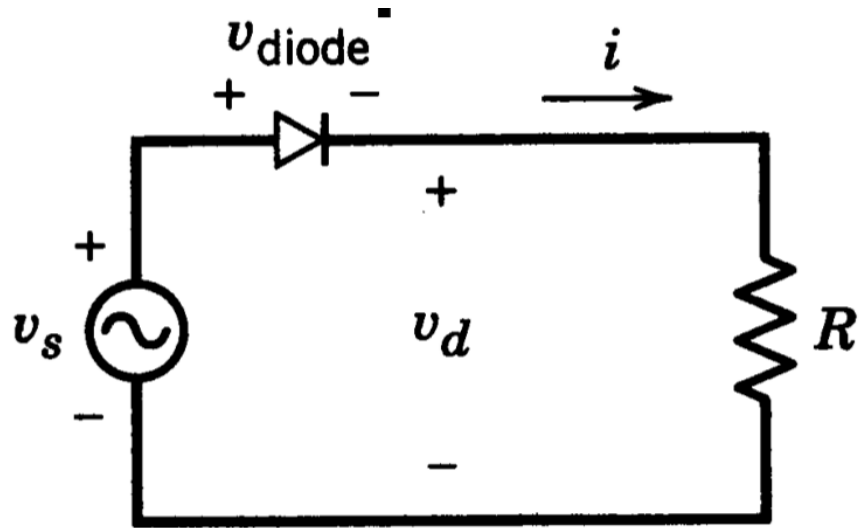Simplest Case: One diode with resistive load



Can you plot the voltage-current waveforms?

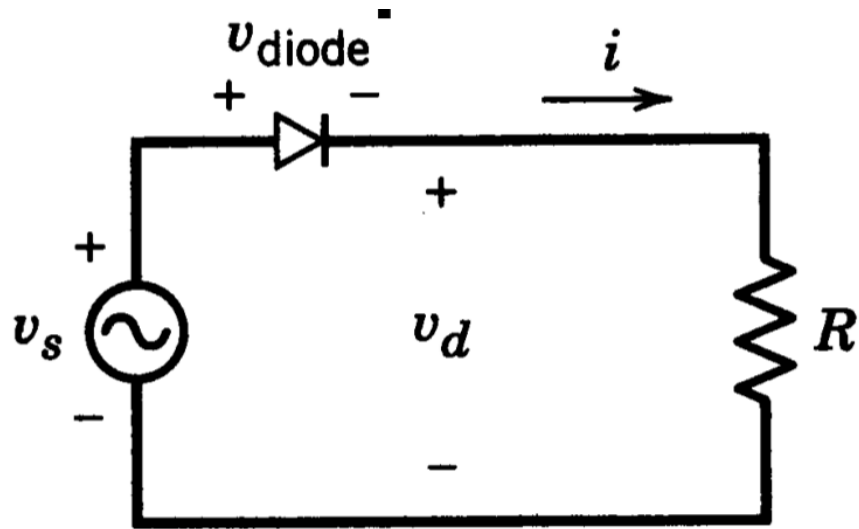Simplest Case: One diode with resistive load




Can you plot the voltage-current waveforms?

What about the average voltage?


One Diode with R-L Load

One Diode with R-L Load

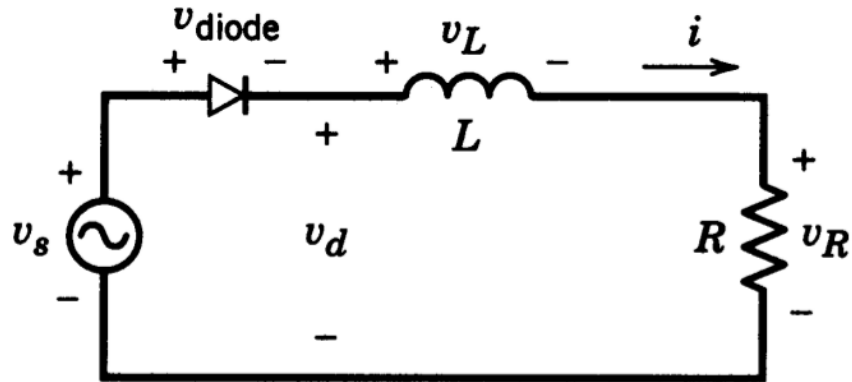

One Diode with R-L Load

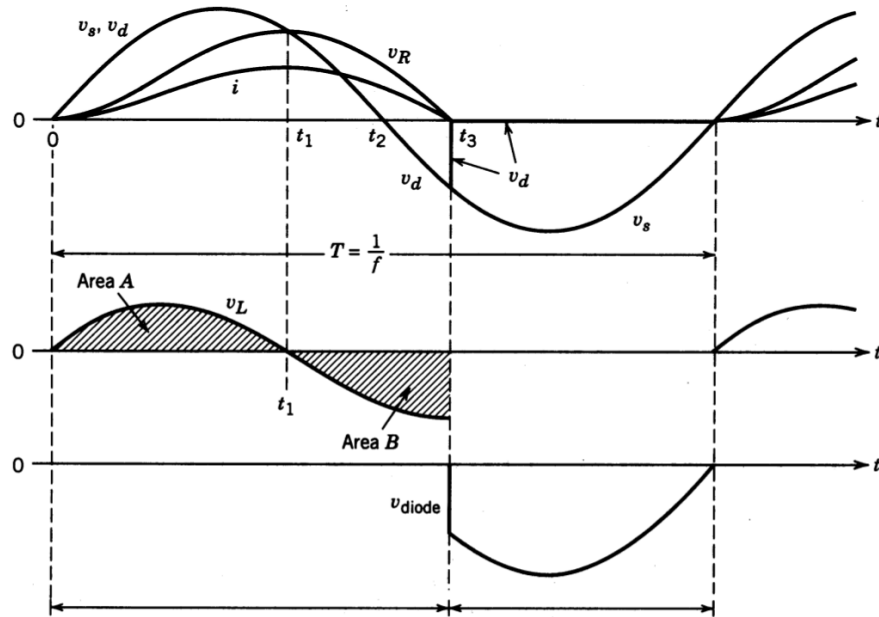Diode continues to conduct for extended period



One Diode with R-L Load

One Diode with R-L Load

Diode continues to conduct for extended period:

Commutation!

One Diode with R-L Load

Diode continues to conduct for extended period:

Commutation!

How does the average voltage change with commutation?

One Diode with R-L Load

Diode continues to conduct for extended period:

Commutation!

How does the average voltage change with commutation?

It becomes smaller!


Single-Phase Diode Rectifier



 Drawing

Commercial Bridge Rectifiers

Single-Phase Diode Rectifier

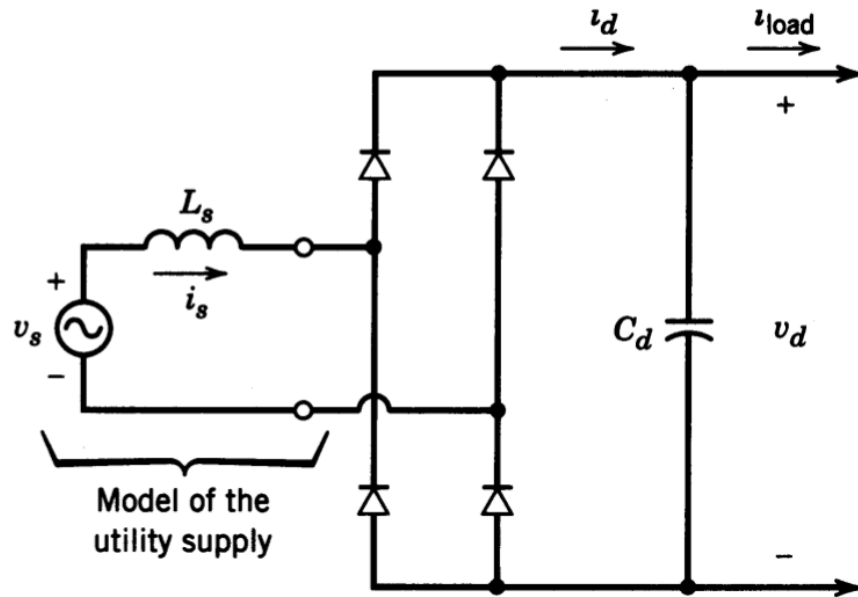


Let's assume ideal source ($L_s=0$) to start with

Single-Phase Diode Rectifier

Also assume load draws constant current (i_d)


Single-Phase Diode Rectifier

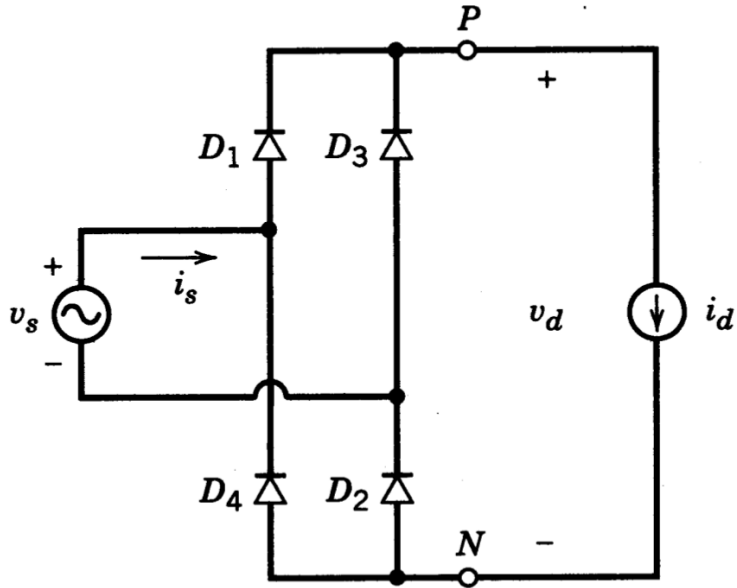Also assume load draws constant current (i_d)



Single-Phase Diode Rectifier

You can redraw it as:

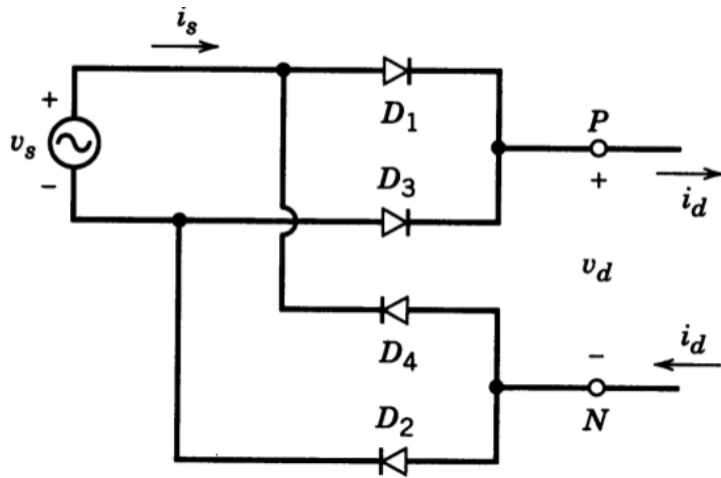

Single-Phase Diode Rectifier

Can you calculate the average output voltage?

Single-Phase Diode Rectifier

Can you calculate the average output voltage?

Can you plot the input current waveform?



Single-Phase Diode Rectifier

Can you calculate the average output voltage?

Can you plot the input current waveform?



What about the THD of input current?

Single-Phase Diode Rectifier

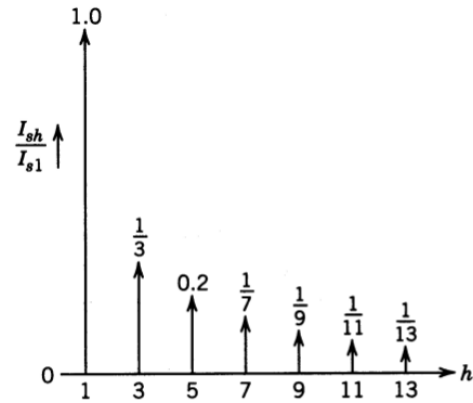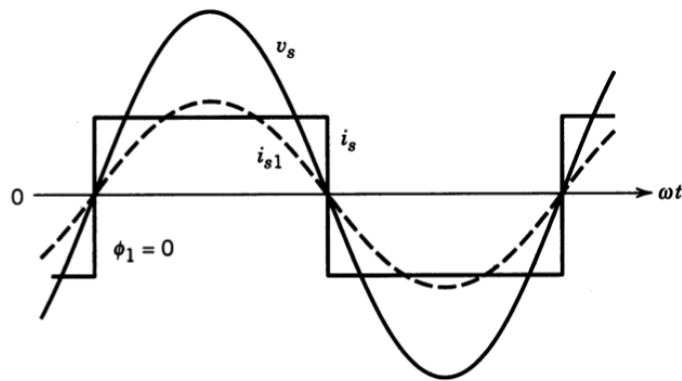



THD of current (square waveform)=

Single-Phase Diode Rectifier

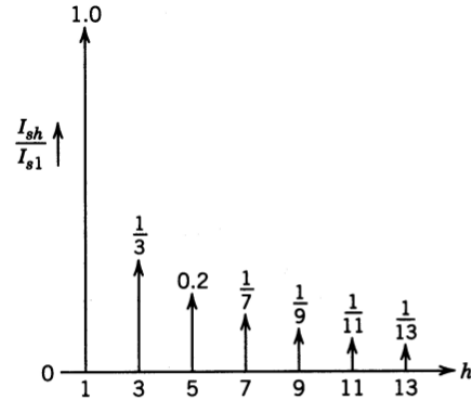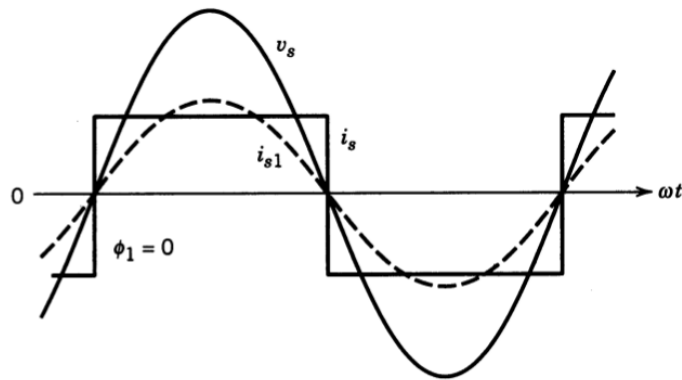

$$\text{THD of current (square waveform)} = \frac{\sqrt{1 - \frac{2\sqrt{2}}{\pi}^2}}{\frac{2\sqrt{2}}{\pi}}$$

Single-Phase Diode Rectifier

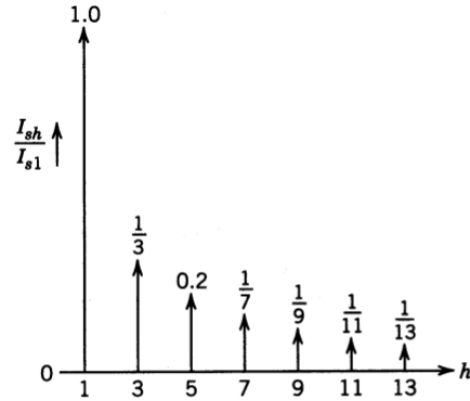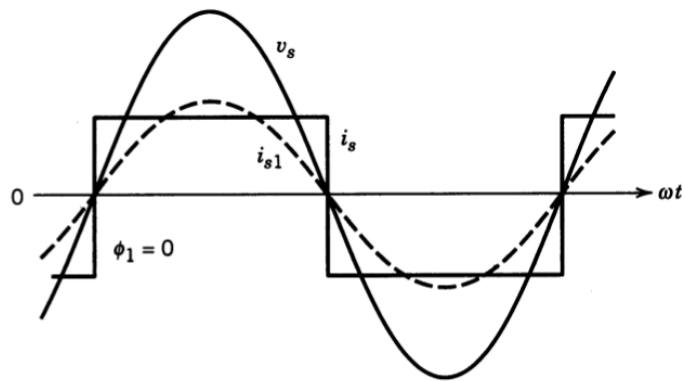


$$\text{THD of current (square waveform)} = \frac{\sqrt{0.19}}{0.9} = 0.484$$

Short Review of Fourier Series

Short Review of Fourier Series

All waveforms, no matter what you scribble or observe in the universe, are actually just the sum of simple sinusoids of different frequencies.

Fourier Series

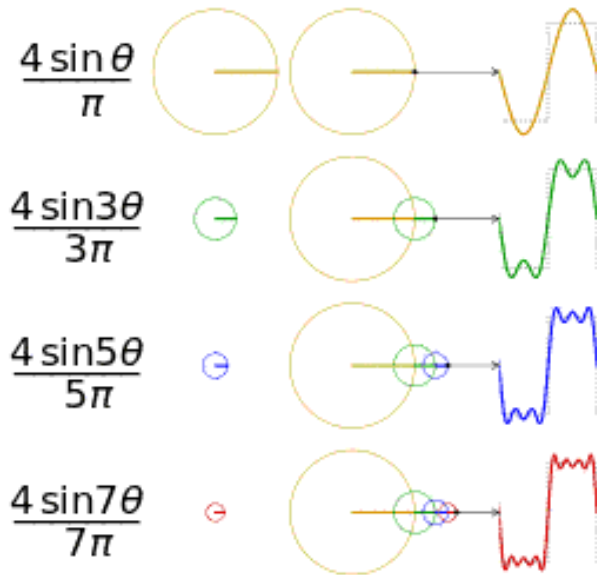

[Interactive Fourier Series](#), [Complex Orbits](#), [Singing Train](#), [Useful applets](#), [Fourier examples](#)

[More Useful Links on Fourier Series](#)

Fourier Series

$$f(x) = \frac{1}{2} a_0 + \sum_{n=1}^{\infty} a_n \cos(nx) + \sum_{n=1}^{\infty} b_n \sin(nx),$$

Fourier Series

$$f(x) = \frac{1}{2} a_0 + \sum_{n=1}^{\infty} a_n \cos(nx) + \sum_{n=1}^{\infty} b_n \sin(nx),$$

Coefficients

$$\begin{cases} a_0 &= \frac{1}{2\pi} \int_{-\pi}^{\pi} f(x) dx, \\ a_n &= \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \cos(nx) dx, \quad 1 \leq n \\ b_n &= \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \sin(nx) dx, \quad 1 \leq n. \end{cases}$$

Some Important Functions

Some Important Functions

Even function:

Some Important Functions

Even function: $f(-t) = f(t)$

Some Important Functions

Even function: $f(-t) = f(t) \rightarrow b_h = 0$

Some Important Functions

Even function: $f(-t) = f(t) \rightarrow b_h = 0$

Odd function:

Some Important Functions

Even function: $f(-t) = f(t) \rightarrow b_h = 0$

Odd function: $f(-t) = -f(t)$

Some Important Functions

Even function: $f(-t) = f(t) \rightarrow b_h = 0$

Odd function: $f(-t) = -f(t) \rightarrow a_h = 0$

Some Important Functions

Even function: $f(-t) = f(t) \rightarrow b_h = 0$

Odd function: $f(-t) = -f(t) \rightarrow a_h = 0$

Half-wave symmetry:

Some Important Functions

Even function: $f(-t) = f(t) \rightarrow b_h = 0$

Odd function: $f(-t) = -f(t) \rightarrow a_h = 0$

Half-wave symmetry: $f(t) = -f(t + T/2)$

Some Important Functions

Even function: $f(-t) = f(t) \rightarrow b_h = 0$

Odd function: $f(-t) = -f(t) \rightarrow a_h = 0$

Half-wave symmetry: $f(t) = -f(t + T/2)$

$\rightarrow a_h = b_h = 0$ for even harmonics

Some Important Functions

Even function: $f(-t) = f(t) \rightarrow b_h = 0$

Odd function: $f(-t) = -f(t) \rightarrow a_h = 0$

Half-wave symmetry: $f(t) = -f(t + T/2)$

$\rightarrow a_h = b_h = 0$ for even harmonics

Even quarter-wave:

Some Important Functions

Even function: $f(-t) = f(t) \rightarrow b_h = 0$

Odd function: $f(-t) = -f(t) \rightarrow a_h = 0$

Half-wave symmetry: $f(t) = -f(t + T/2)$

$\rightarrow a_h = b_h = 0$ for even harmonics

Even quarter-wave: Even function and Half-wave symmetry

Some Important Functions

Even function: $f(-t) = f(t) \rightarrow b_h = 0$

Odd function: $f(-t) = -f(t) \rightarrow a_h = 0$

Half-wave symmetry: $f(t) = -f(t + T/2)$

$\rightarrow a_h = b_h = 0$ for even harmonics


Even quarter-wave: Even function and Half-wave symmetry

$\rightarrow b_h = 0$ for all harmonics

$\rightarrow a_h = 0$ for even harmonics


Effect of Line Inductance

Effect of Line Inductance

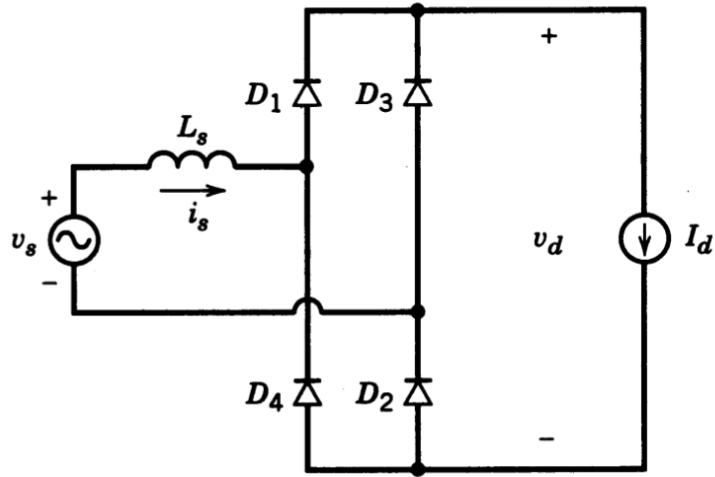

Can you still draw square current from grid?

Effect of Line Inductance

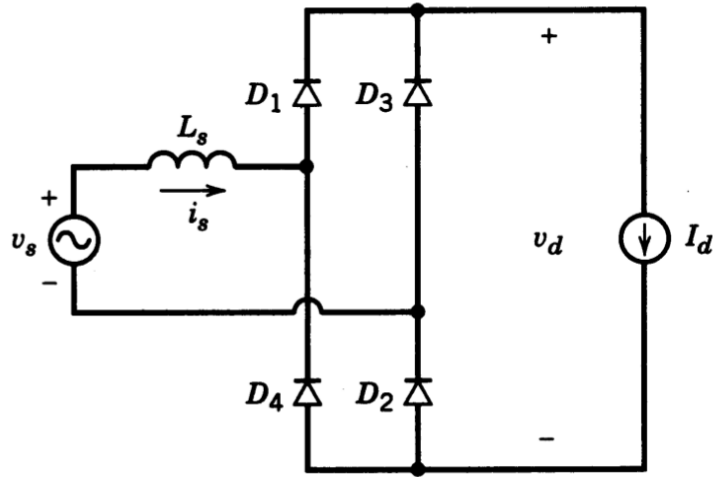


Can you still draw square current from grid?


There has to be finite time between $+I_d$ to $-I_d$ transition.

Let's start with a simple circuit

Let's start with a simple circuit

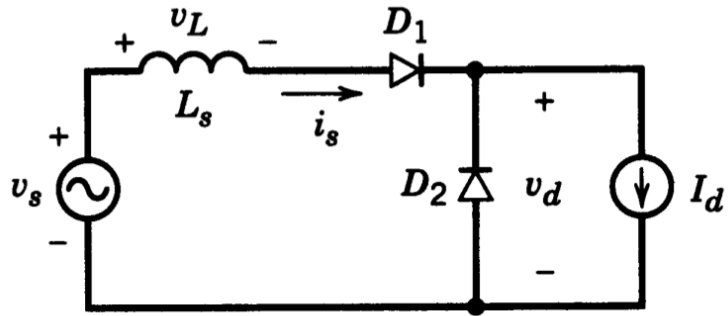


Let's start with a simple circuit

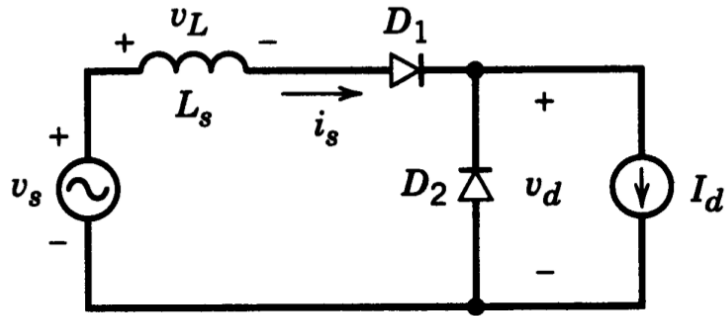

Draw the equivalent circuits at each interval

Voltage Waveforms

Voltage Waveforms

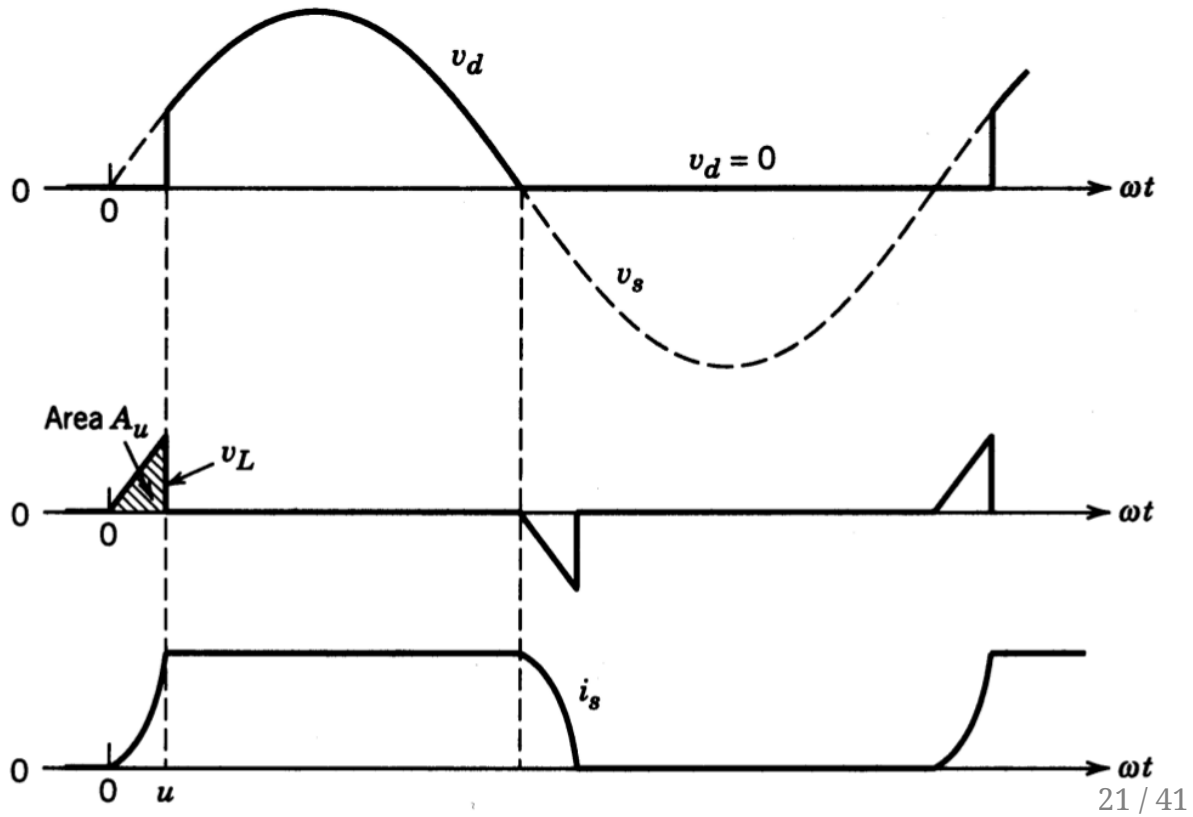

How to calculate the commutation period (u)?

How to calculate the commutation period (μ)?

$$\cos(\mu) = 1 - \frac{\omega L_s I_d}{\sqrt{2}V_s}$$

How to calculate the commutation period (μ)?

$$\cos(\mu) = 1 - \frac{\omega L_s I_d}{\sqrt{2} V_s}$$

- L_s, I_d increases commutation time

How to calculate the commutation period (μ)?

$$\cos(\mu) = 1 - \frac{\omega L_s I_d}{\sqrt{2} V_s}$$

- L_s, I_d increases commutation time
- V_s reduces commutation time

How does the average voltage changes?

How does the average voltage changes?

$$V_d = \frac{0.9V_s}{2} - \frac{Au}{2\pi}$$


How does the average voltage changes?

$$V_d = \frac{0.9V_s}{2} - \frac{Au}{2\pi}$$


Reduction in average voltage

$$\Delta V_d = \frac{\omega L_s}{2\pi} I_d$$

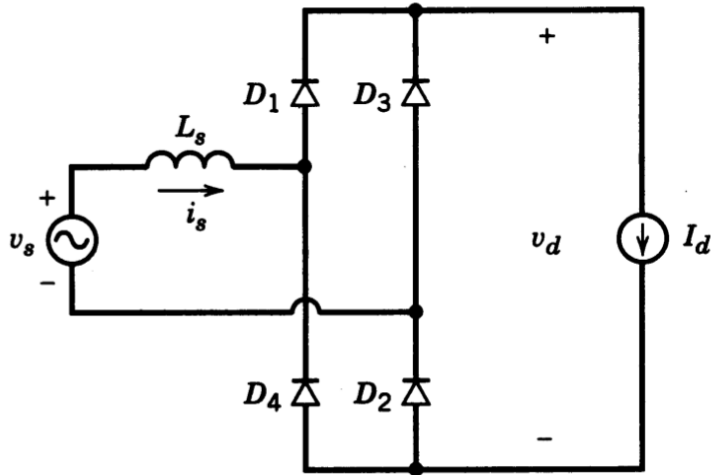What about commutation in single phase rectifier?



Voltage-Current Waveforms

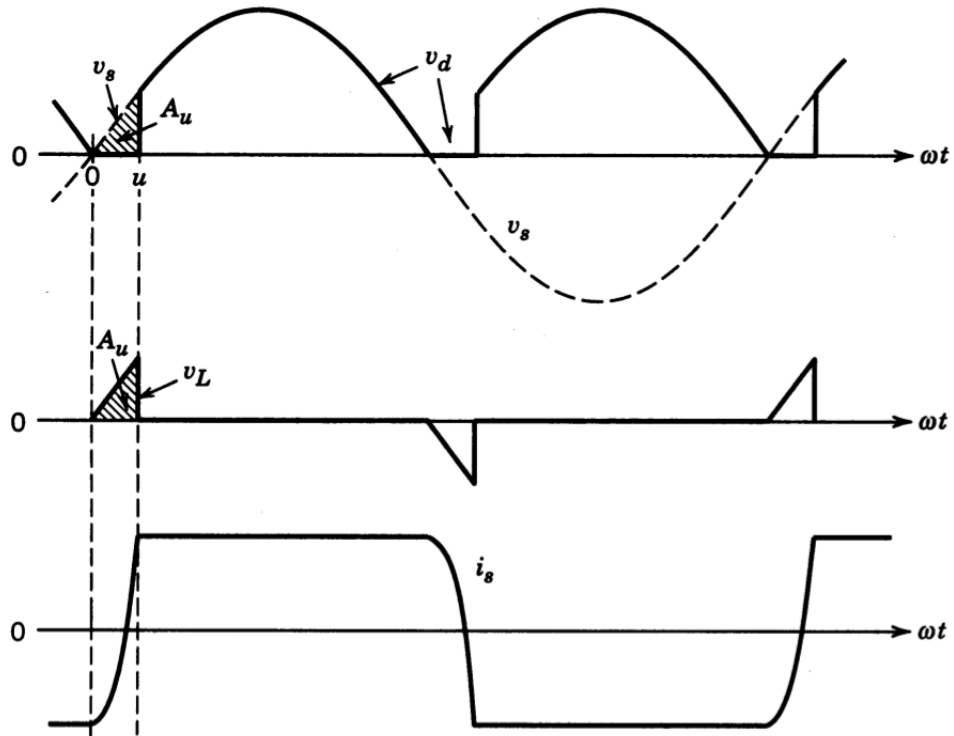

How does the average voltage changes?

How does the average voltage changes?

Similar to previous case, but:

- Current goes from $-I_d$ to I_d
- Commutation happens twice ($2A_u$)

How does the average voltage changes?


Similar to previous case, but:

- Current goes from $-I_d$ to I_d
- Commutation happens twice ($2A_u$)

$$V_d = 0.9V_s - \frac{2\omega L_s}{\pi} I_d$$


Rectifier with DC Side Voltage

Rectifier with DC Side Voltage

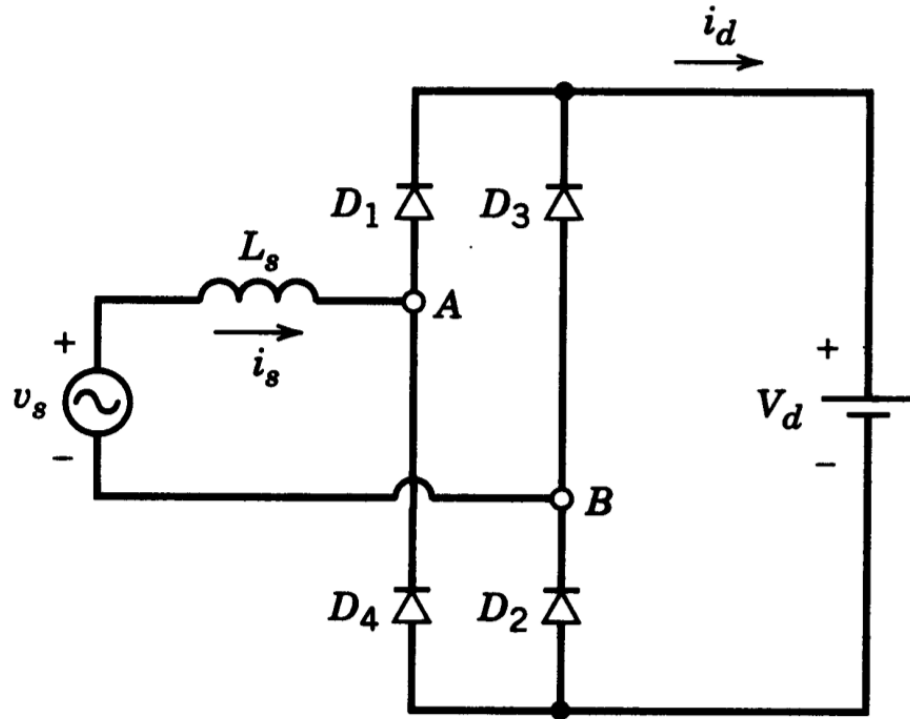

Can you plot the voltage waveforms?

Can you plot the voltage waveforms?

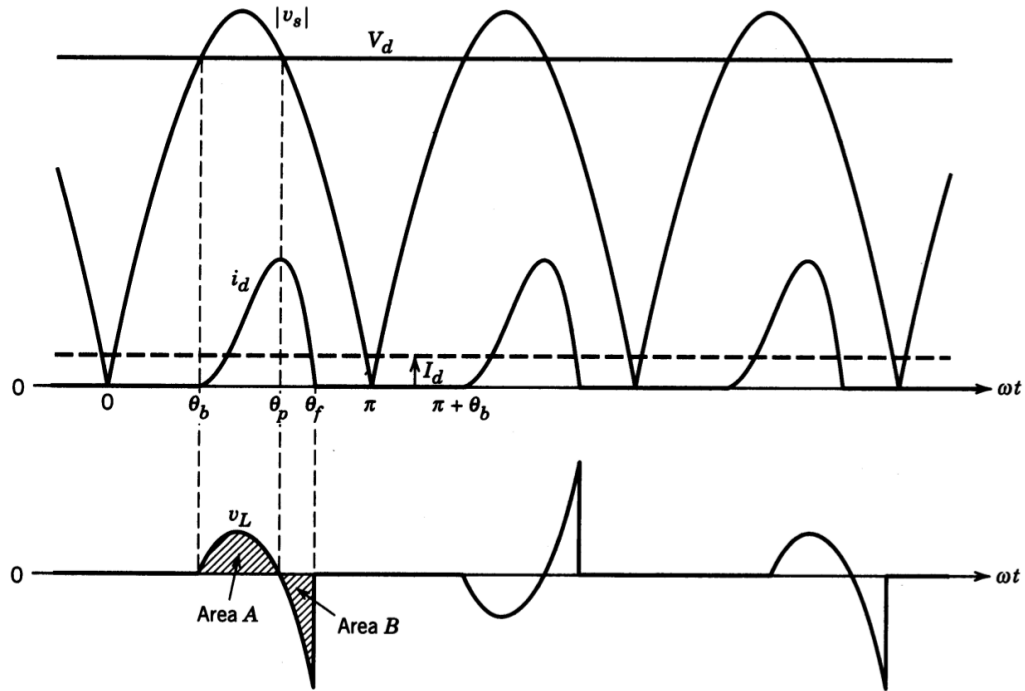

Average current

$$I_{d_{av}} = \frac{\int_b^f i(\theta) d\theta}{\pi}$$

Average current

$$I_{d_{av}} = \frac{\int_b^f i(\theta) d\theta}{\pi}$$

What is the short circuit current (when $V_d=0$)?

Average current

$$I_{d_{av}} = \frac{\int_b^f i(\theta) d\theta}{\pi}$$

What is the short circuit current (when $V_d=0$)?


$$I_{d_{(short-circuit)}} = \frac{V_s}{\omega L_s}$$

Some Alternative Topologies


Some Alternative Topologies

Centre-Tap Rectifier

Centre-Tap Rectifier

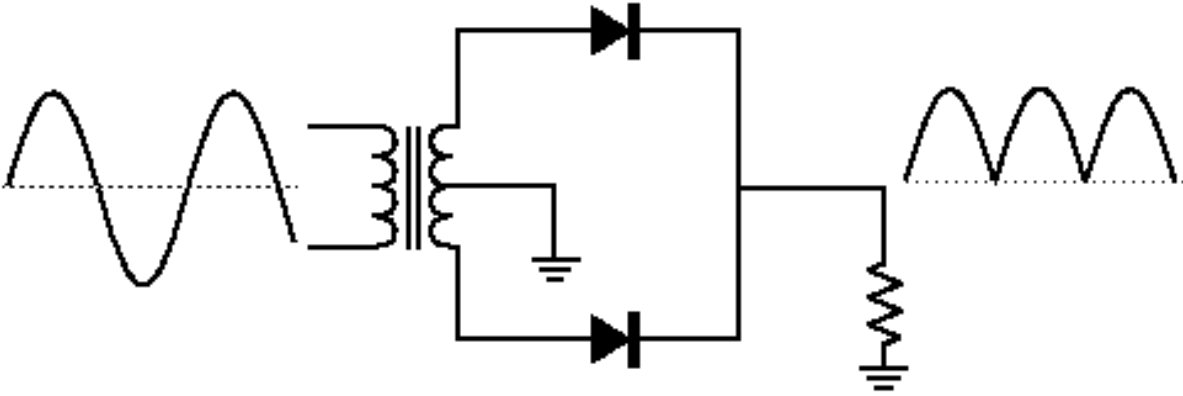

Centre-Tap Rectifier

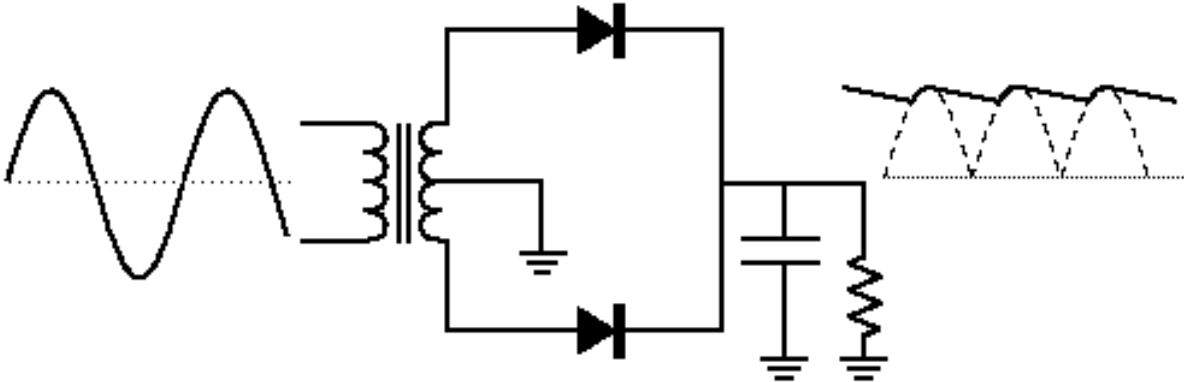

Centre-Tap Rectifier

Can you compare it with the full-bridge rectifier?

in terms of:

Centre-Tap Rectifier

Can you compare it with the full-bridge rectifier?

in terms of:

- Number of Diodes (and ratings)

Centre-Tap Rectifier

Can you compare it with the full-bridge rectifier?

in terms of:

- Number of Diodes (and ratings)
- Cost

Centre-Tap Rectifier


Can you compare it with the full-bridge rectifier?

in terms of:

- Number of Diodes (and ratings)
- Cost
- Current Waveform


Voltage Doubler Rectifier

Voltage Doubler Rectifier

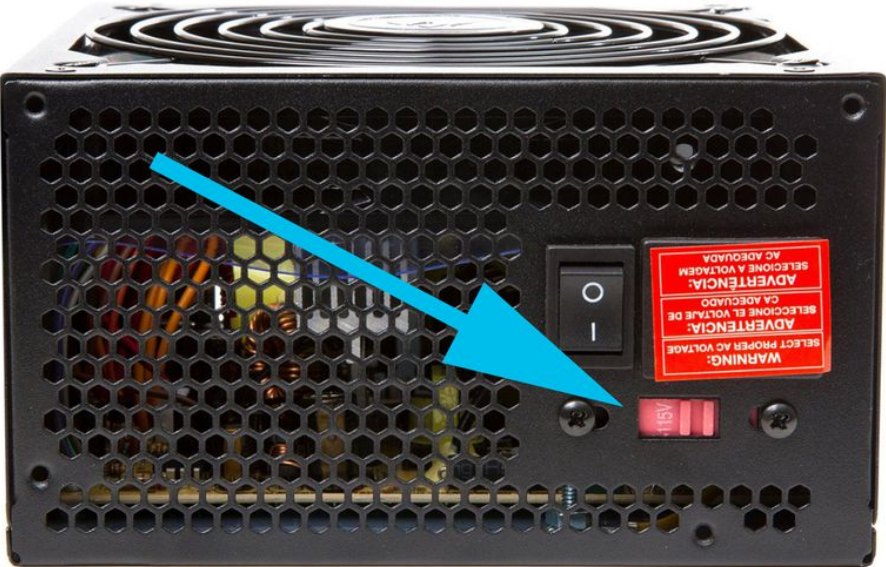

Voltage Doubler Rectifier

Voltage Doubler Rectifier

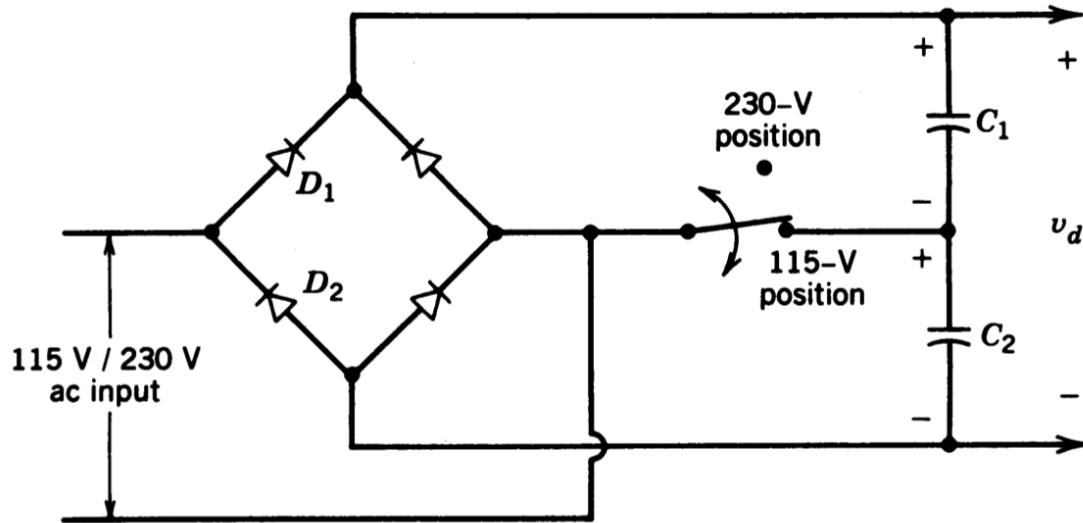

Quiz

Quiz

Many single-phase rectifiers are connected to three phase system.

Can you plot the neutral line current?

Effects of Single Phase Rectifiers

Effects of Single Phase Rectifiers

- . Voltage Waveform (Notching)

Effects of Single Phase Rectifiers


- Voltage Waveform (Notching)
- Neutral Line Current

Effects of Single Phase Rectifiers

- Voltage Waveform (Notching)
- Neutral Line Current
- THD


Effects of Single Phase Rectifiers

Current Distortion

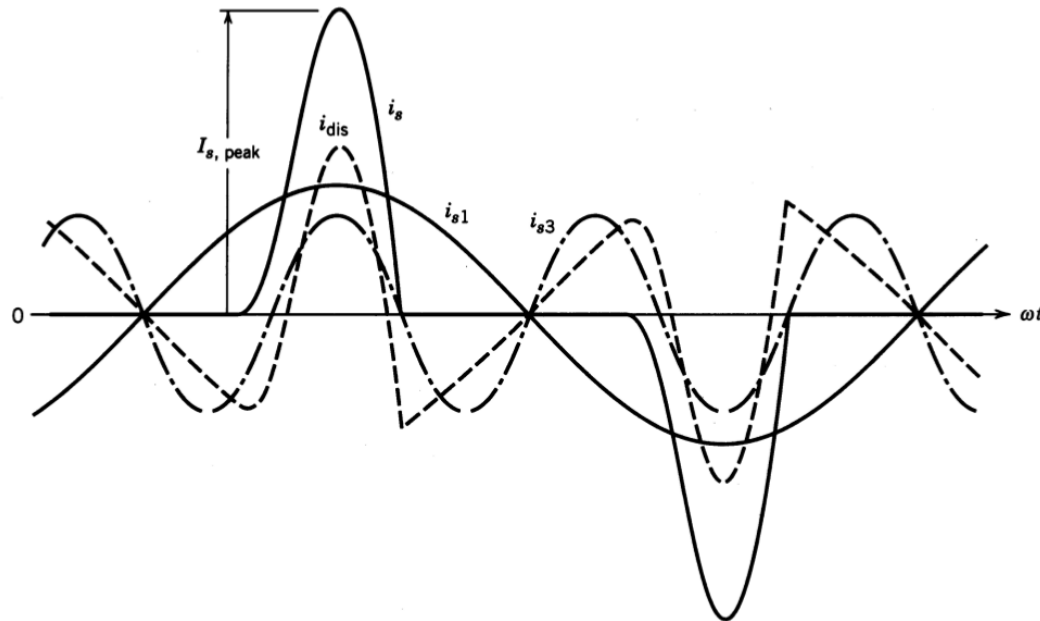


Effects of Single Phase Rectifiers

Line Voltage Distortion

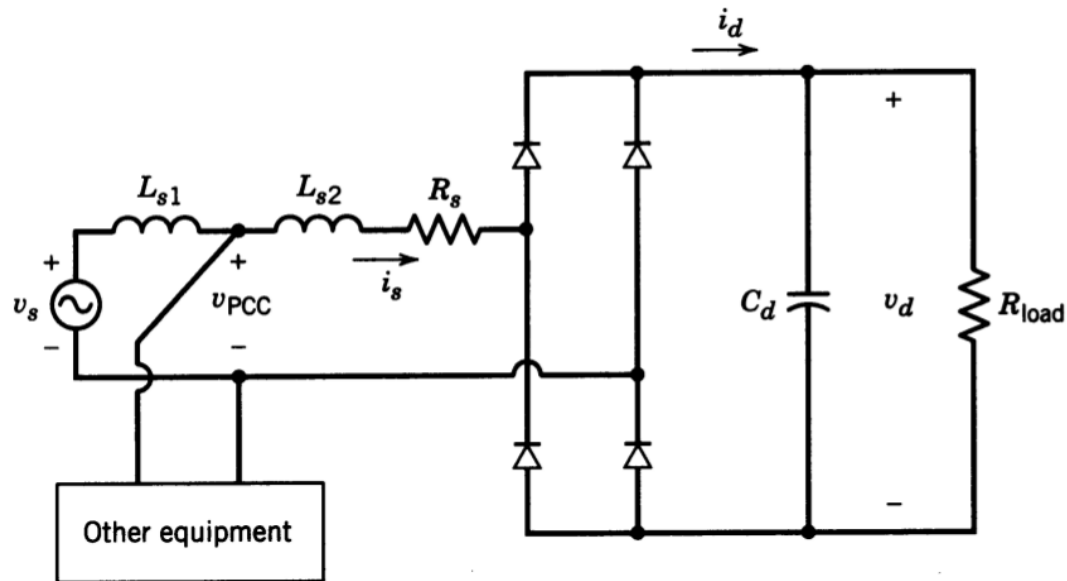

Effects of Single Phase Rectifiers

Neutral Line Current

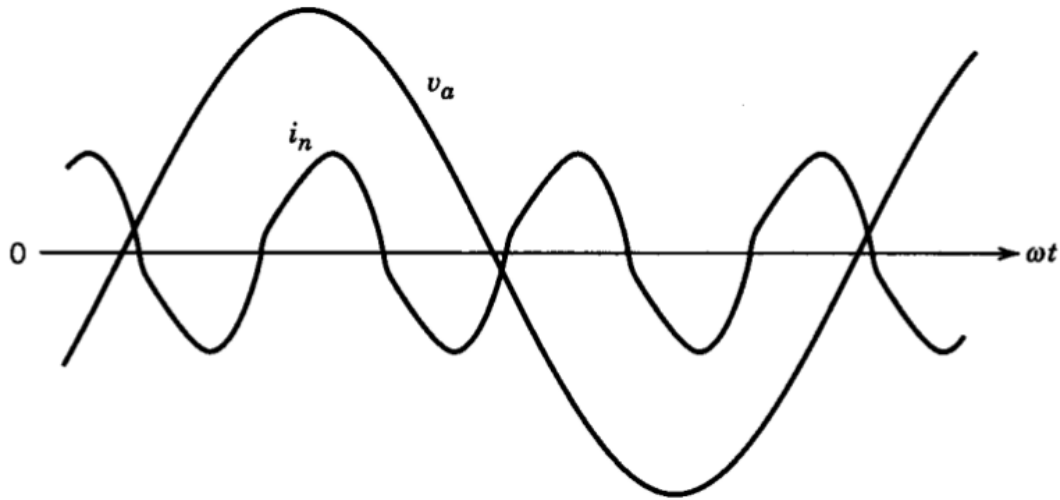

You can download this presentation from:
keysan.me/ee463.