

EE-464 STATIC POWER CONVERSION-II


Bridge Converters

Ozan Keysan

keysan.me

Office: C-113 • Tel: 210 7586

Full Bridge Isolating Converter

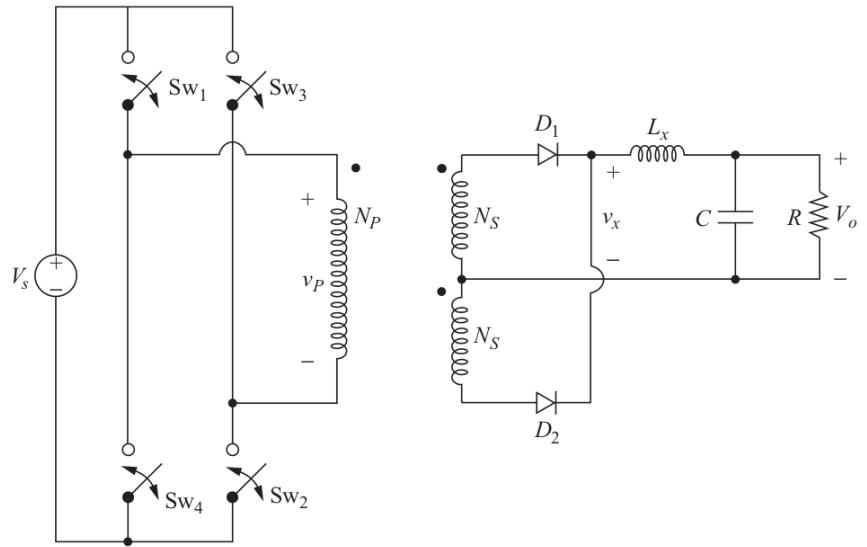


Compact solution for high power levels ($>500W$)

Similar to push-pull converter


Full Bridge Converter: Operating Modes

Full Bridge Converter: Operating Modes

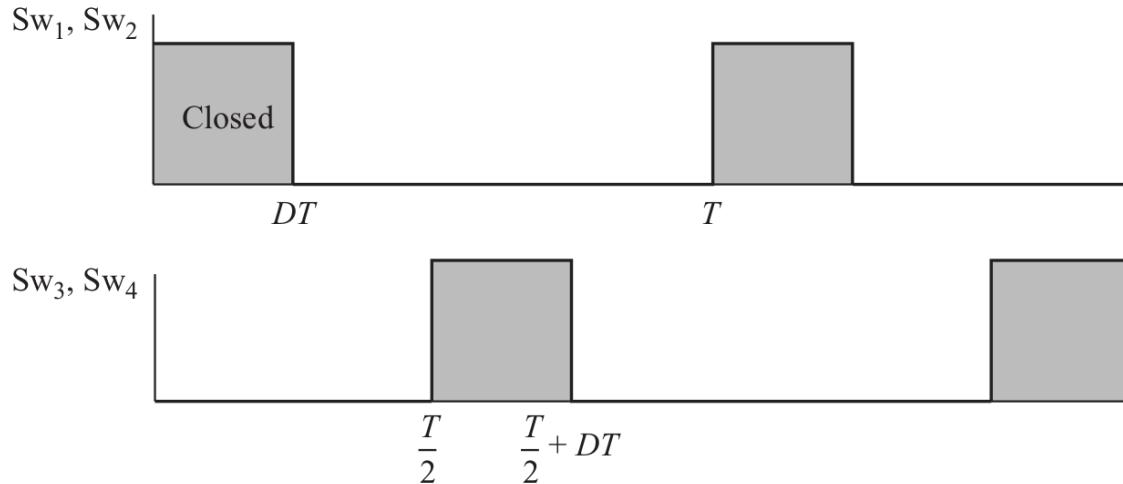


$S_1 \& S_2, S_3 \& S_4$ operate alternatively

Full Bridge Converter: Operating Modes

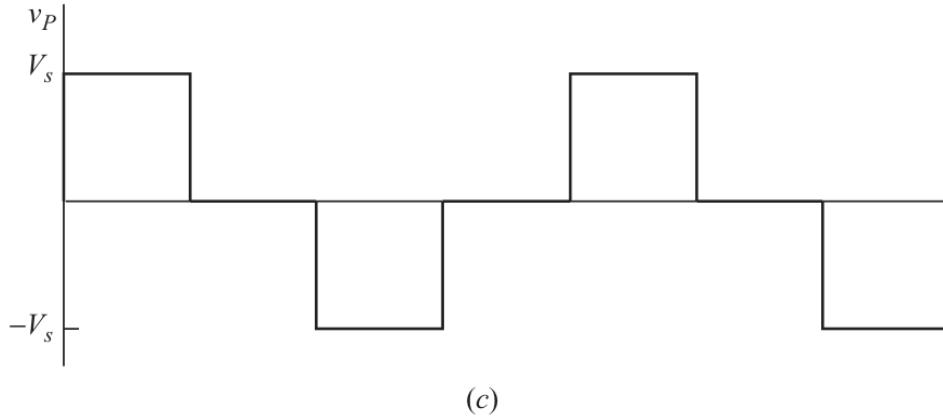

(c)

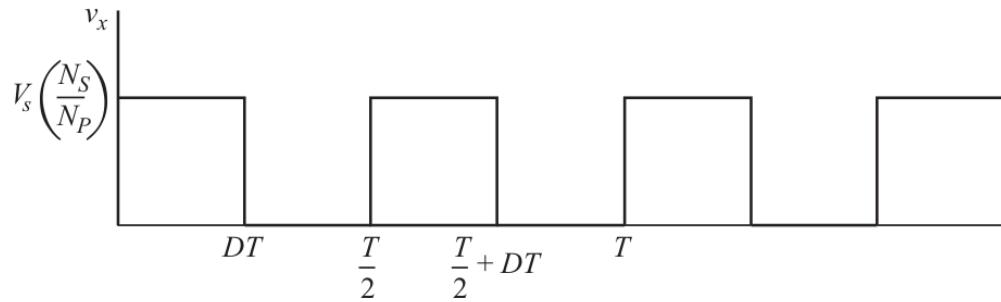


Full Bridge Converter

$$V_o = 2V_s \left(\frac{N_s}{N_p} \right) D$$

$$D < 0.5$$

Same with the push-pull converter

Half Bridge Isolating Converter

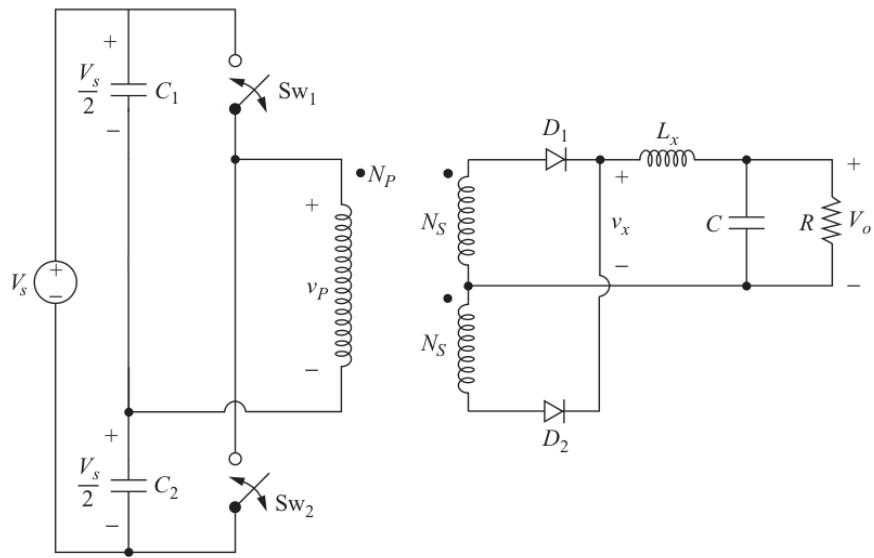


Derived from the Buck Converter



S_1, S_2 turned on alternatively each for t_{on} , then both off for Δ

6 / 48

Half Bridge Converter: Operating Modes

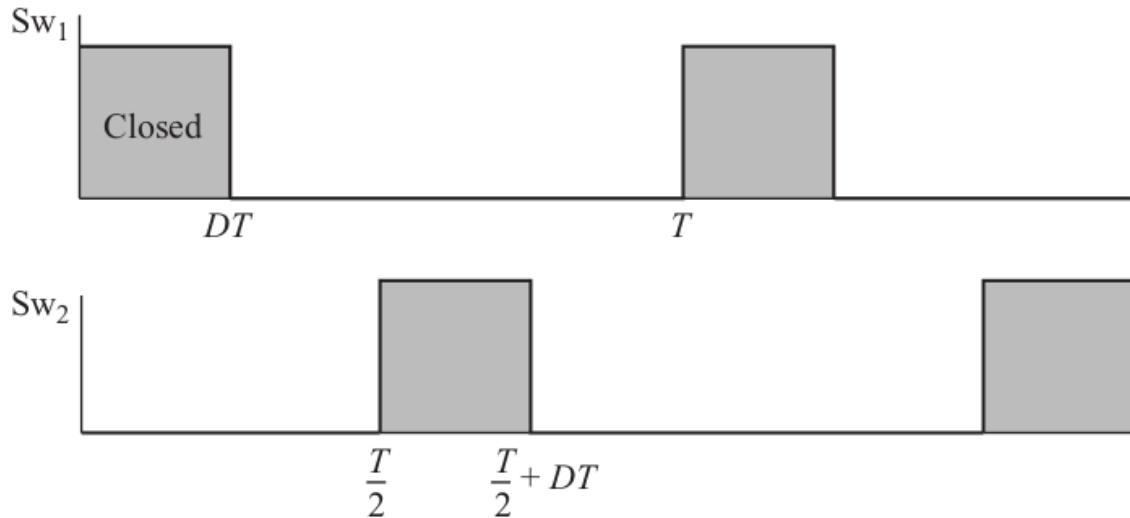

Half Bridge Converter: Operating Modes

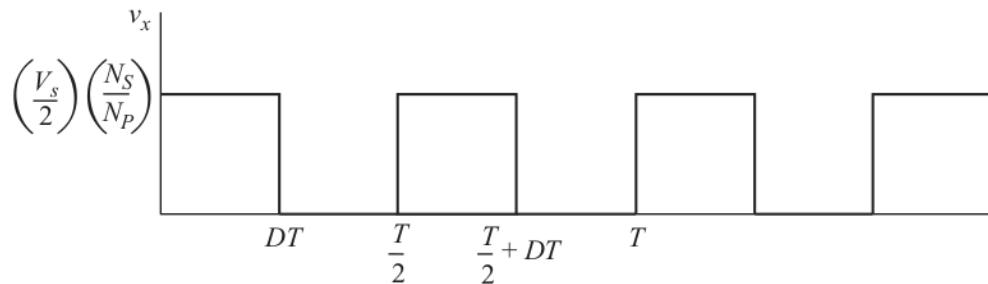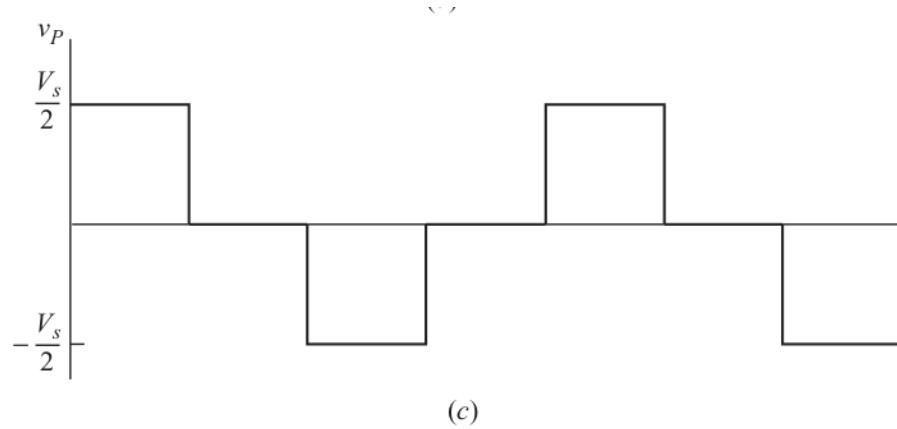

Half Bridge Converter

$$V_o = V_s \left(\frac{N_s}{N_p} \right) D$$

$$D < 0.5$$

Half of the push-pull converter

Current Source Converter


Current Source Converter

- . Voltage Source Inverter (VSI): Fed by a voltage source (i.e. a capacitor large enough)

Current Source Converter


- . Voltage Source Inverter (VSI): Fed by a voltage source (i.e. a capacitor large enough)
- . Current Source Inverter (VCI): Fed by a current source (i.e. an inductor large enough)

Current Source Converter

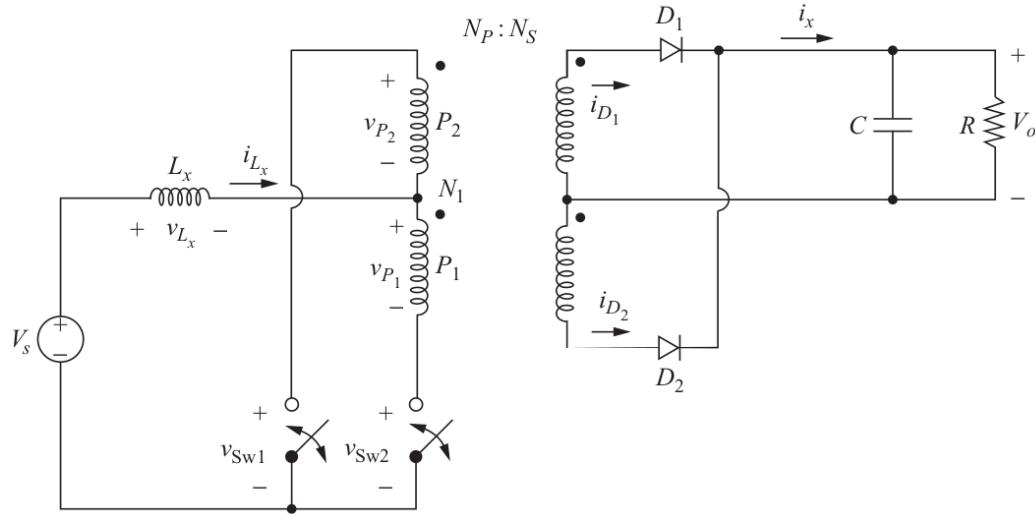

Fed with constant source current (due to large source inductance)

Current Source Converter

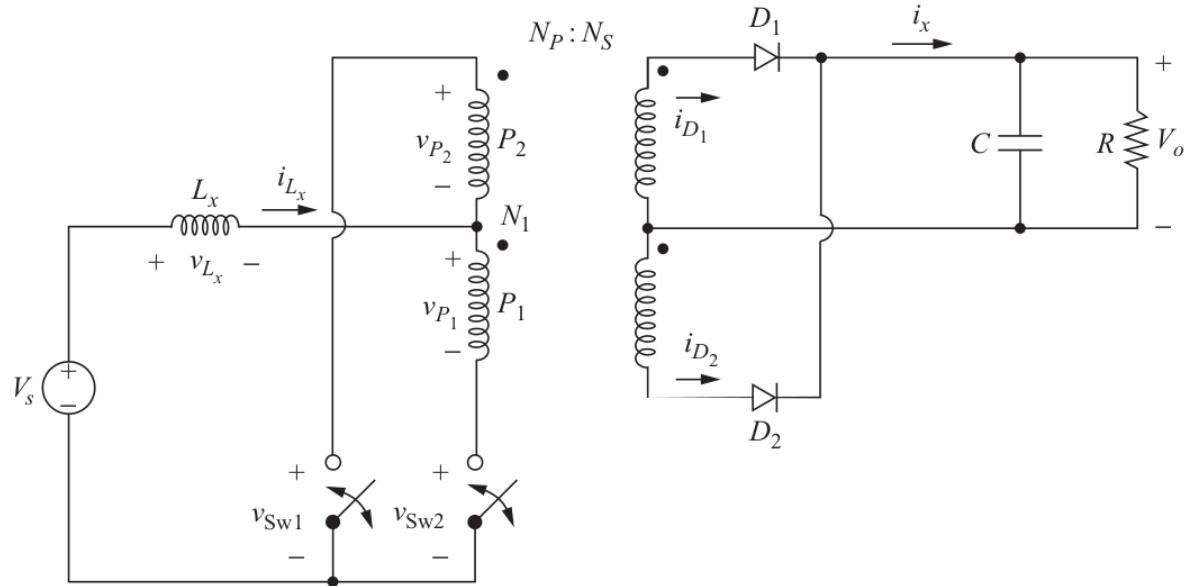

Same with push-pull, but the inductance moved to the source side

Voltage Source Converter:

Do not turn both switches ON (to prevent short-circuit)


Voltage Source Converter:

Do not turn both switches ON (to prevent short-circuit)

Current Source Converter


Do not turn both switches OFF (to prevent open-circuit)

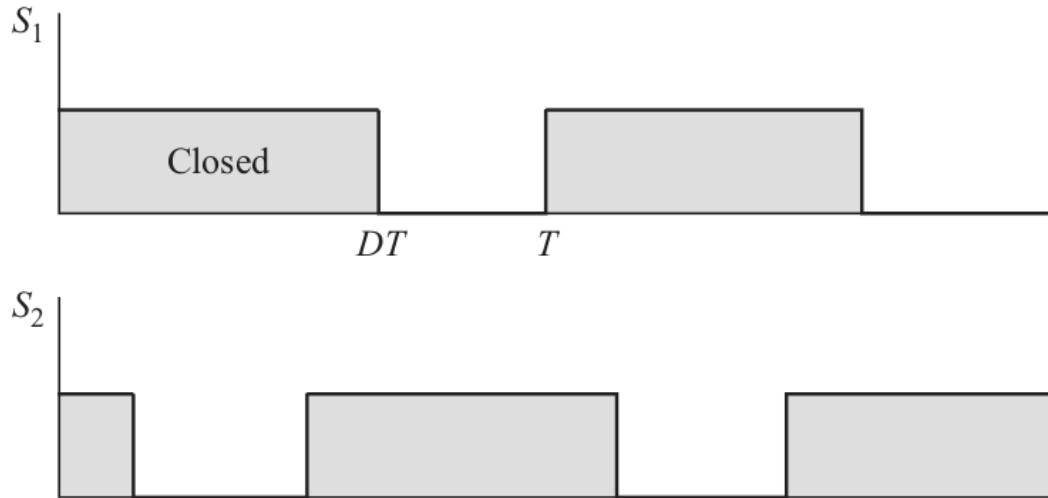Current Source Converter: Operating Modes



Notice the overlapping periods between switches

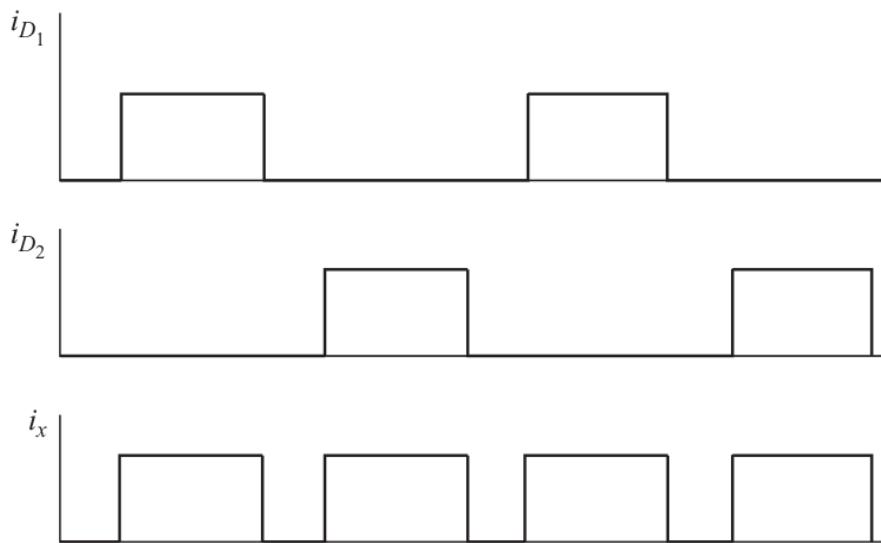Current Source Converter: Operating Modes



Diode currents are added at the output

Current Source Converter

Current Source Converter

$$V_o = V_s \left(\frac{N_s}{N_p} \right) \left(\frac{1}{2(1 - D)} \right)$$


$$D > 0.5$$

Operates as a Boost Converter

Multi-Quadrant DC Converters


First Quadrant Converter

(Type A Chopper)

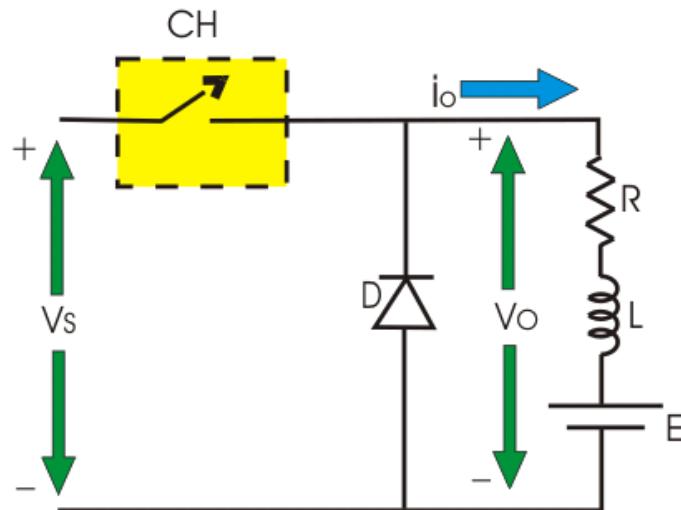


Second Quadrant Converter

(Type B Chopper)

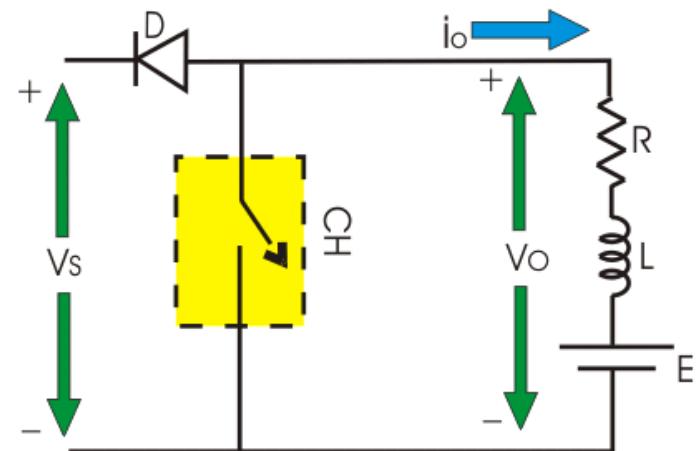


Two Quadrant Converter


(Type C Chopper)

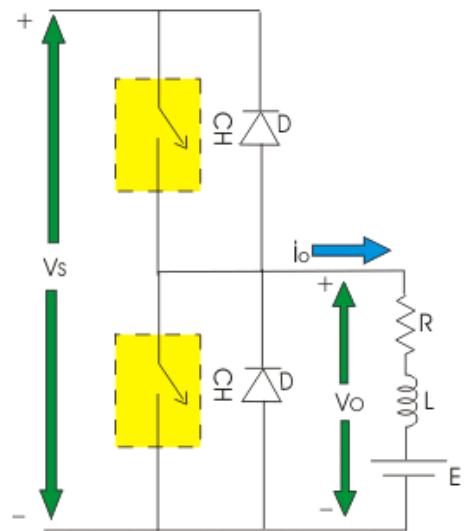

First and Fourth Quadrant Converter


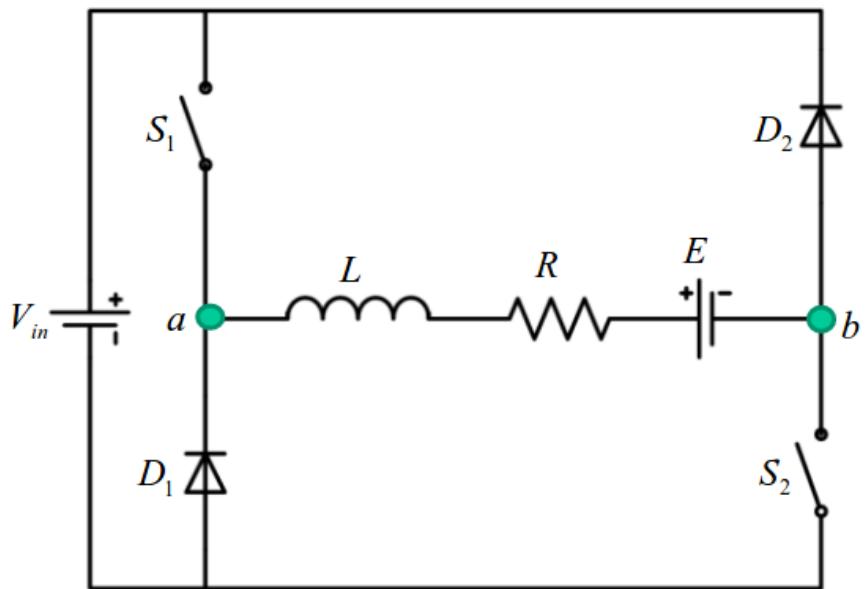


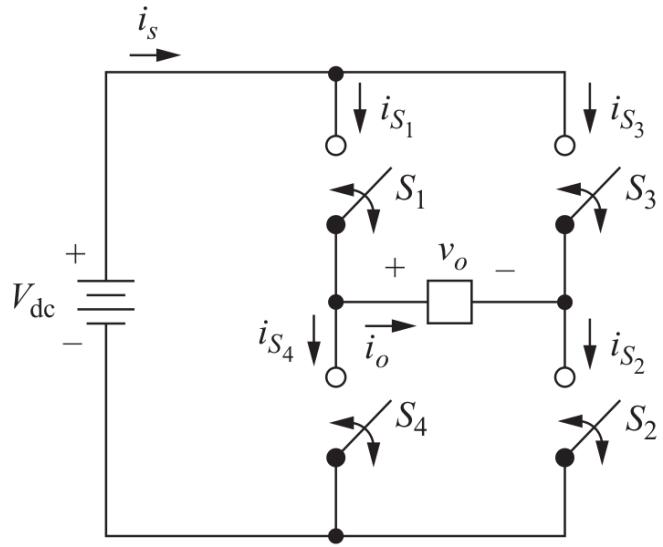Full-Bridge (Four Quadrant) DC-DC Converter



Simplified Circuit

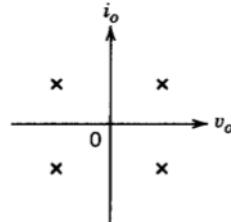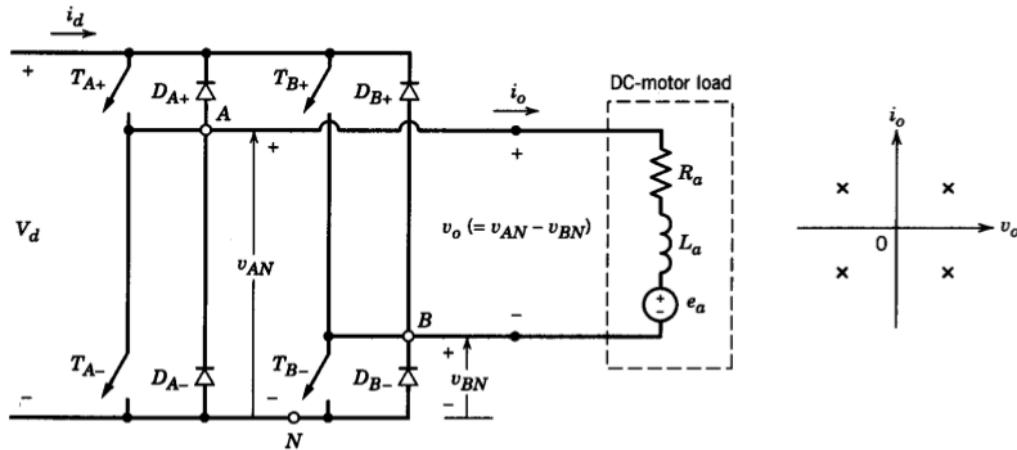Full-Bridge (Four Quadrant) DC-DC Converter



Suitable for four quadrant operation

Control of Full-Bridge Converter

- . Bi-polar Voltage Switching
- . Uni-polar Voltage Switching


Bi-polar Voltage Switching

T_{A+} and T_{B-} are turn on and off together


T_{A-} and T_{B+} are complimentary of T_{A+} and T_{B-}

Output can be $+V_d$ or $-V_d$

Bi-polar Voltage Switching

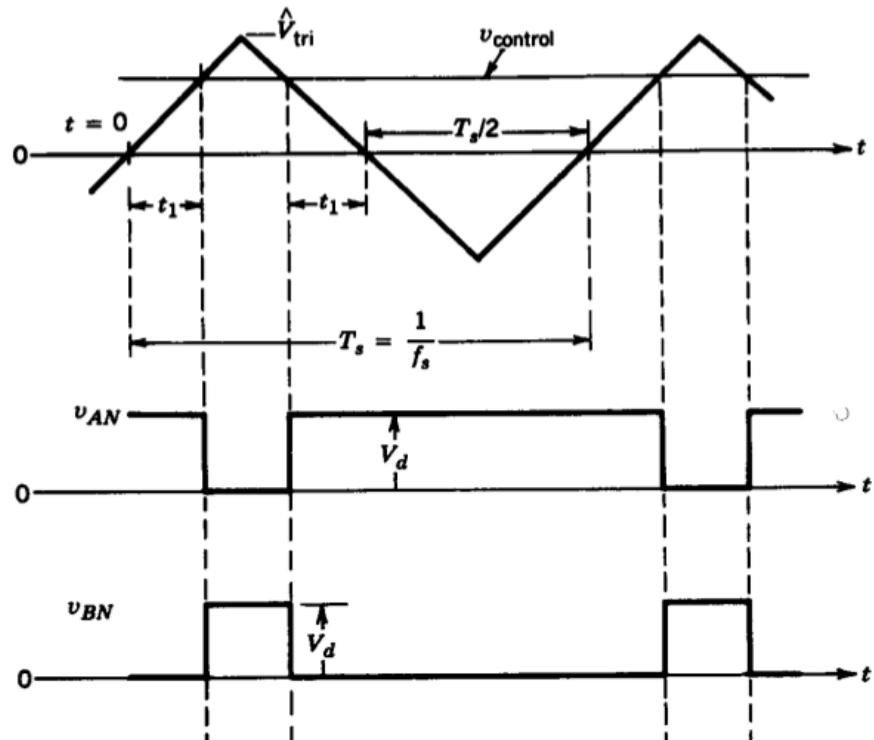

Bi-polar Voltage Switching

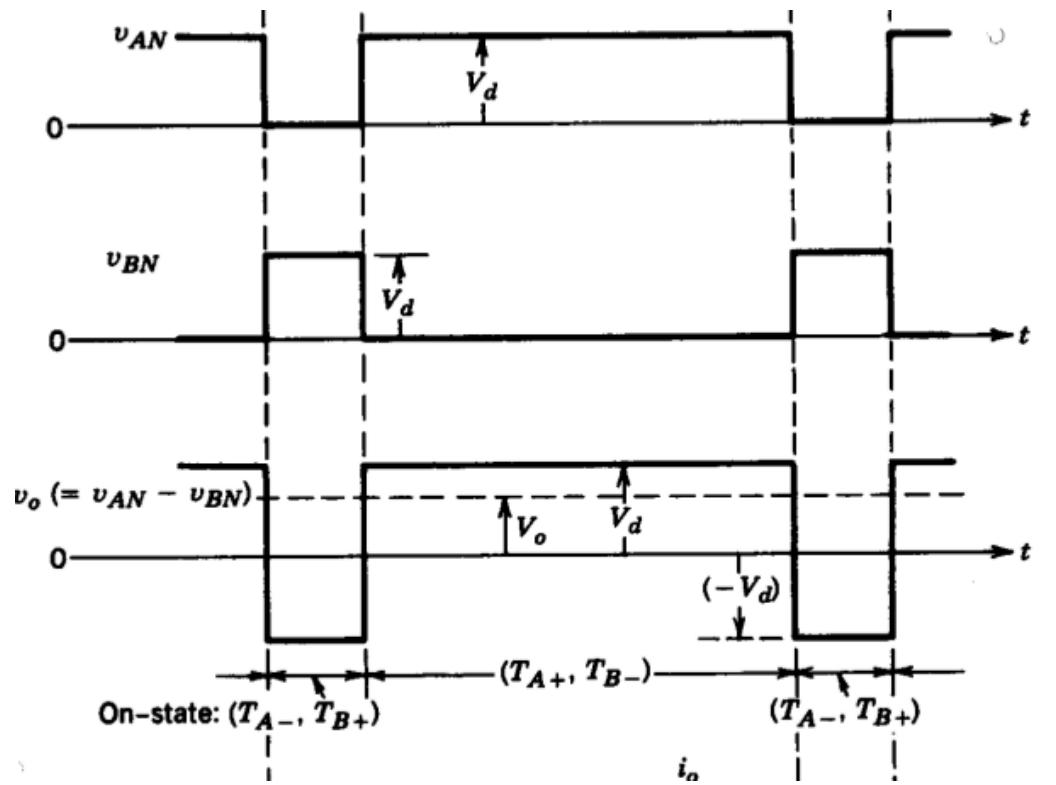

Bi-polar Voltage Switching

$$V_o = V_d \frac{v_{control}}{\hat{V}_{tri}}$$

Uni-polar Voltage Switching

T_{A+} and T_{B+} are controlled separately

T_{A-} and T_{B-} are complimentary of T_{A+} and T_{B+}

Uni-polar Voltage Switching

T_{A+} and T_{B+} are controlled separately


T_{A-} and T_{B-} are complimentary of T_{A+} and T_{B+}

Output can be $+V_d$ or 0 or $-V_d$


$V_o = 0$ if T_{A+} and T_{B+} are ON

$V_o = 0$ if T_{A-} and T_{B-} are ON

Uni-polar Voltage Switching

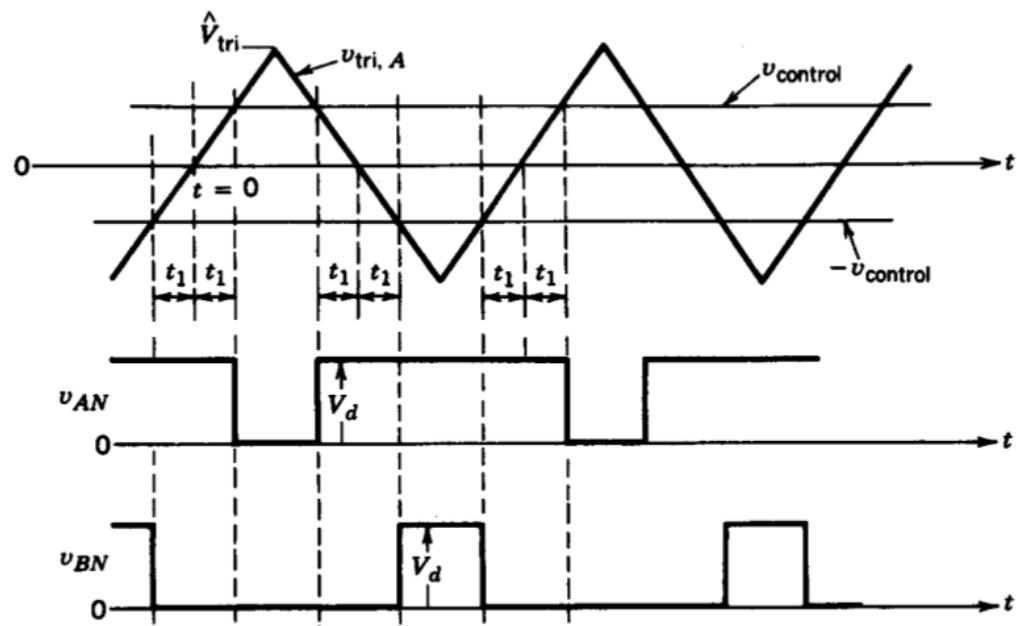

Uni-polar Voltage Switching

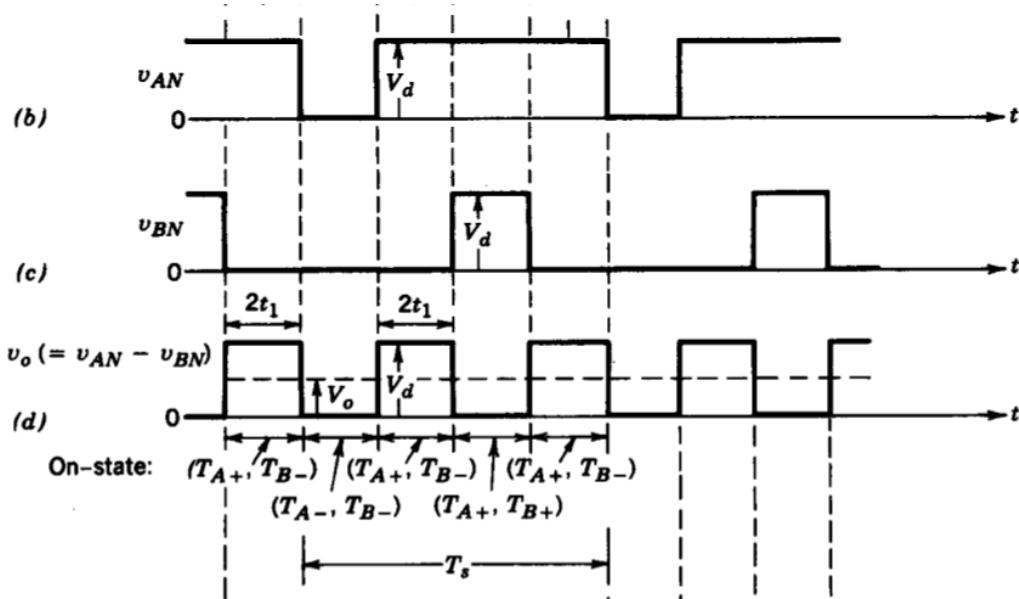

Uni-polar Voltage Switching

$$V_o = V_d \frac{v_{control}}{\hat{V}_{tri}}$$


Uni-polar Voltage Switching

$$V_o = V_d \frac{v_{control}}{\hat{V}_{tri}}$$

So, what's the point?


Ripple Comparison

Homework: Mohan Example 7.4

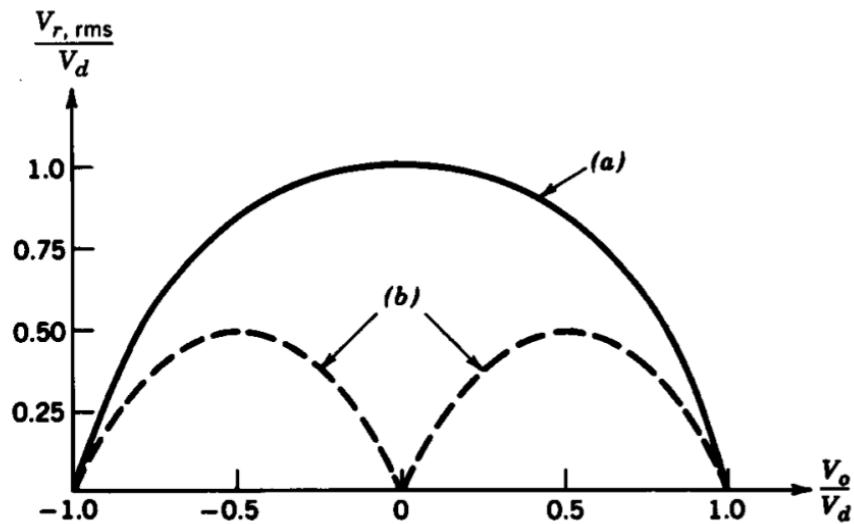

a) Bipolar PWM, b) Unipolar PWM

Dead Time (Blanking Time)

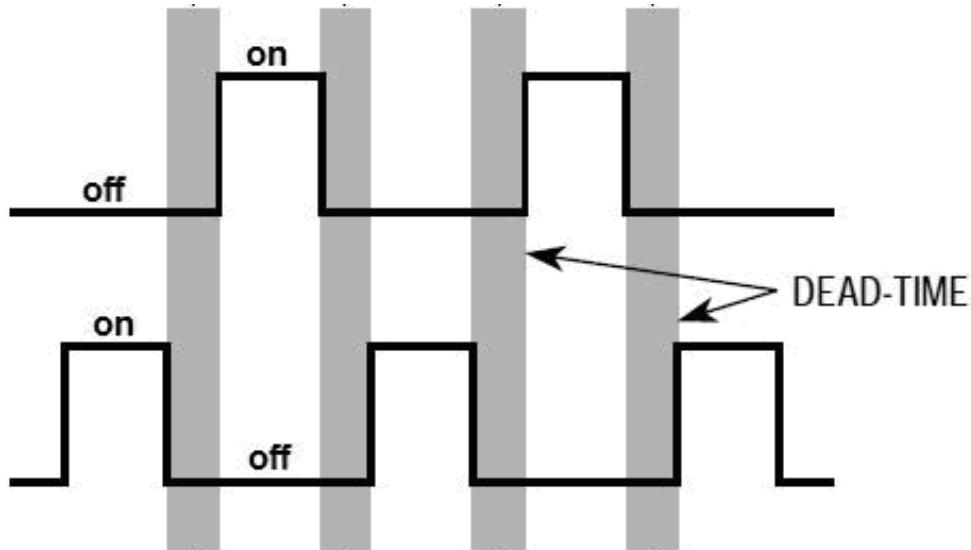

Off periods are added to compensate with non-zero turn-off time


Dead Time

Introduces non-linearity between V_{ref} and V_o .

Pulses shorter than dead-time will be omitted
(introduce harmonics)

V_{ref} can be increased to compensate for the off period.

Full Bridge as a DC Converter

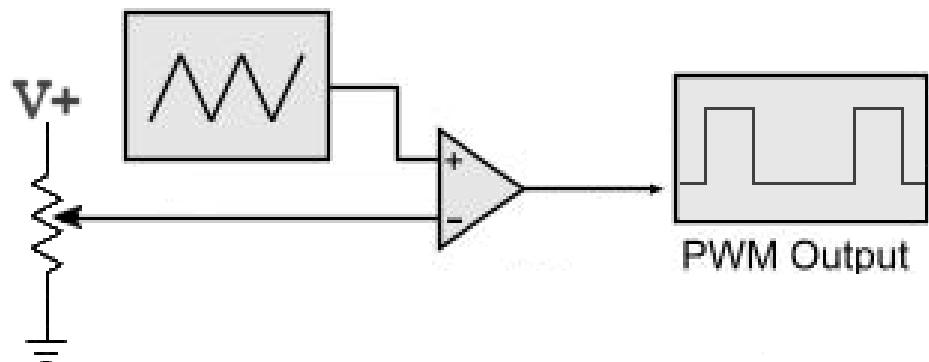


Operate it with Constant Reference Voltage


Full Bridge as an Inverter

Full Bridge as an Inverter

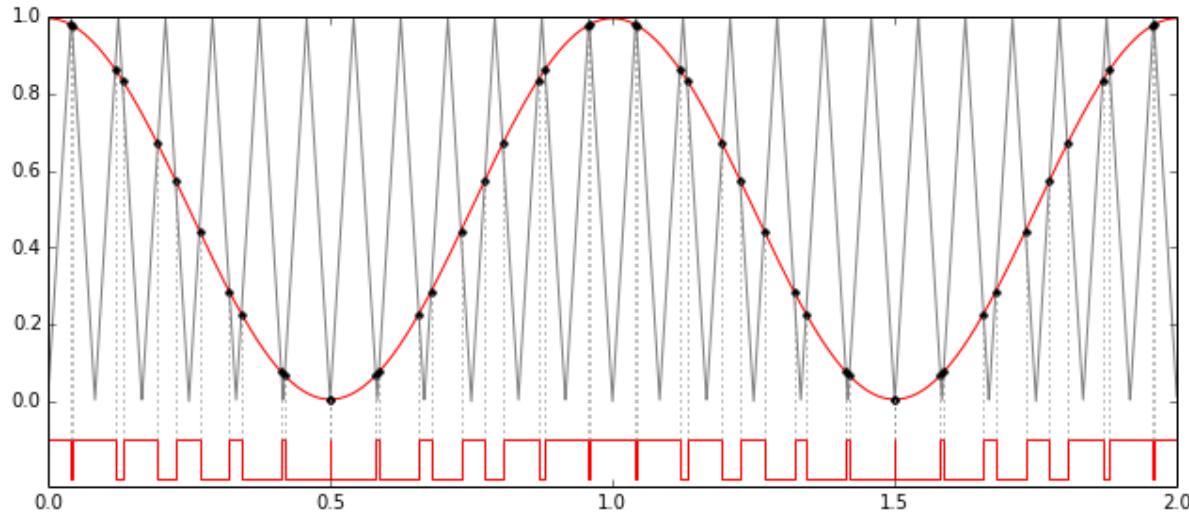Just change the reference voltage with a sinusoid



Full Bridge as an Inverter

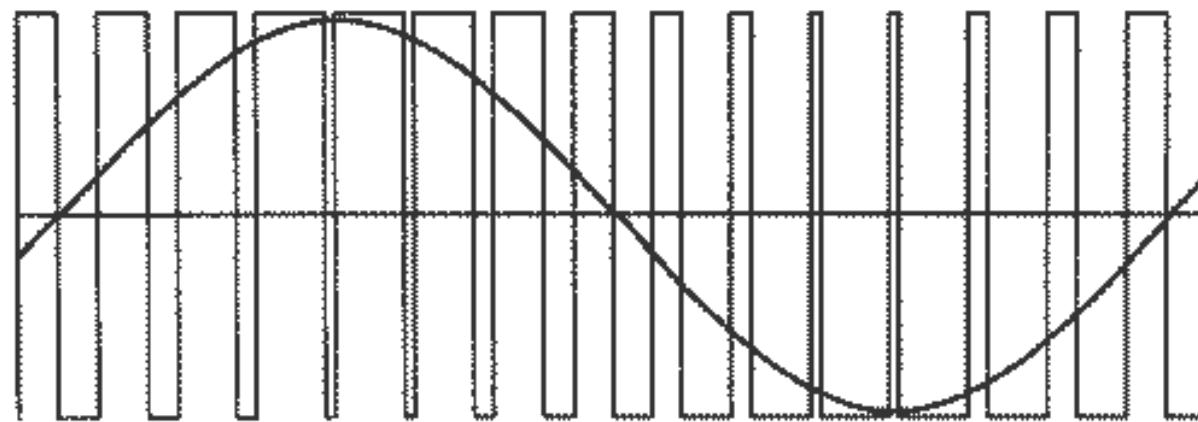

Will be covered in detail in the following weeks

PFC?

PFC?

Power Factor Correction

PFC?


Power Factor Correction

Power Factor of a 1Ph Diode Rectifier?

PFC?


Power Factor Correction

Power Factor of a 1Ph Diode Rectifier?

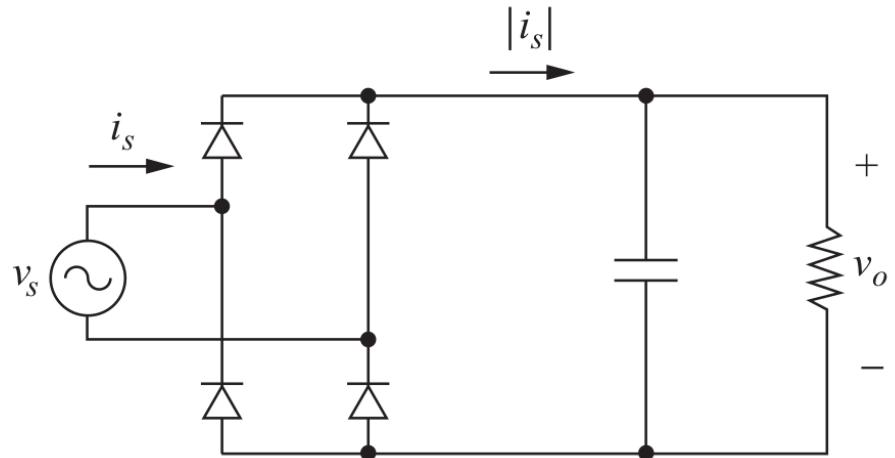

Diode Rectifier

Source current

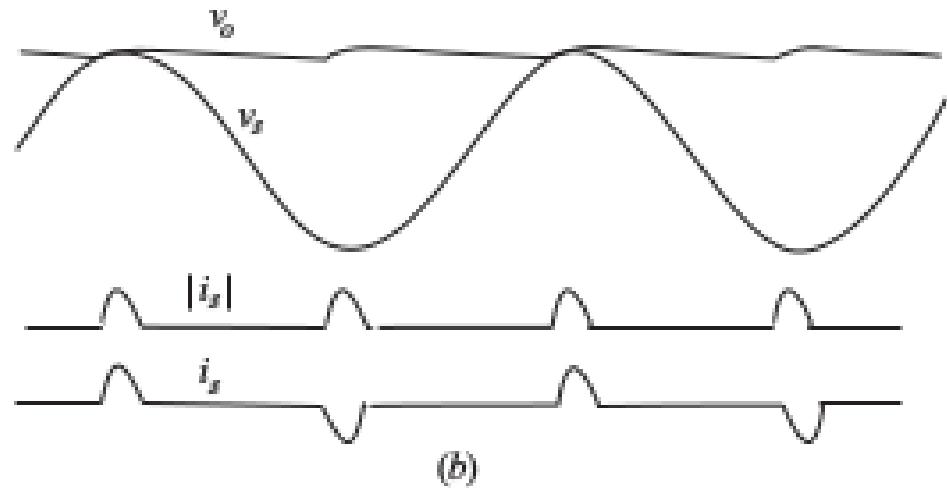

PFC required for many applications

PFC required for many applications

- Computer Power Supplies, LED Drives

PFC required for many applications

- Computer Power Supplies, LED Drives
- Arc Furnaces


PFC required for many applications

- Computer Power Supplies, LED Drives
- Arc Furnaces
- Welding

 Drawing

PFC Circuit

PFC Circuit

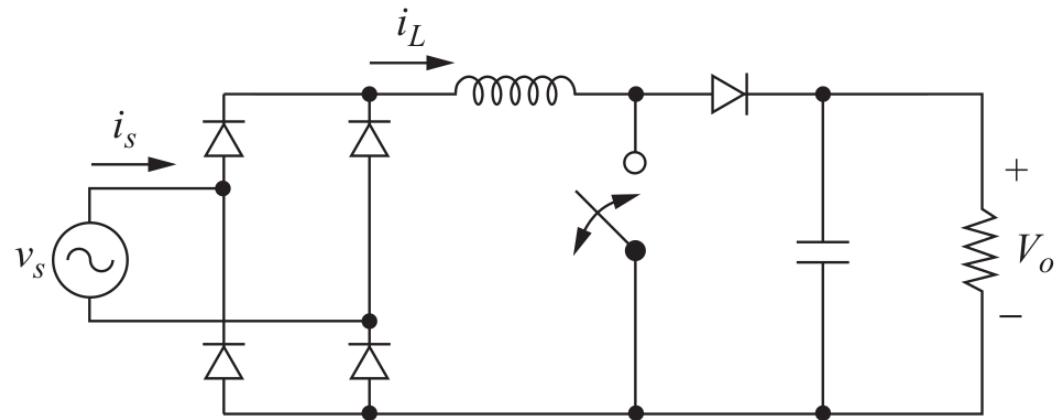


PFC Current

PFC Current



(b)

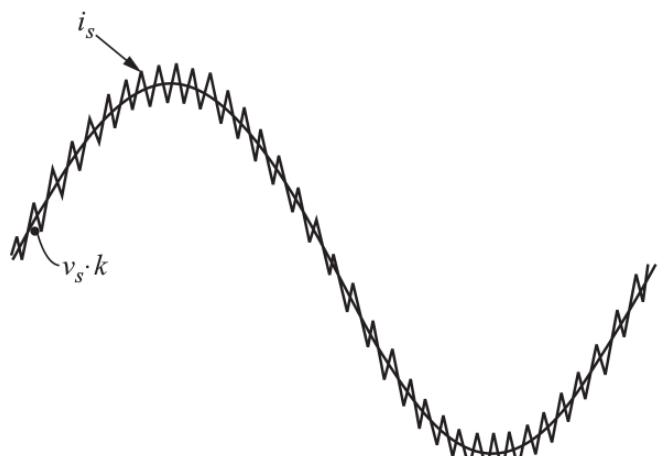


PFC Current

Critical Current Mode (Discontinuous Current Mode)


PFC Current

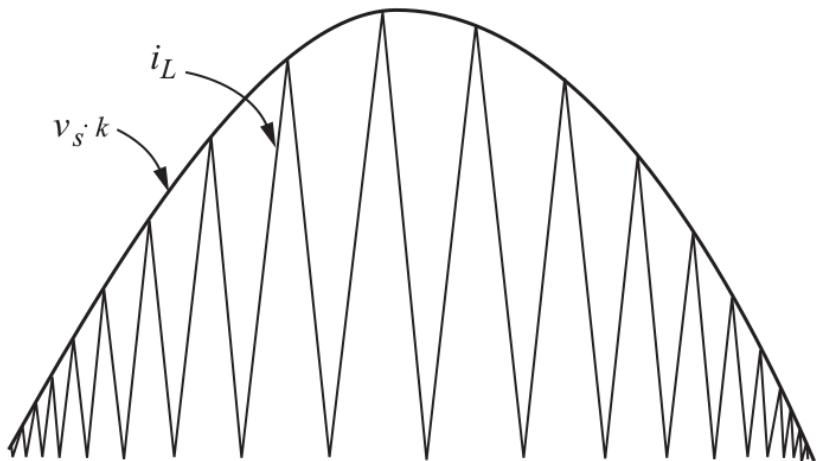Critical Current Mode (Discontinuous Current Mode)



PFC Effect

PFC Effect

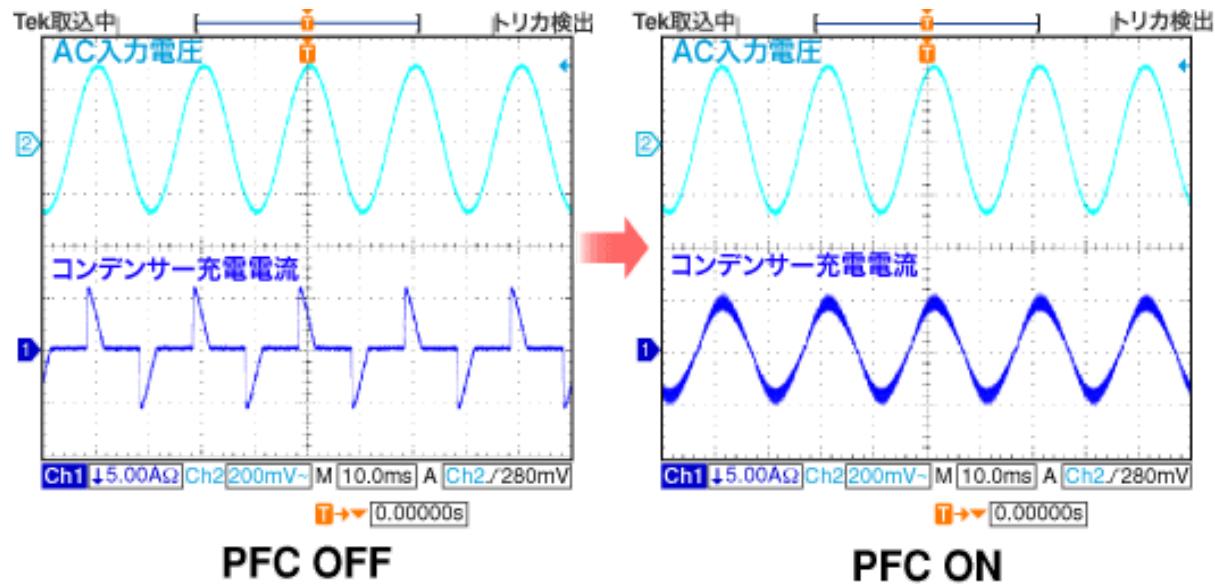


Commercial PFC Controllers

Commercial PFC Controllers

- [Toshiba-TB6819AFG](#)
- [OnSemi PFC Controllers](#)
- [TI PFC Controllers](#)
- [TI UCC28180](#)

PFC Application Study: Welding Circuit

PFC Application Study: Welding Circuit

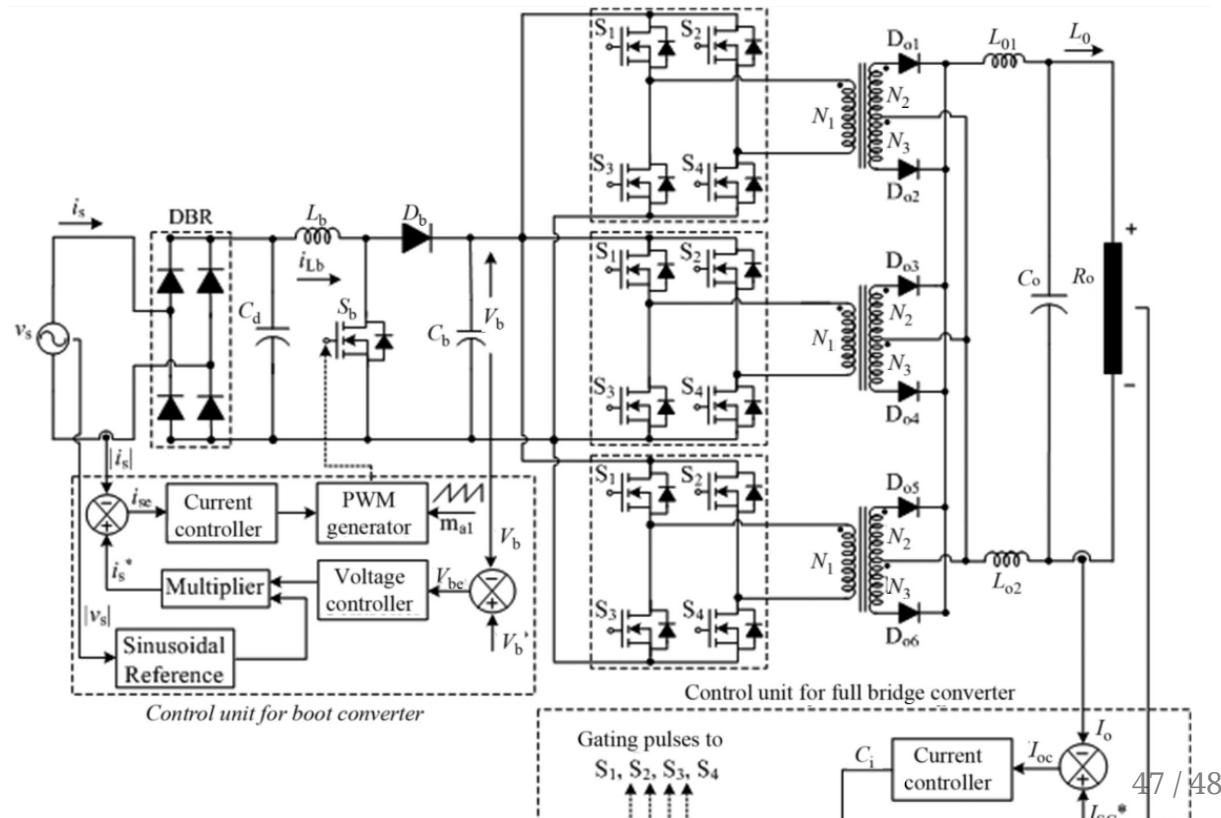

You can download this presentation from:
keysan.me/ee464