

# EE-464 STATIC POWER CONVERSION-II

## Controller Design in Power Electronics


Ozan Keysan

[keysan.me](http://keysan.me)


Office: C-113 • Tel: 210 7586

# Control in Power Electronics

## Control of a Wind Turbine

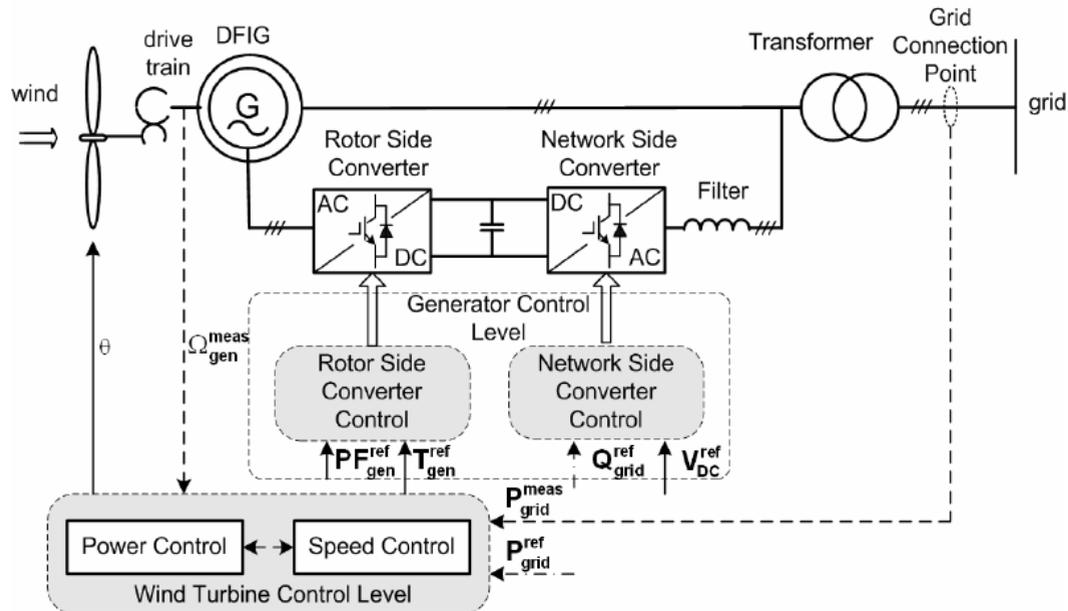

# Detailed Control of a Wind Turbine

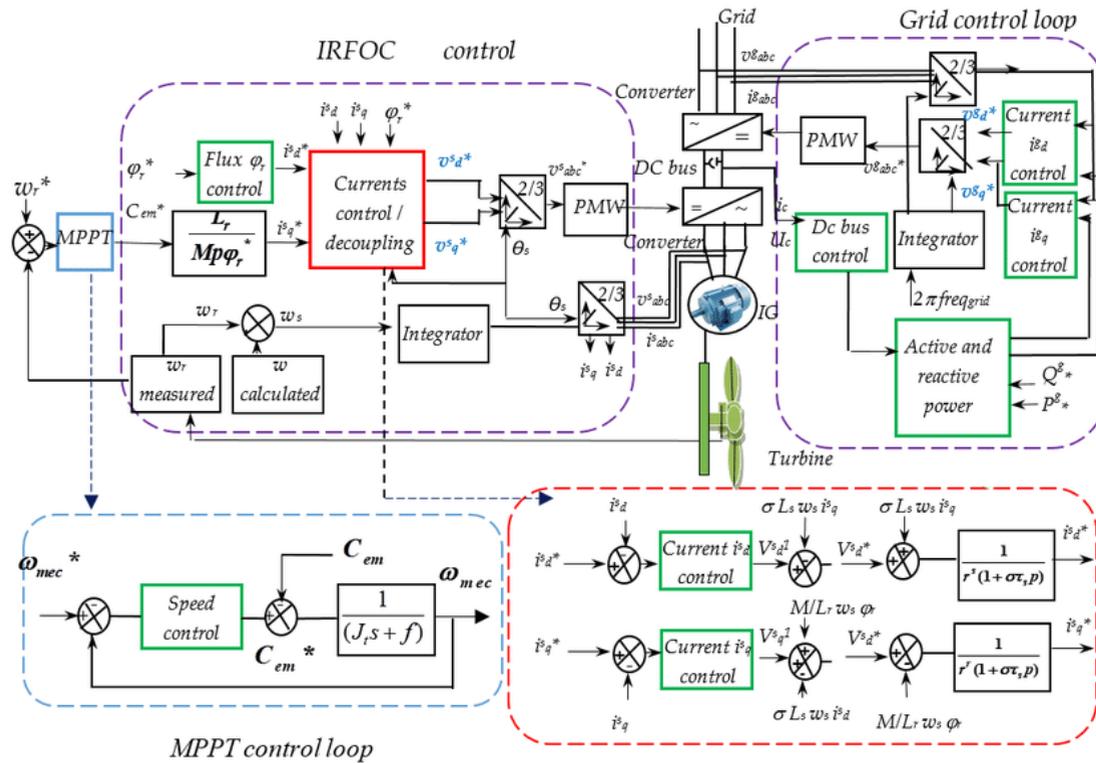


# Control in Power Electronics

Most DC/DC converters controlled by analog controllers:


- Micro-controllers are not fast enough (both for computing and sampling) at high switching frequencies
- Cheap (just an IC and a few passive elements)
- Could be integrated to with drive circuit ([LM1771](#))

# Control in Power Electronics

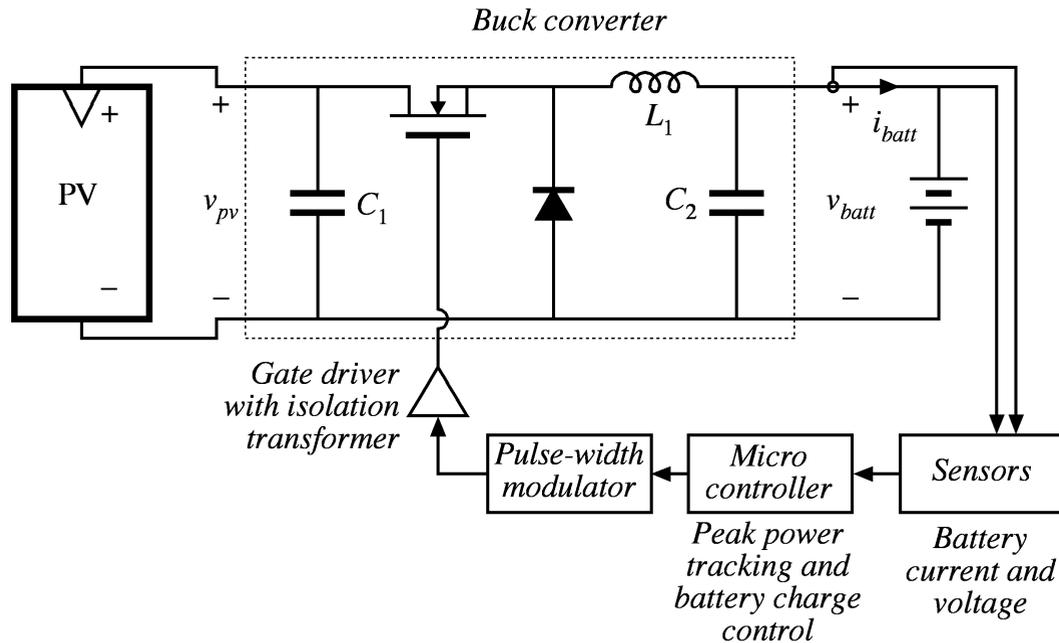


## Control with a microcontroller

# Control in Power Electronics

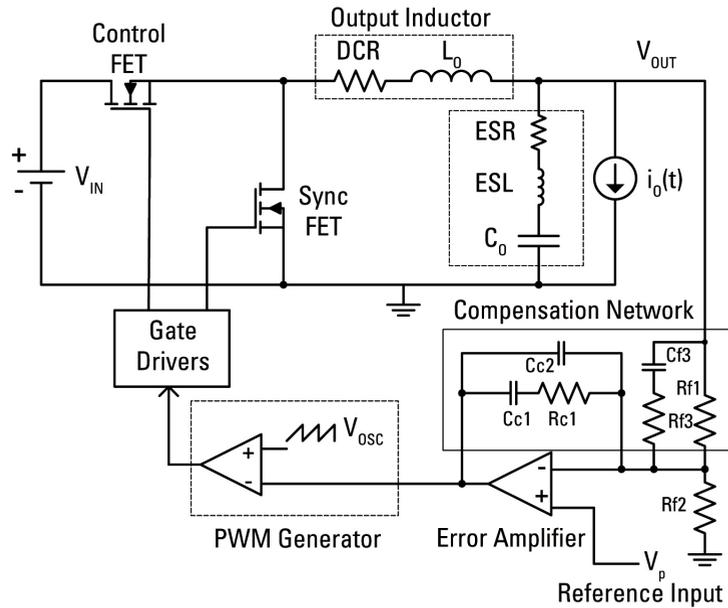


## Control with an error amplifier

# Buck Converter Controller

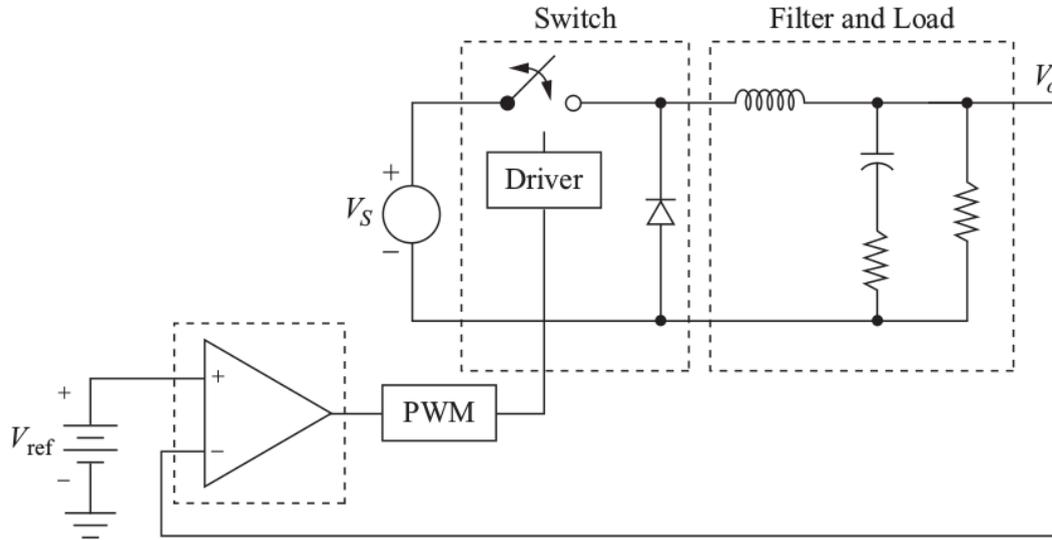

# Buck Converter Controller

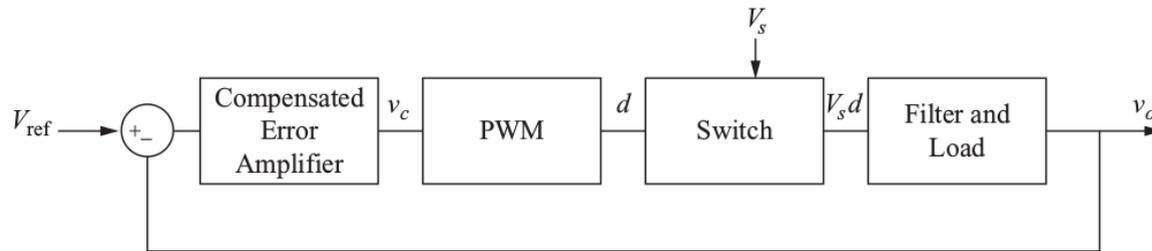

# Control Loop Stability


- Small steady-state error (i.e. gain at low frequencies should be large)
- No resonance: (i.e. gain at switching frequency should be small)
- Enough phase-margin: ( usually at least 45 degree phase margin is aimed for stability)

# Phase Margin



Difference to -180 degrees when the gain is unity  
(0dB)

# Phase Margin

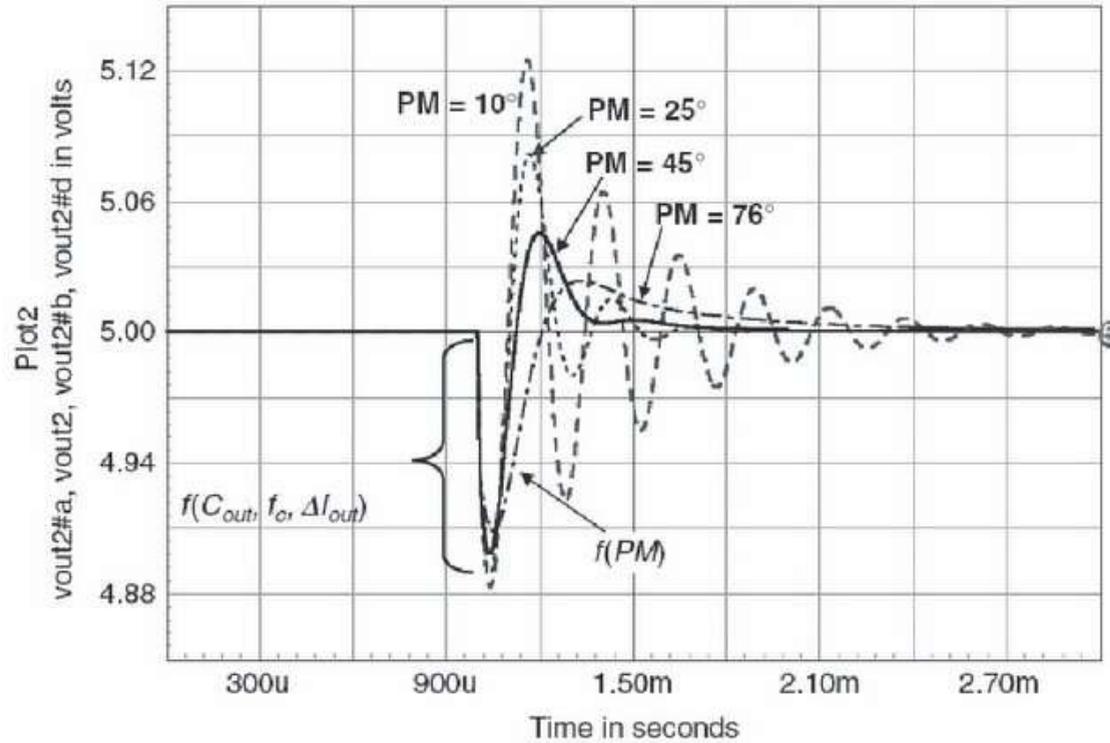


# Small Signal Analysis

Don't worry, will be revisited!


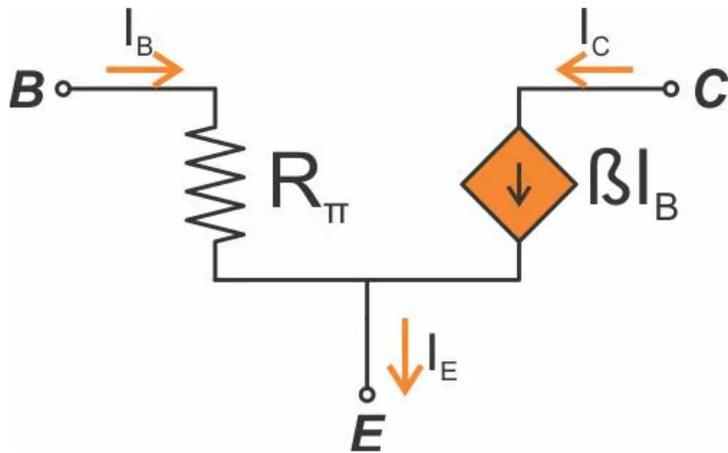
# Small Signal Analysis

Don't worry, will be revisited!

Small Signal Model of a Transistor (EE311)


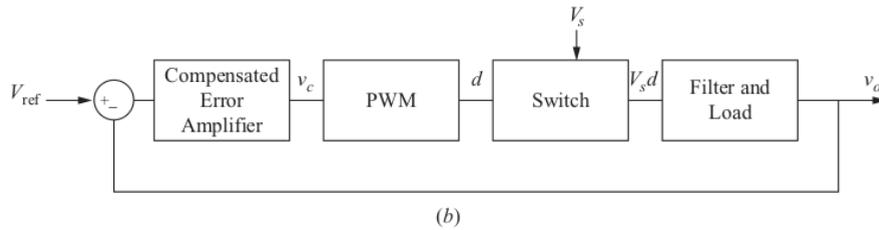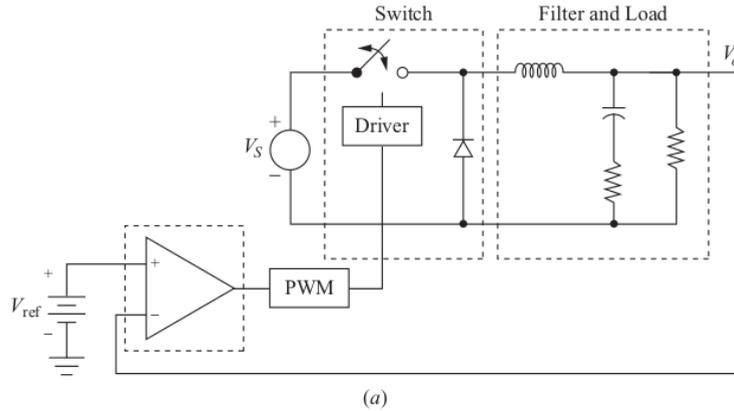
# Small Signal Analysis for the Buck Converter



# Small Signal Analysis

# Small Signal Analysis

For a parameter,  $x$ :

# Small Signal Analysis

For a parameter,  $x$ :

- $x$ : total quantity

# Small Signal Analysis

For a parameter,  $x$ :

- $x$ : total quantity
- $X$ : steady-state (DC) component

# Small Signal Analysis

For a parameter,  $x$ :

- $x$ : total quantity
- $X$ : steady-state (DC) component
- $\tilde{x}$ : AC term (small-signal variation)

# Small Signal Analysis

For a parameter,  $x$ :

- $x$ : total quantity
- $X$ : steady-state (DC) component
- $\tilde{x}$ : AC term (small-signal variation)

$$x = X + \tilde{x}$$

# Small Signal Analysis

# Small Signal Analysis

For the buck converter

$$v_o = V_o + \tilde{v}_o$$



$$d = D + \tilde{d}$$

$$i_L = I_L + \tilde{i}_L$$

$$v_s = V_s + \tilde{v}_s$$

# Small Signal Analysis

## Average Model of the buck converter

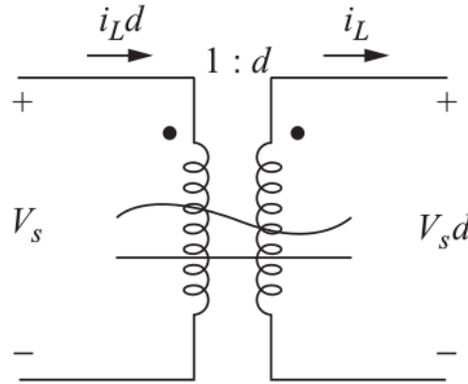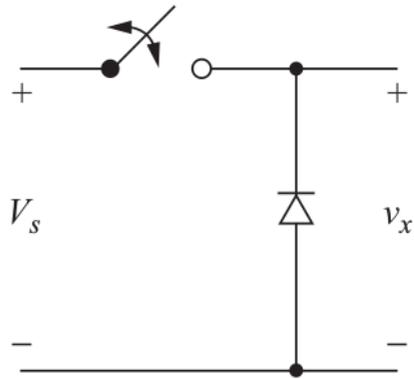

# Small Signal Analysis for the Buck Converter

Let's derive the small signal model for voltage

# Small Signal Analysis for the Buck Converter

Let's derive the small signal model for voltage

$$v_x = v_s d$$

# Small Signal Analysis for the Buck Converter

Let's derive the small signal model for voltage

$$v_x = v_s d = (V_s + \tilde{v}_s)(D + \tilde{d})$$

# Small Signal Analysis for the Buck Converter

Let's derive the small signal model for voltage

$$v_x = v_s d = (V_s + \tilde{v}_s)(D + \tilde{d})$$

$$v_x = V_s D + \tilde{v}_s D + V_s \tilde{d} + \tilde{v}_s \tilde{d}$$

# Small Signal Analysis for the Buck Converter

Let's derive the small signal model for voltage

$$v_x = v_s d = (V_s + \tilde{v}_s)(D + \tilde{d})$$

$$v_x = V_s D + \tilde{v}_s D + V_s \tilde{d} + \tilde{v}_s \tilde{d}$$

ignoring the last term

# Small Signal Analysis for the Buck Converter

Let's derive the small signal model for voltage

$$v_x = v_s d = (V_s + \tilde{v}_s)(D + \tilde{d})$$

$$v_x = V_s D + \tilde{v}_s D + V_s \tilde{d} + \tilde{v}_s \tilde{d}$$

ignoring the last term

$$v_x \approx V_s D + \tilde{v}_s D + V_s \tilde{d} = v_s D + V_s \tilde{d}$$

# Small Signal Analysis for the Buck Converter

Let's repeat for current

$$i_s = i_L d = (I_L + \tilde{i}_L)(D + \tilde{d})$$

$$\approx i_L D + I_L \tilde{d}$$


# Exercise Assignment:

Power Electronics, Hart, Section 7.13

Buck Converter Small Signal Model

# Transfer Functions


## RC Filter

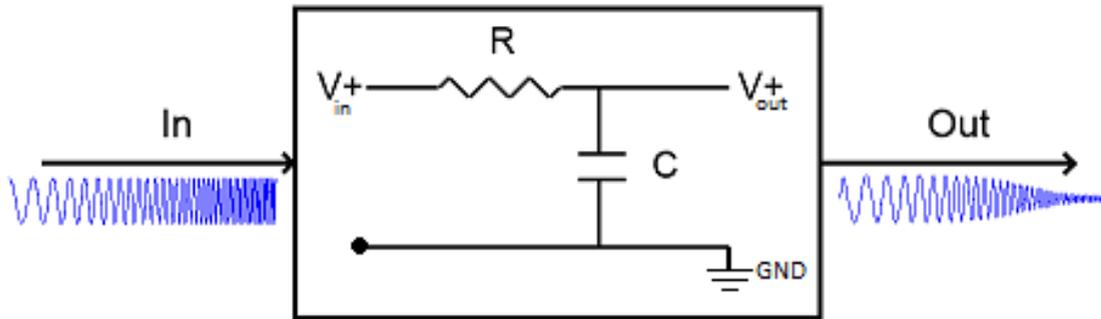

Transfer Function: 
$$T(j\omega) = \frac{\text{Out}}{\text{In}} = \frac{1}{1 + j\omega CR}$$


# Transfer Functions

## RC Filter [Bode Plot](#)

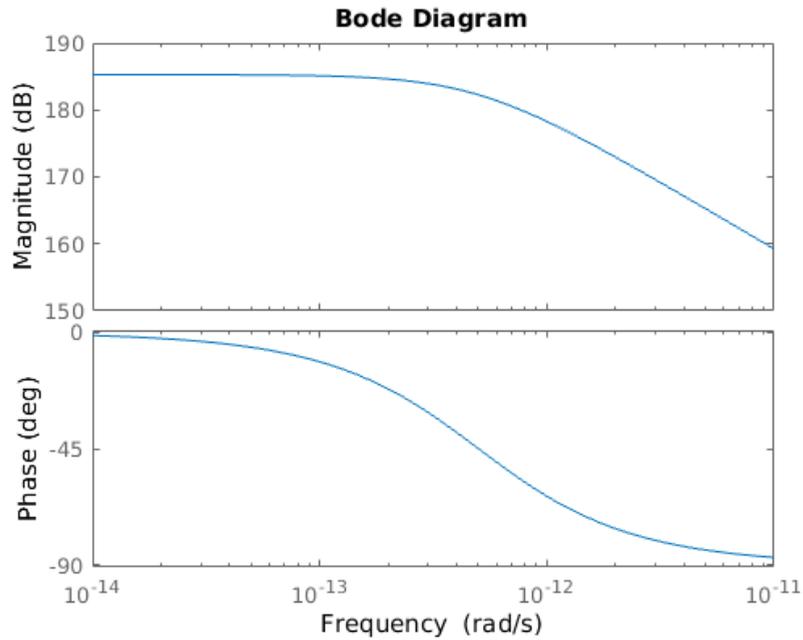
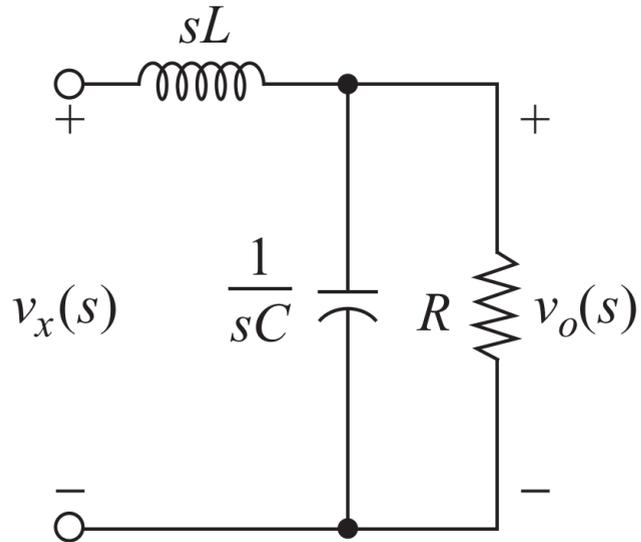
# Transfer Functions

Let's do for the LCR part of the converter



Representation in the s-domain

# Transfer Functions

Let's do for the LCR part of the converter

$$\frac{v_o(s)}{v_x(s)} = \frac{1}{LC(s^2 + (1/RC)s + 1/LC)}$$

$$v_x(s) = V_s d(s)$$

Transfer function in terms of  $d(s)$


$$\frac{v_o(s)}{d(s)} = \frac{V_s}{LC(s^2 + (1/RC)s + 1/LC)}$$

# Realistic RLC

Non-ideal elements can effect stability

- . Resistance of the inductor
- . ESR of capacitor (series resistance)

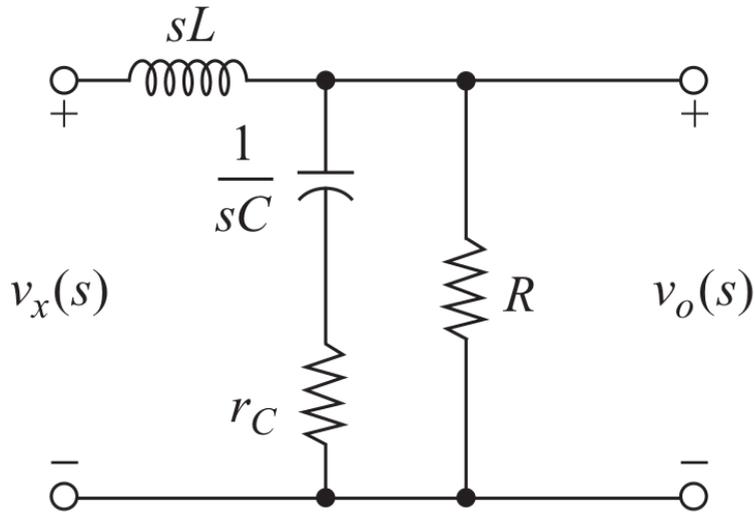Let's repeat the case with non-ideal capacitor



Capacitor with series resistance

Let's repeat the case with non-ideal capacitor

$$\frac{v_o(s)}{d(s)} = \frac{V_s}{LC} \frac{1 + sr_C R}{s^2(1 + r_C/R) + s(1/RC + r_C/L) + 1/LC}$$

Let's repeat the case with non-ideal capacitor

$$\frac{v_o(s)}{d(s)} = \frac{V_s}{LC} \frac{1 + sr_C R}{s^2(1 + r_C/R) + s(1/RC + r_C/L) + 1/LC}$$

Can be simplified by assuming  $r_C \ll R$

$$\frac{V_s}{LC} \frac{1 + sr_C R}{s^2 + s(1/RC + r_C/L) + 1/LC}$$

Notice the extra zero introduced by ESR!

# PWM Block Transfer Function

## PWM Block Transfer Function

$$d = \frac{v_c}{V_p}$$

for a saw-tooth PWM generator with  $V_p$  peak voltage

## PWM Block Transfer Function

$$d = \frac{v_c}{V_p}$$

for a saw-tooth PWM generator with  $V_p$  peak voltage

Transfer function


$$\frac{d(s)}{v_c(s)} = \frac{1}{V_p}$$

# PWM Block Transfer Function

Be careful with high-frequency control bandwidth
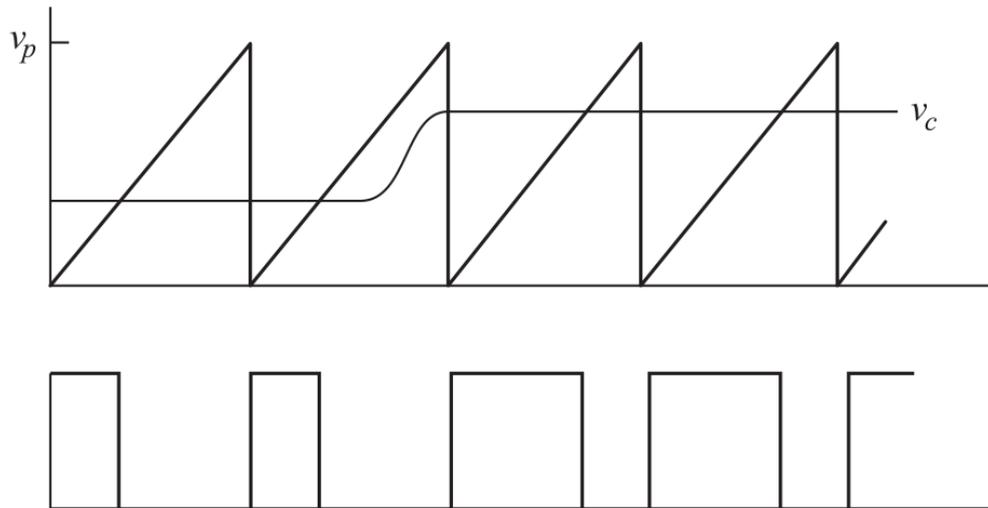
# PWM Block Transfer Function

Be careful with high-frequency control bandwidth



What about in switching components?

# What about in switching components?

Problem:

# What about in switching components?

## Problem:

- Multi-mode systems (topology changes with switching)

# What about in switching components?

## Problem:

- . Multi-mode systems (topology changes with switching)
- . Different transfer function for on-off states

# What about in switching components?

## Problem:

- . Multi-mode systems (topology changes with switching)
- . Different transfer function for on-off states
- . Can use non-linear controller, or multiple linear controllers (but difficult to implement)

What about in switching components?

What about in switching components?

Solution:

# What about in switching components?

Solution:

- Convert multi-mode to single-mode system

# What about in switching components?

Solution:

- Convert multi-mode to single-mode system
- Linearizing the system with averaging wrt duty cycle

# What about in switching components?

Solution:

- Convert multi-mode to single-mode system
- Linearizing the system with averaging wrt duty cycle
- Use a linear controller with required characteristics

# What about in switching components?

Solution:

- Convert multi-mode to single-mode system
- Linearizing the system with averaging wrt duty cycle
- Use a linear controller with required characteristics


Details in the textbook (Mohan)

# Case Study (Mohan 10-1)

Find the transfer function of forward converter
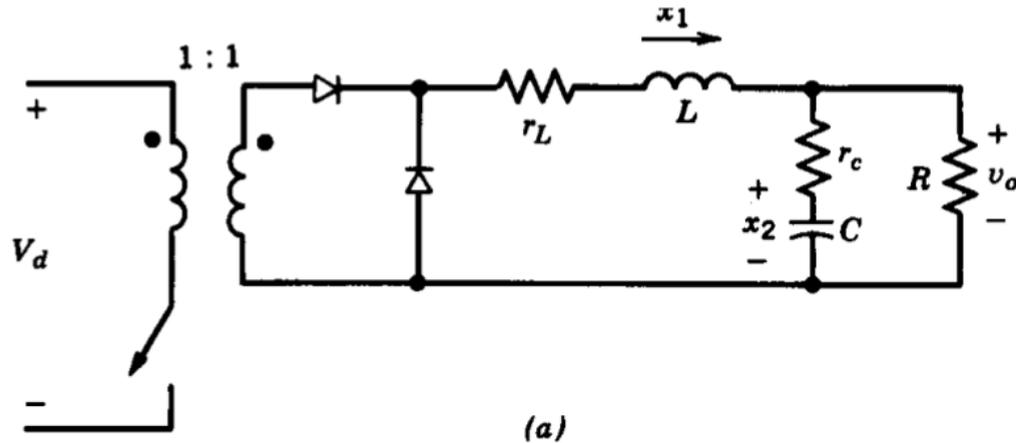
# Case Study (Mohan 10-1)


Find the transfer function of forward converter



Note the state variables


# Case Study (Mohan 10-1)

Switch ON

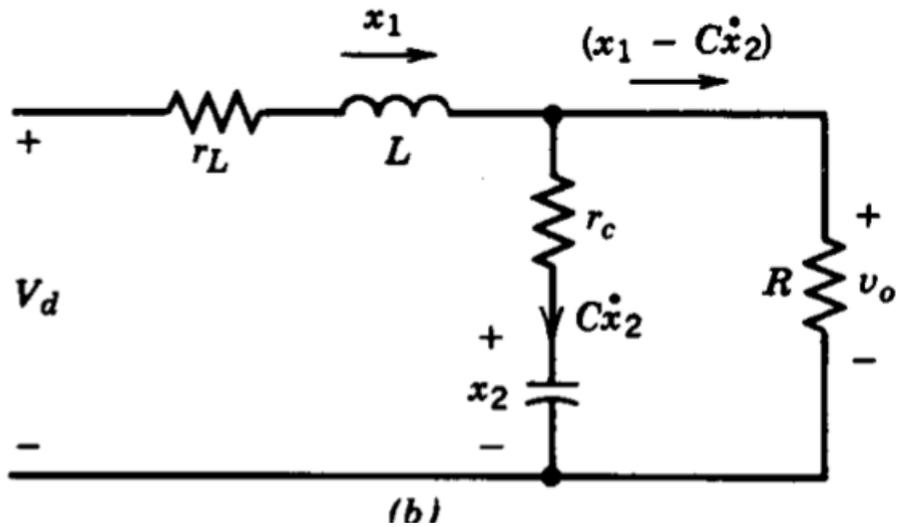

# Case Study (Mohan 10-1)

Switch OFF

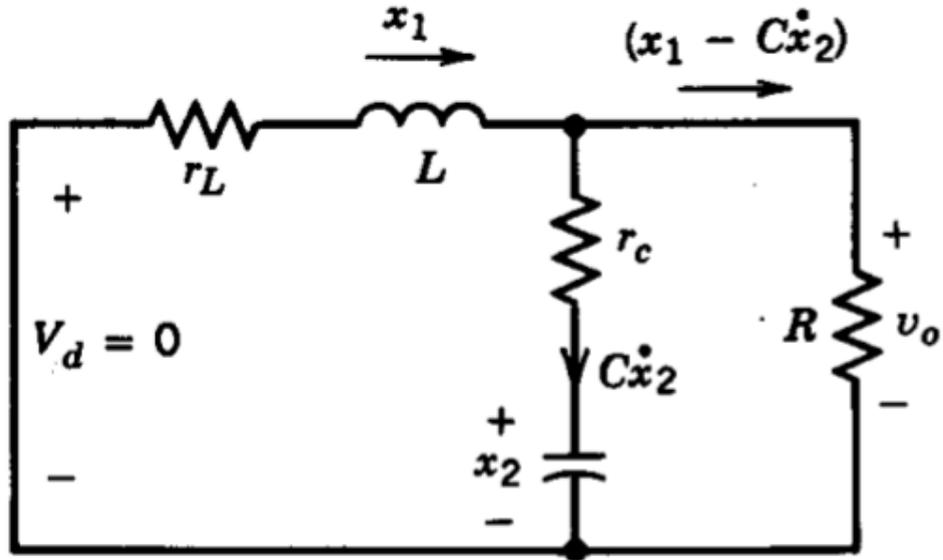

# Case Study (Mohan 10-1)

## Steady State Transfer Function

# Case Study (Mohan 10-1)

## Steady State Transfer Function

$$\frac{V_o}{V_d} = -CA^{-1}B$$

# Case Study (Mohan 10-1)

## Steady State Transfer Function

$$\frac{V_o}{V_d} = -CA^{-1}B$$

$$\frac{V_o}{V_d} = D \frac{R + r_C}{R + (r_C + r_L)}$$

# Case Study (Mohan 10-1)

## Steady State Transfer Function

$$\frac{V_o}{V_d} = -CA^{-1}B$$

$$\frac{V_o}{V_d} = D \frac{R + r_C}{R + (r_C + r_L)}$$

If parasitic resistances are small

# Case Study (Mohan 10-1)

## Steady State Transfer Function

$$\frac{V_o}{V_d} = -CA^{-1}B$$

$$\frac{V_o}{V_d} = D \frac{R + r_C}{R + (r_C + r_L)}$$

If parasitic resistances are small

$$\frac{V_o}{V_d} \approx D$$

# Case Study (Mohan 10-1)

## AC Transfer Function

# Case Study (Mohan 10-1)

## AC Transfer Function

$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$

# Case Study (Mohan 10-1)

## AC Transfer Function

$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$
$$= V_d \frac{1 + sr_C C}{LC[s^2 + s(1/RC + (r_C + r_L)/L) + 1/LC]}$$

# Case Study (Mohan 10-1)

AC Transfer Function

$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$
$$= V_d \frac{1 + sr_C C}{LC[s^2 + s(1/RC + (r_C + r_L)/L) + 1/LC]}$$

Remember this equation?

# Case Study (Mohan 10-1)

## AC Transfer Function

$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$
$$= V_d \frac{1 + sr_C C}{LC[s^2 + s(1/RC + (r_C + r_L)/L) + 1/LC]}$$

Remember this equation?

$$s^2 + 2\xi\omega_0 s + \omega_0^2$$

# Case Study (Mohan 10-1)

AC Transfer Function

$$s^2 + 2\xi\omega_0 s + \omega_0^2$$

# Case Study (Mohan 10-1)

## AC Transfer Function

$$s^2 + 2\xi\omega_0 s + \omega_0^2$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

# Case Study (Mohan 10-1)

## AC Transfer Function

$$s^2 + 2\xi\omega_0 s + \omega_0^2$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\xi = \frac{1/RC + (r_C + r_L)/L}{2\omega_0}$$

# Case Study (Mohan 10-1)

AC Transfer Function Becomes

$$T_p(s) = V_d \frac{\omega_0^2}{\omega_z} \frac{s + \omega_z}{s^2 + 2\xi\omega_0 s + \omega_0^2}$$

$$\text{where } \omega_z = \frac{1}{r_C C}$$

# Example (Mohan 10-1)

Put the parameters into the equation

$$V_d = 8V$$

$$V_o = 5V$$

$$r_L = 20m\Omega$$

$$L = 5\mu H$$

$$r_C = 10m\Omega$$


$$C = 2mF$$

$$R = 200m\Omega$$

$$f_s = 200kHz$$


# Example (Mohan 10-1)

## Bode Plot (Gain)

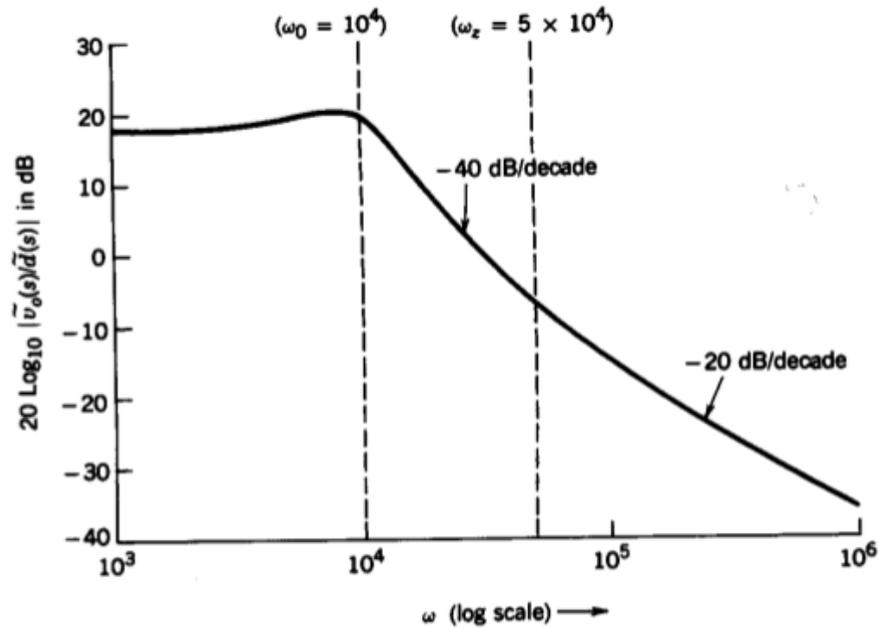

# Example (Mohan 10-1)

## Bode Plot (Phase)

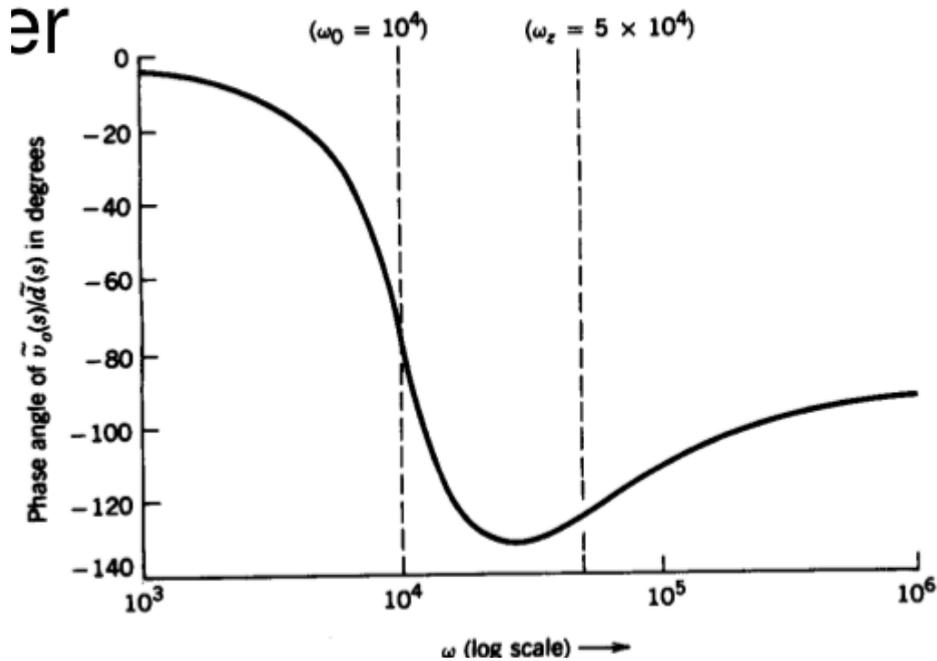

# Flyback Converter

# Flyback Converter

Equation 10-86

$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$

# Flyback Converter

Equation 10-86


$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$

$$T_p(s) = V_d f(D) \frac{(1 + s/\omega_{z1})(1 - s/\omega_{z2})}{as^2 + bs + c}$$

# Flyback Converter

# Flyback Converter


## Bode Plot (Gain)

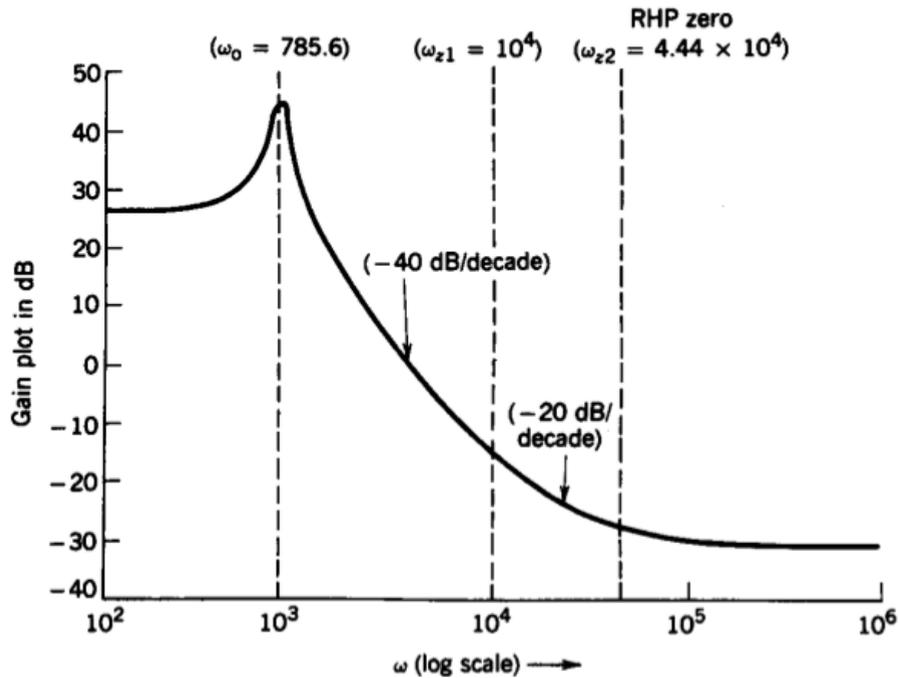

# Flyback Converter

# Flyback Converter

## Bode Plot (Phase)

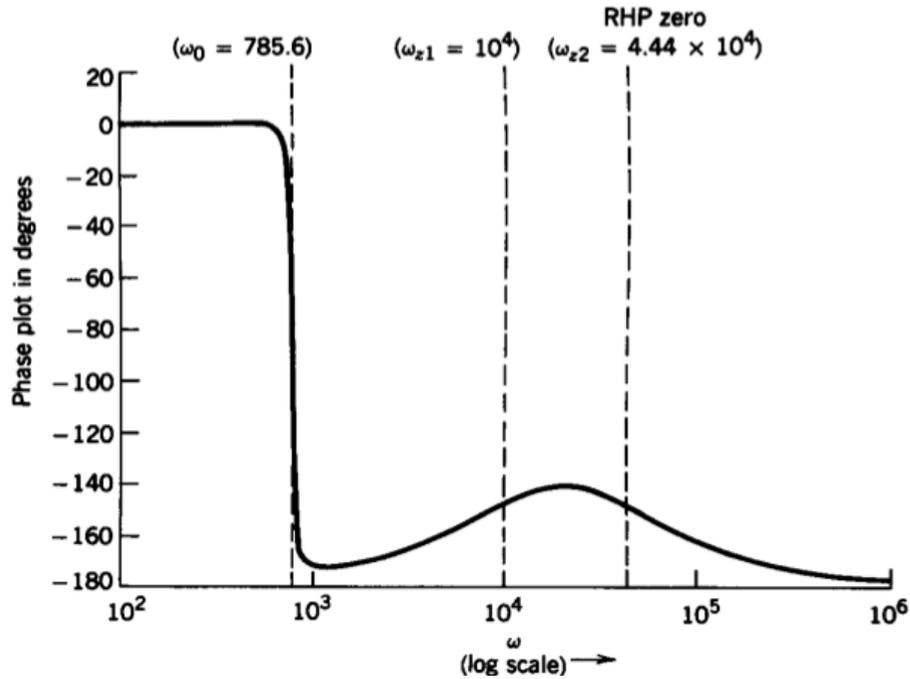

# A few readings for controller design

# A few readings for controller design

- [Control Design of a Boost Converter Using Frequency Response Data](#)
- [PID Control Tuning for Buck Converter](#)
- [Design digital controllers for power electronics using simulation](#)
- [Bode Response of Simulink Model](#)
- [How to Run an AC Sweep with PSIM?](#)
- [Peak Current Control with PSIM](#)
- [Plexim-Frequency Analysis of Buck Converter](#)


# Controller Design

# Controller Design

## Generalized Compensated Error Amplifier

# Controller Design
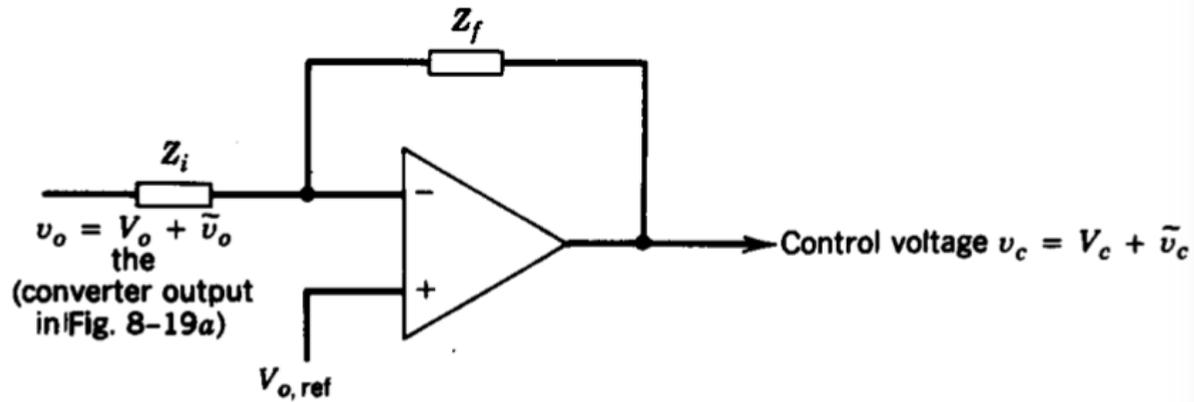
## Generalized Compensated Error Amplifier



# Types of Error Amplifier

# Types of Error Amplifier

Common Ones:

- Type-1
- Type-2
- Type-3

# Type-1 Error Amplifier


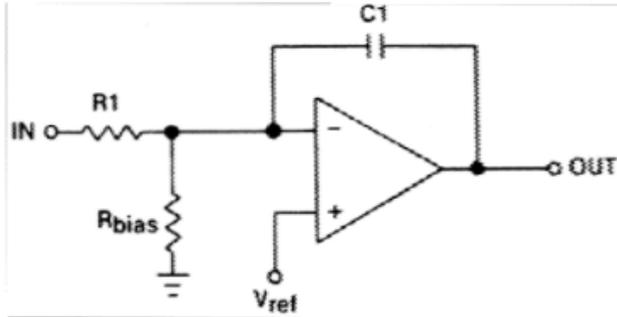


Figure 5. Schematic Diagram of a Type 1 Amplifier

Simple Integrator

Has one pole at the origin

# Type-1 Error Amplifier

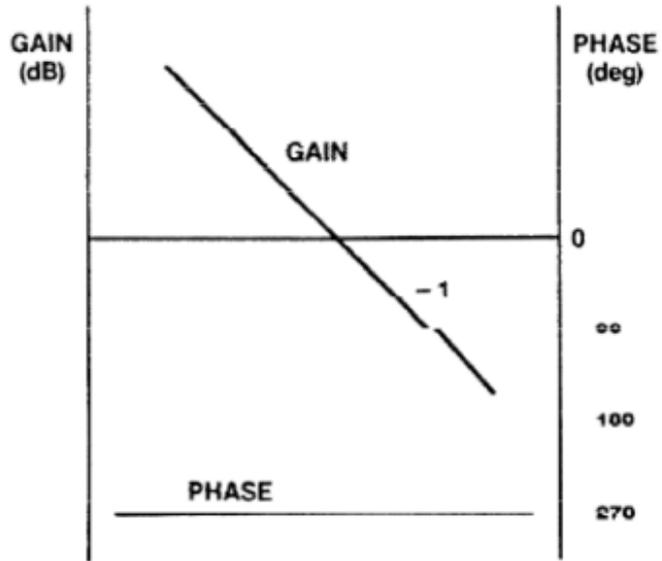

*Figure 6. Transfer Function of a Type 1 Amplifier*

# Type-2 Error Amplifier (Most Common Type)

# Type-2 Error Amplifier (Most Common Type)

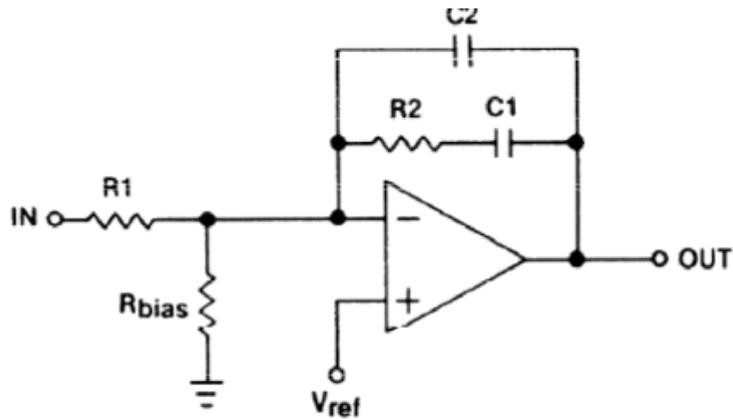


Figure 7. Schematic Diagram of a Type 2 Amplifier

Has two poles: at origin and one at zero-pole pair

90 degrees phase boost can be obtained due to single zero

# Type-2 Error Amplifier (Most Common Type)

# Type-2 Error Amplifier (Most Common Type)

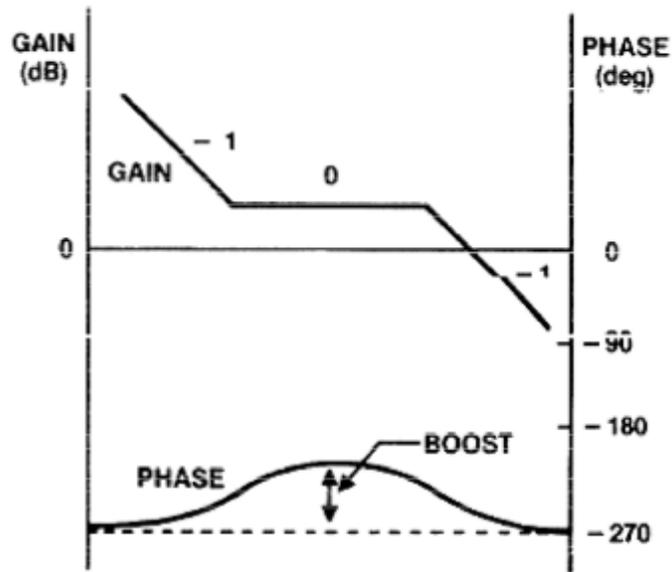


Figure 8. Transfer Function of a Type 2 Amplifier

Note the phase boost

# Type-3 Error Amplifier

# Type-3 Error Amplifier


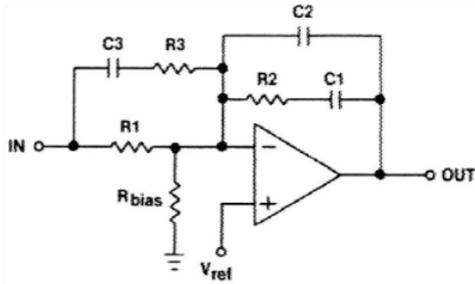


Figure 9. Schematic Diagram of a Type 3 Amplifier

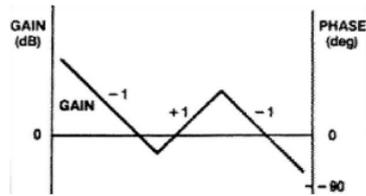

has two zeros can boost up to 180 degrees

# A Few Examples

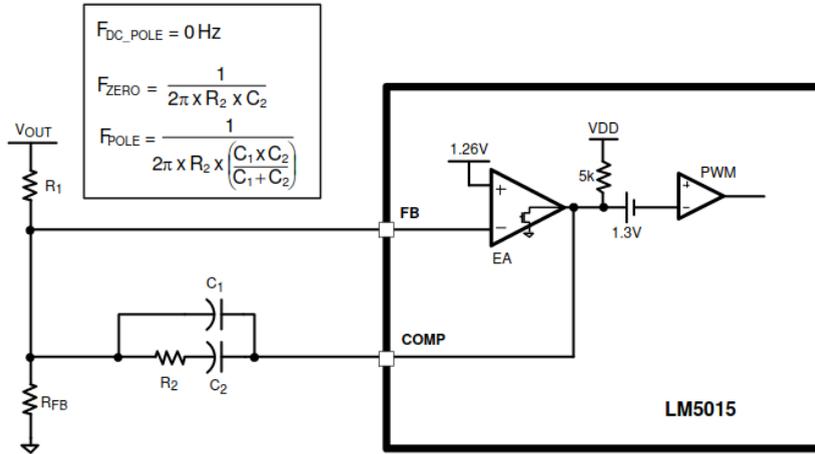


Figure 15. Type II Compensator

- [TL494](#), pg. 7, 15
- [LM5015](#), Fig. 12, 15


# Putting all Together

## Putting all Together

A controller just increases the gain (Proportional)

# Putting all Together
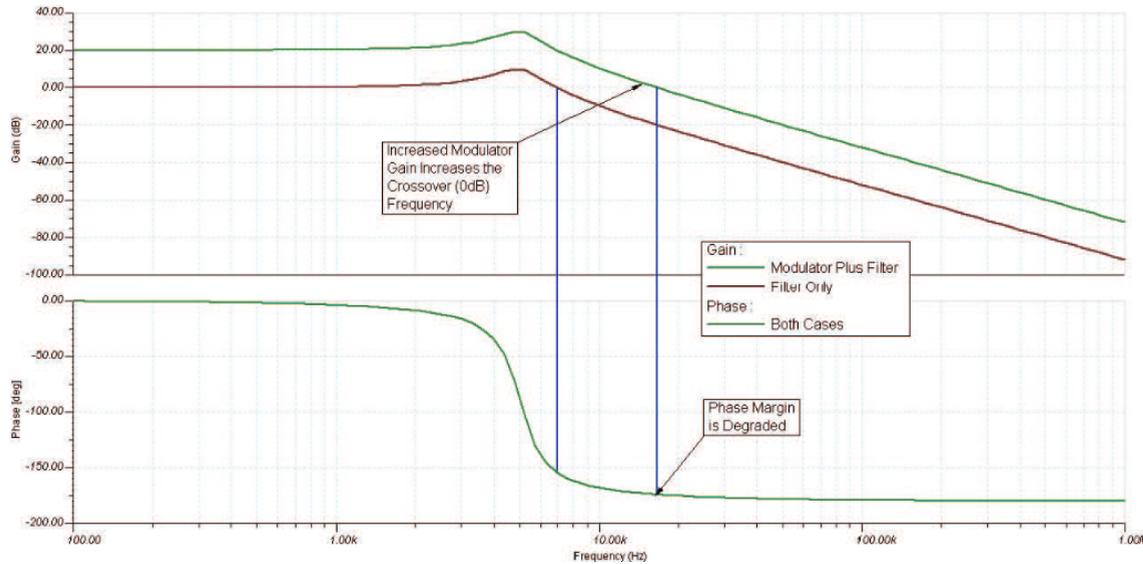
## A controller just increases the gain (Proportional)



Increasing gain usually reduces phase margin (and reduces stability) 53 / 80


# Putting all Together

## Putting all Together

A proper controller (adjust gain and phase margin)
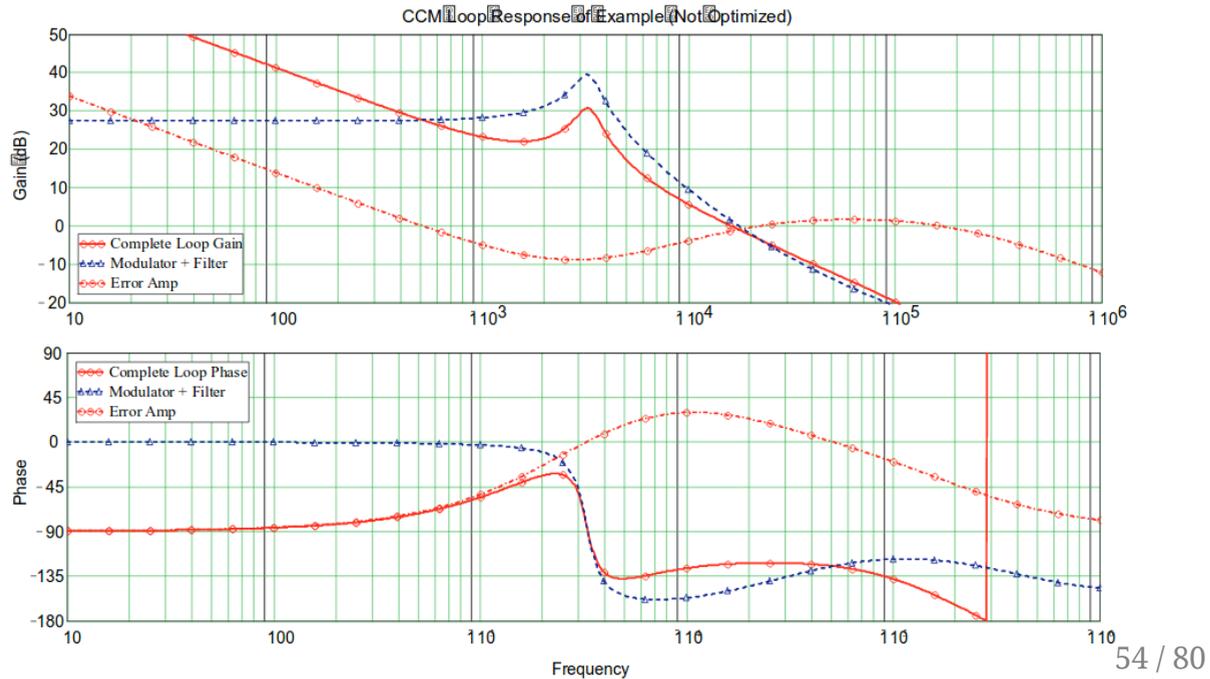
# Putting all Together

A proper controller (adjust gain and phase margin)



# More Information



# More Information

- Fundamentals of Power Electronics, Erickson
- [Phase Margin, Crossover Frequency, and Stability](#)
- [Loop Stability Analysis of Voltage Mode Buck Regulator](#)
- [DC-DC Converters Feedback and Control](#)
- [Modeling and Loop Compensation Design](#)
- [Compensator Design Procedure](#)

You can download this presentation from:  
[keysan.me/ee464](https://keysan.me/ee464)


Saved for further reference

Ready?

Saved for further reference

Ready?

Down the rabbit hole

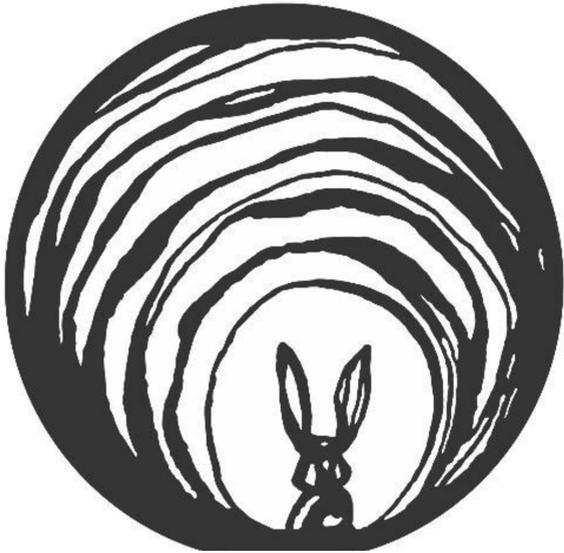

# Linearization with State-Space Averaging

# Linearization with State-Space Averaging

- Represent everything in matrix form

# Linearization with State-Space Averaging

- Represent everything in matrix form
- Inductor current, and capacitor voltage as state variables

# Linearization with State-Space Averaging

- Represent everything in matrix form
- Inductor current, and capacitor voltage as state variables
- Obtain two states (for switch on and switch off)

## Linearization with State-Space Averaging

- Represent everything in matrix form
- Inductor current, and capacitor voltage as state variables
- Obtain two states (for switch on and switch off)
- Find the weighted average

# Linearization with State-Space Averaging

# Linearization with State-Space Averaging

Obtain two states (for switch on and switch off)

## Linearization with State-Space Averaging

Obtain two states (for switch on and switch off)

$$\dot{x} = A_1 x + B_1 v_d \text{ (for switch on, dTs)}$$

## Linearization with State-Space Averaging

Obtain two states (for switch on and switch off)

$$\dot{x} = A_1 x + B_1 v_d \text{ (for switch on, } dTs)$$

$$\dot{x} = A_2 x + B_2 v_d \text{ (for switch off, } (1-d)Ts)$$

where,  $A_1$  and  $A_2$  are state matrices

$B_1$  and  $B_2$  are vectors

**Example:**

**Mohan 10.1**

# Linearization with State-Space Averaging

# Linearization with State-Space Averaging

Find weighted average

## Linearization with State-Space Averaging

Find weighted average

$$A = dA_1 + (1 - d)A_2$$

$$B = dB_1 + (1 - d)B_2$$

## Linearization with State-Space Averaging

Find weighted average

$$A = dA_1 + (1 - d)A_2$$

$$B = dB_1 + (1 - d)B_2$$

$$\dot{x} = Ax + Bv_d \text{ (for switch off, } (1-d)T_s)$$

Similar calculations for the output voltage

$$v_o = C_1 x \text{ (for switch on, } dT_s)$$

$$v_o = C_2 x \text{ (for switch off, } (1-d)T_s)$$

where  $C_1$  and  $C_2$  are transposed vectors

Similar calculations for the output voltage

$$v_o = Cx$$

$$C = dC_1 + (1 - d)C_2$$

where  $C_1$  and  $C_2$  are transposed vectors

# Use Small signal model

Equations 10.46-10.52

## Use Small signal model

Equations 10.46-10.52

$$x = X + \tilde{x}$$

## Use Small signal model

Equations 10.46-10.52

$$\mathbf{x} = \mathbf{X} + \tilde{\mathbf{x}}$$

$$\dot{\tilde{\mathbf{x}}} = \mathbf{A}\mathbf{X} + \mathbf{B}V_d + \mathbf{A}\tilde{\mathbf{x}}$$

$$+ [(\mathbf{A}_1 - \mathbf{A}_2)\mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2)V_d]\tilde{d}$$

## Use Small signal model

Equations 10.46-10.52

$$x = X + \tilde{x}$$

$$\dot{\tilde{x}} = AX + BV_d + A\tilde{x}$$

$$+ [(A_1 - A_2)X + (B_1 - B_2)V_d]\tilde{d}$$

In the steady state:

$$\dot{X} = 0$$

Use derivations from eq.10.53-10.59

# Steady State DC Voltage Transfer Function

# Steady State DC Voltage Transfer Function

$$\frac{V_o}{V_d} = -CA^{-1}B$$

# Small Signal Model to Get AC Transfer Function

# Small Signal Model to Get AC Transfer Function


$$\begin{aligned} T_p(s) &= \frac{\tilde{v}_o(s)}{\tilde{d}(s)} \\ &= C[sI - A]^{-1}[(A_1 - A_2)X + (B_1 - B_2)V_d] \\ &\quad + (C_1 - C_2)X] \end{aligned}$$

## Example (Mohan 10-1)

Find the transfer function of forward converter
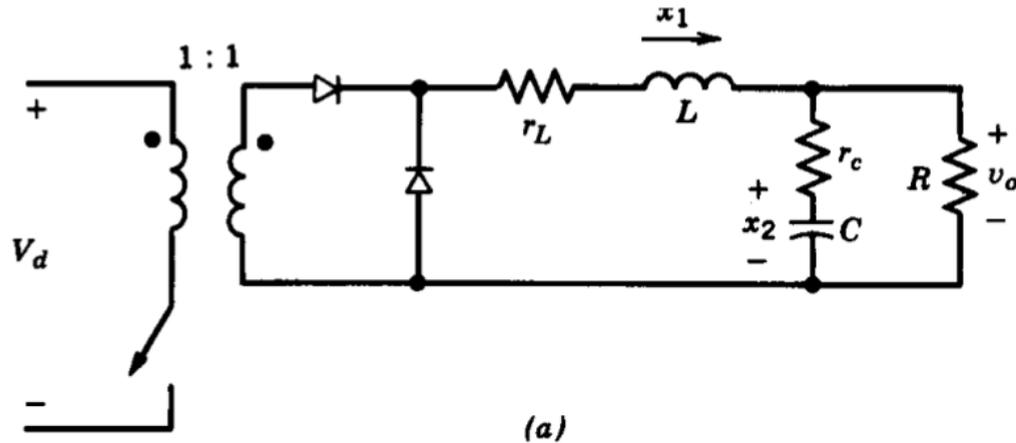
# Example (Mohan 10-1)

Find the transfer function of forward converter




Note the state variables

# Example (Mohan 10-1)

Switch ON

# Example (Mohan 10-1)

Switch ON

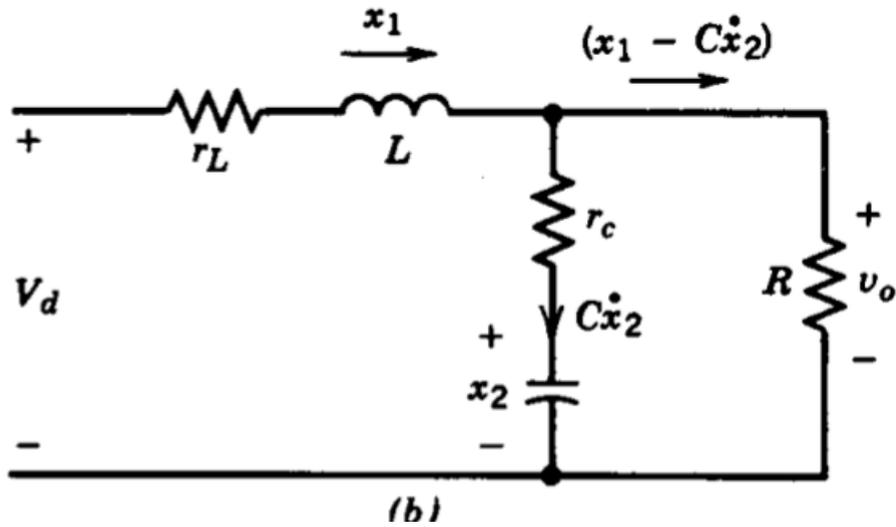


# Example (Mohan 10-1)

Switch OFF

# Example (Mohan 10-1)

Switch OFF

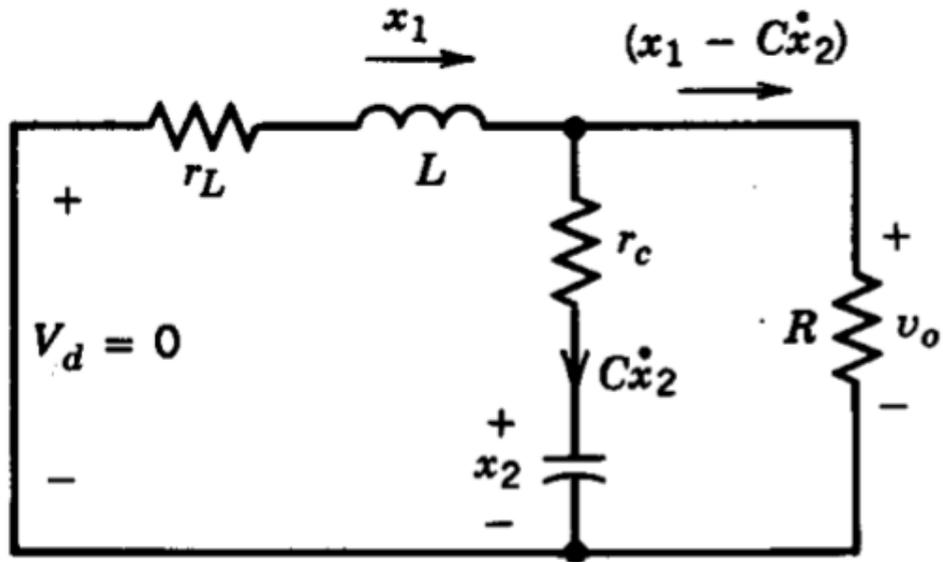

# Example (Mohan 10-1)

## Steady State Transfer Function

# Example (Mohan 10-1)

Steady State Transfer Function

$$\frac{V_o}{V_d} = -CA^{-1}B$$

# Example (Mohan 10-1)

Steady State Transfer Function

$$\frac{V_o}{V_d} = -CA^{-1}B$$

$$\frac{V_o}{V_d} = D \frac{R + r_C}{R + (r_C + r_L)}$$

# Example (Mohan 10-1)

## Steady State Transfer Function

$$\frac{V_o}{V_d} = -CA^{-1}B$$

$$\frac{V_o}{V_d} = D \frac{R + r_C}{R + (r_C + r_L)}$$

If parasitic resistances are small

# Example (Mohan 10-1)

## Steady State Transfer Function

$$\frac{V_o}{V_d} = -CA^{-1}B$$

$$\frac{V_o}{V_d} = D \frac{R + r_C}{R + (r_C + r_L)}$$

If parasitic resistances are small

$$\frac{V_o}{V_d} \approx D$$

# Example (Mohan 10-1)

## AC Transfer Function

# Example (Mohan 10-1)

AC Transfer Function

$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$

# Example (Mohan 10-1)

## AC Transfer Function

$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$

$$T_p(s) = V_d \frac{1 + sr_C C}{LC[s^2 + s(1/RC + (r_C + r_L)/L) + 1/LC]}$$

# Example (Mohan 10-1)

## AC Transfer Function

$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$

$$T_p(s) = V_d \frac{1 + sr_C C}{LC[s^2 + s(1/RC + (r_C + r_L)/L) + 1/LC]}$$

Remember this equation?

# Example (Mohan 10-1)

## AC Transfer Function

$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$

$$T_p(s) = V_d \frac{1 + sr_C C}{LC[s^2 + s(1/RC + (r_C + r_L)/L) + 1/LC]}$$

Remember this equation?

$$s^2 + 2\xi\omega_0 s + \omega_0^2$$

# Example (Mohan 10-1)

AC Transfer Function

$$s^2 + 2\xi\omega_0 s + \omega_0^2$$

# Example (Mohan 10-1)

AC Transfer Function

$$s^2 + 2\xi\omega_0 s + \omega_0^2$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

# Example (Mohan 10-1)

## AC Transfer Function

$$s^2 + 2\xi\omega_0 s + \omega_0^2$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\xi = \frac{1/RC + (r_C + r_L)/L}{2\omega_0}$$

# Example (Mohan 10-1)

AC Transfer Function Becomes

$$T_p(s) = V_d \frac{\omega_0^2}{\omega_z} \frac{s + \omega_z}{s^2 + 2\xi\omega_0 s + \omega_0^2}$$

$$\text{where } \omega_z = \frac{1}{r_C C}$$

# Example (Mohan 10-1)

Put the parameters into the equation

$$V_d = 8V$$

$$V_o = 5V$$

$$r_L = 20m\Omega$$

$$L = 5\mu H$$

$$r_C = 10m\Omega$$


$$C = 2mF$$

$$R = 200m\Omega$$

$$f_s = 200kHz$$


# Example (Mohan 10-1)

## Bode Plot (Gain)

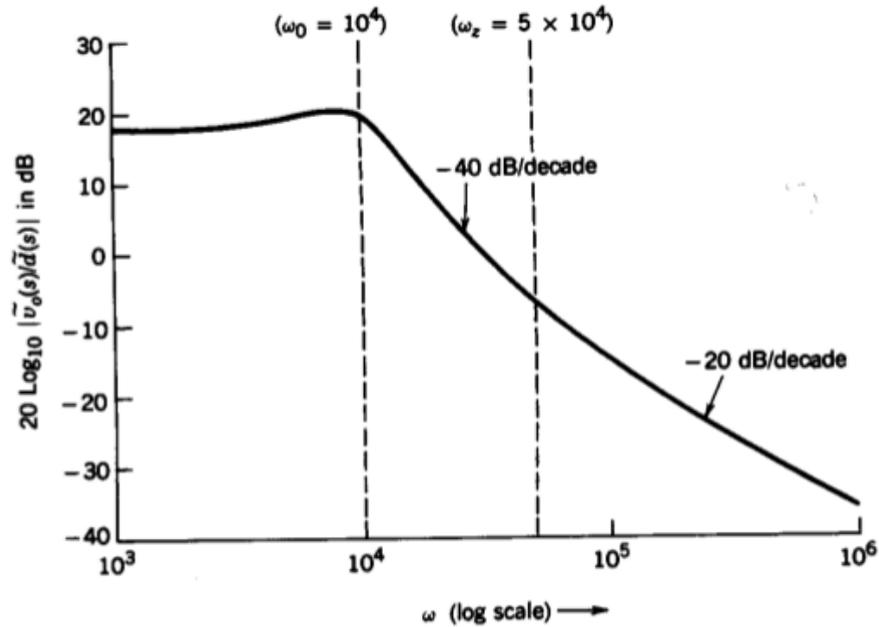

# Example (Mohan 10-1)

## Bode Plot (Phase)

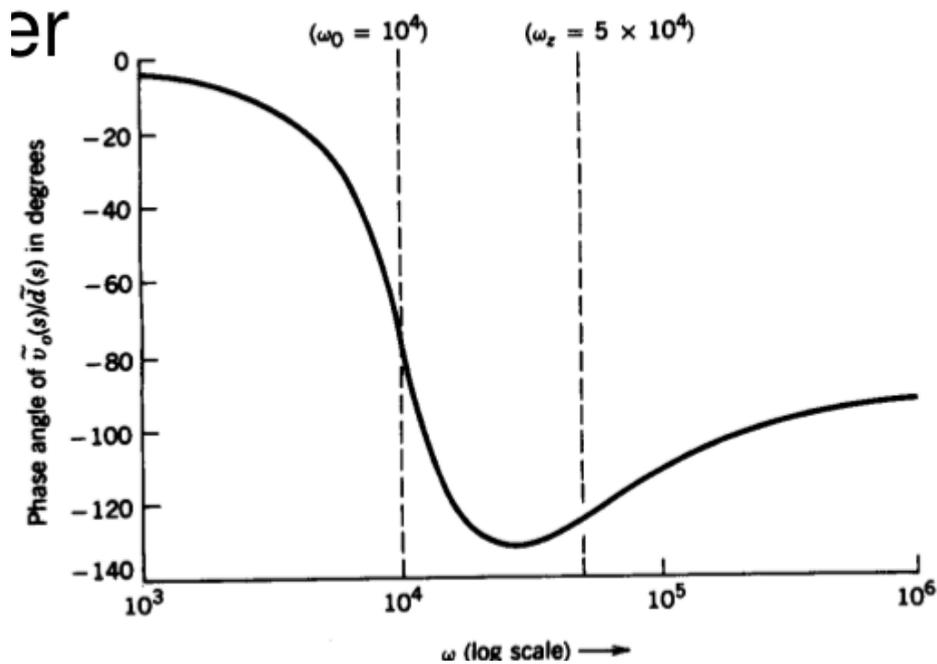

# Flyback Converter

# Flyback Converter

Equation 10-86

$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$

# Flyback Converter

Equation 10-86


$$T_p(s) = \frac{\tilde{v}_o(s)}{\tilde{d}(s)}$$

$$T_p(s) = V_d f(D) \frac{(1 + s/\omega_{z1})(1 - s/\omega_{z2})}{as^2 + bs + c}$$

# Flyback Converter

# Flyback Converter

## Bode Plot (Gain)

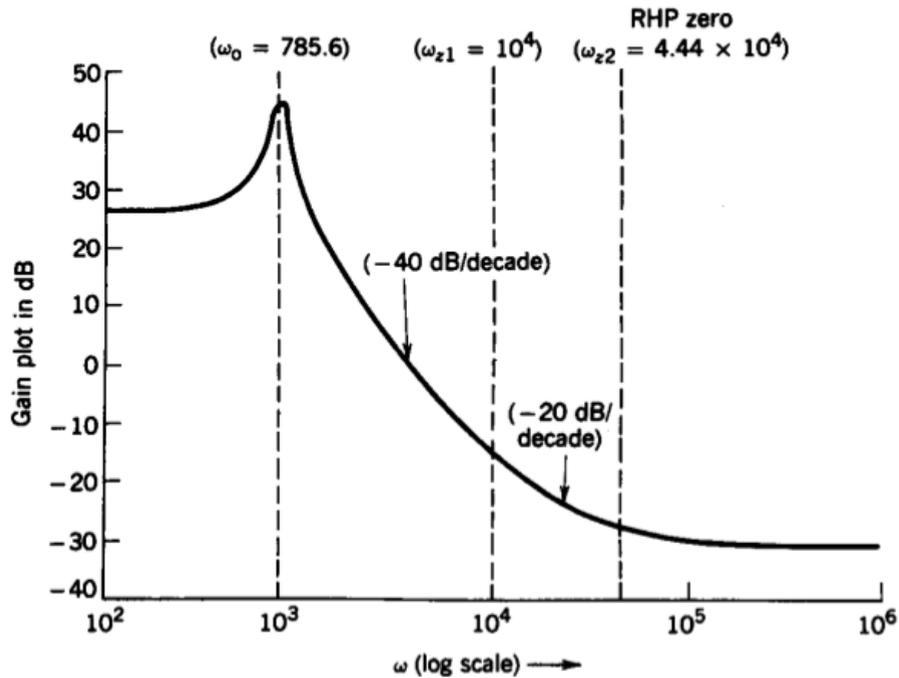

# Flyback Converter

# Flyback Converter

## Bode Plot (Phase)

