

EE-464 STATIC POWER CONVERSION-II


Multi Level Inverters

Ozan Keysan

keysan.me


Office: C-113 • Tel: 210 7586

Effect of Blanking (Dead) Time

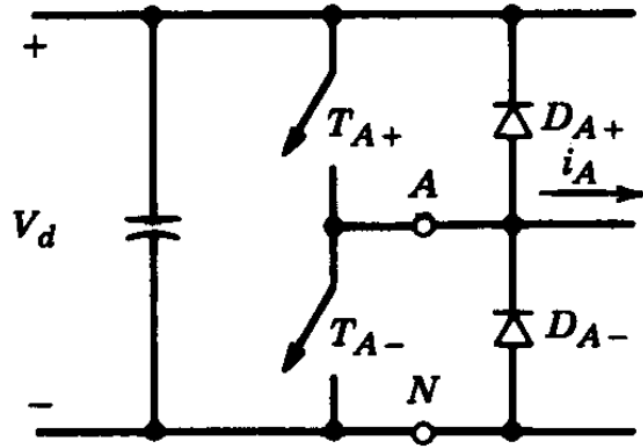


There has to be off time between switching instants to prevent short circuit of V_d (can be up to $2 - 3\mu s$)

Effect of Blanking (Dead) Time

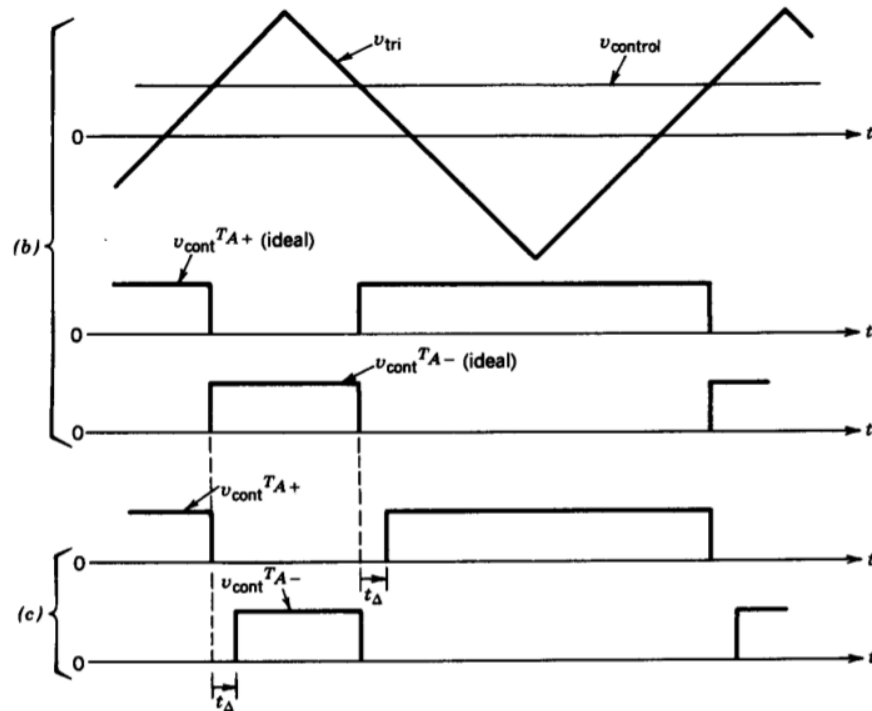

Effect of Blanking (Dead) Time

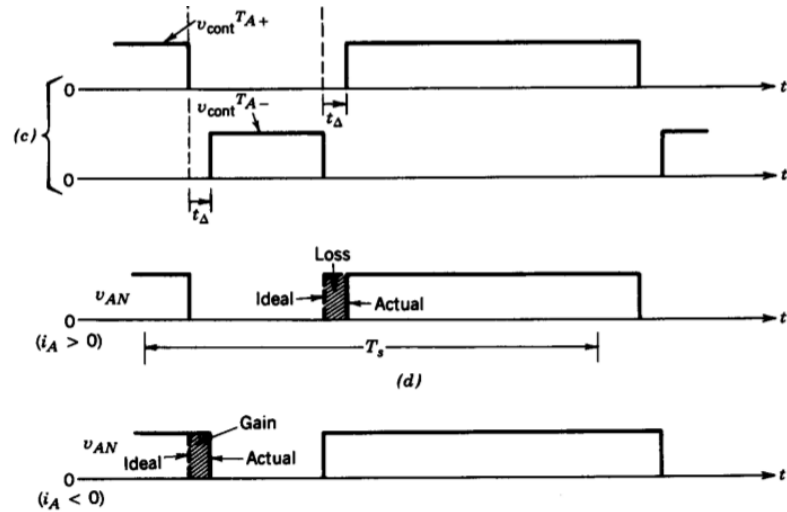

Results in non-linearity in the voltage output



[Reading assignment for curious students](#)

Effect of Blanking (Dead) Time


Effect of Blanking (Dead) Time

$$|\Delta V_o| = \frac{2t_{\Delta}}{T_s} V_d$$

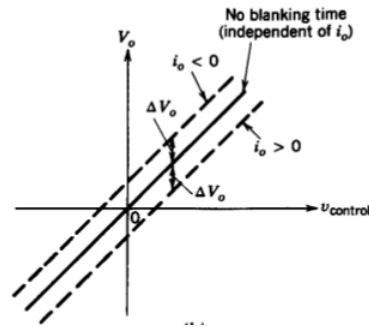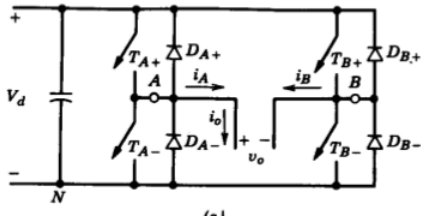Always reduce the output voltage magnitude wrt. current direction



Effect of Blanking (Dead) Time

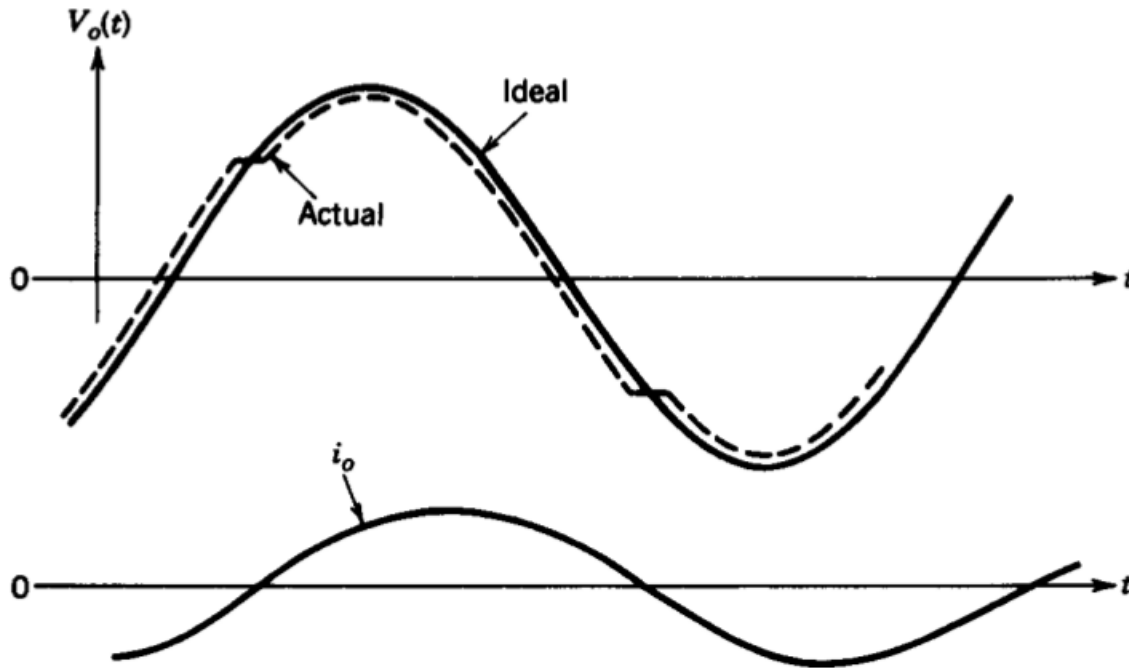

Multi-Level Inverters

Multi-Level Inverters

- Used commonly in high power (MW, kV) converters

Multi-Level Inverters

- Used commonly in high power (MW, kV) converters
- Increases output voltage capacity


Multi-Level Inverters

- Used commonly in high power (MW, kV) converters
- Increases output voltage capacity
- Minimizes THD even with low switching frequencies


Multi-Level Inverters

- Used commonly in high power (MW, kV) converters
- Increases output voltage capacity
- Minimizes THD even with low switching frequencies
- Reduce EMI due to lower voltage steps

Two-Level Inverter Waveform

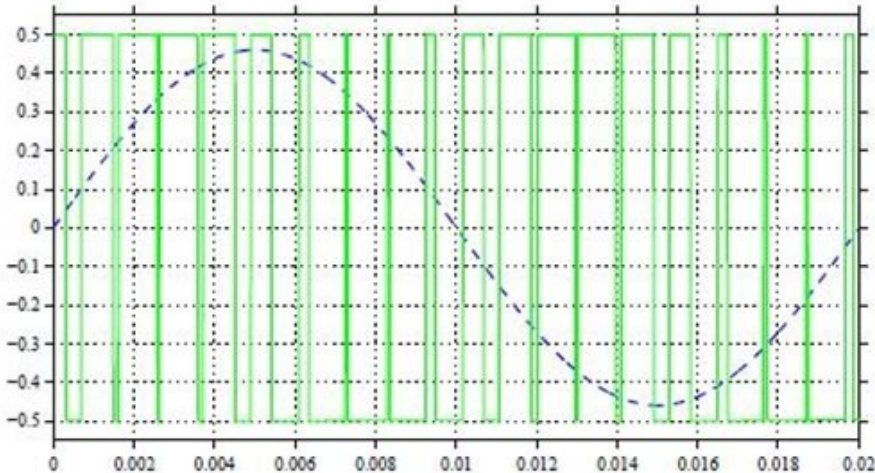

Multi-Level Inverter Waveforms

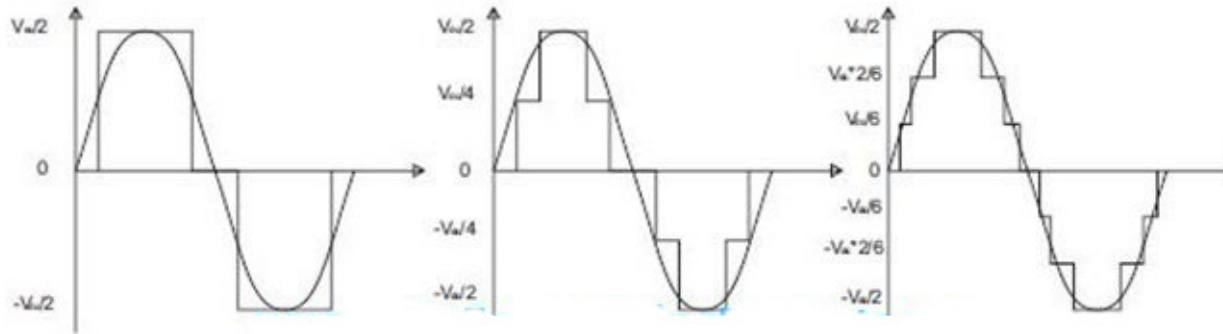


Three level,

Five Level,


and Seven Level Inverter Waveforms

H-Bridge Inverters

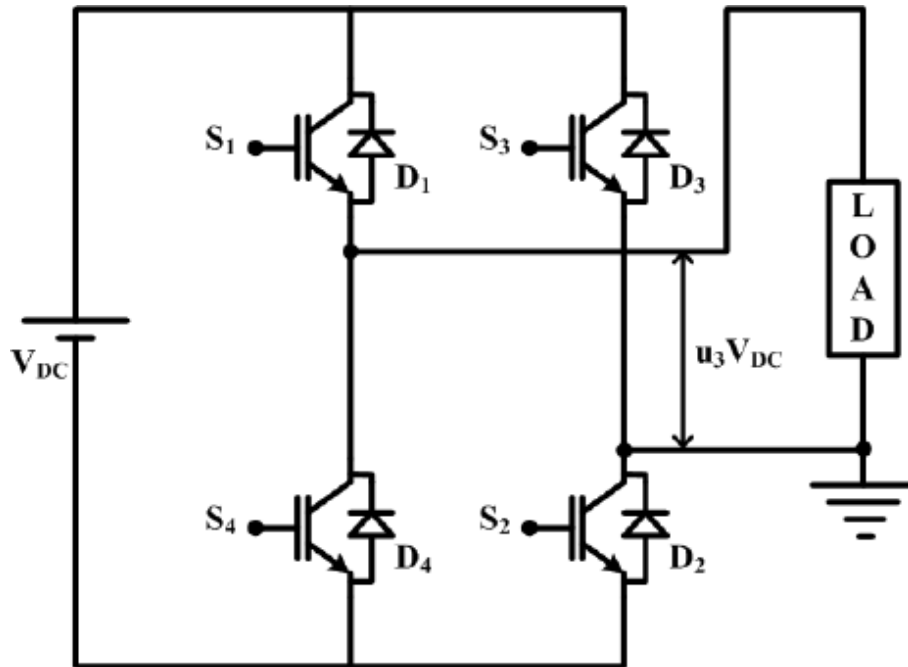

H-Bridge Inverters

Three Level (unipolar) PWM Output

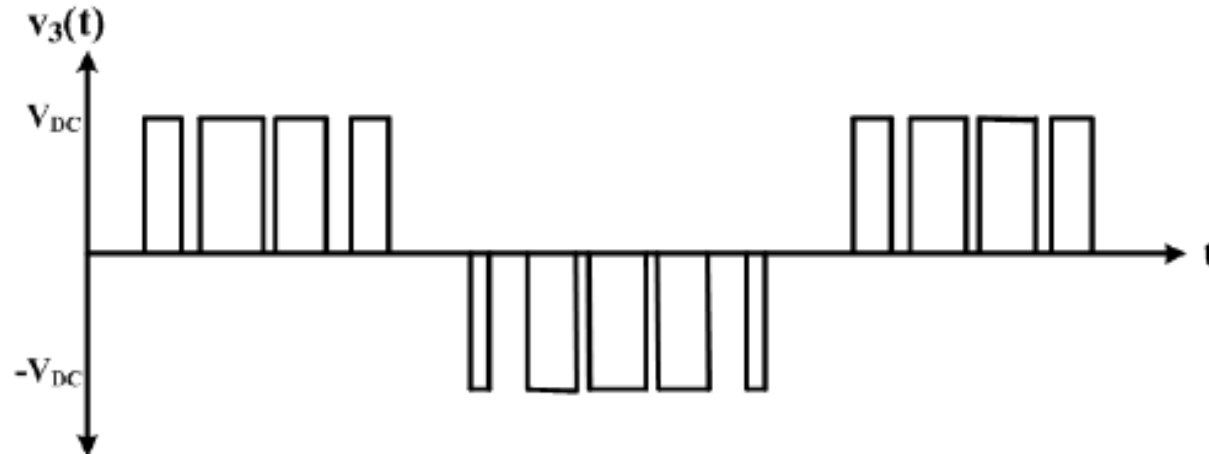

H-Bridges can be connected in series for higher voltages


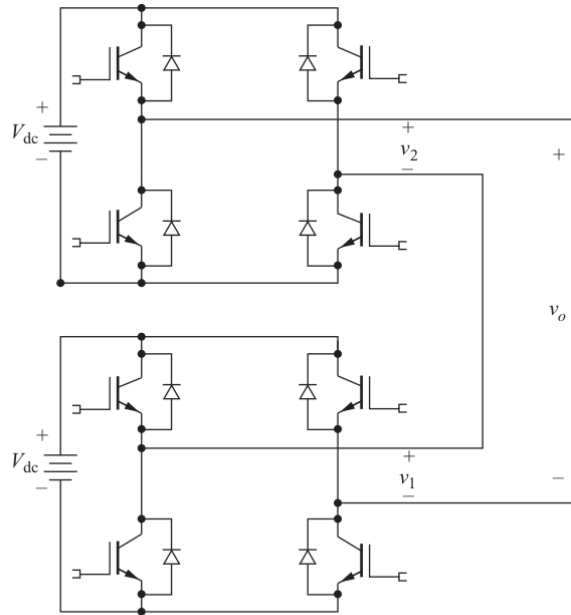


Figure 8-9 An inverter with two dc sources, each with an H bridge implemented with IGBTs.

What are the voltage levels?

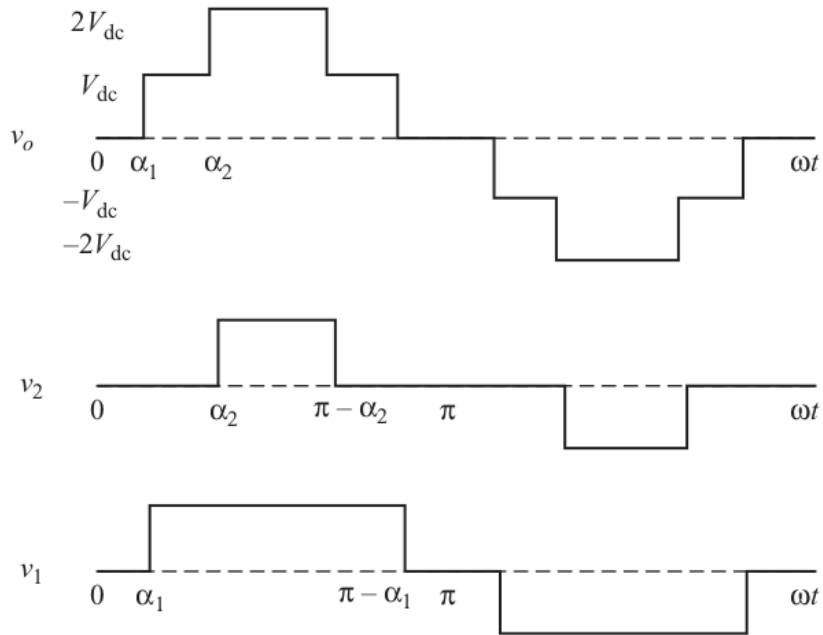
What are the voltage levels?: $2V_{dc}$, V_{dc} , 0 , $-V_{dc}$, $-2V_{dc}$




Specific harmonics can be eliminated by proper α_1 , α_2

Five-Series Cascaded H-Bridge Inverters


How many voltage levels?

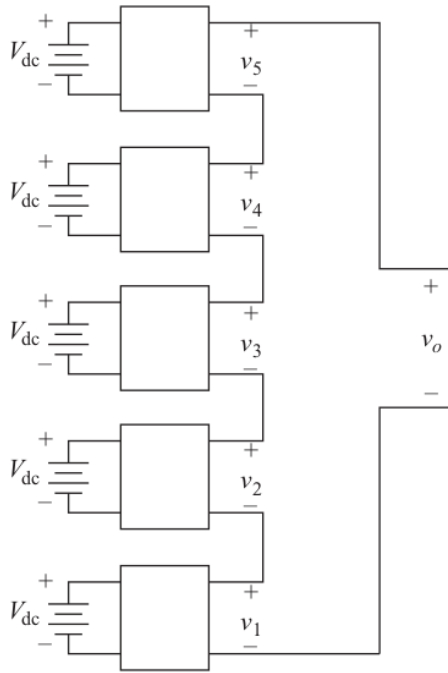


11-Level Cascaded H-Bridge Inverters

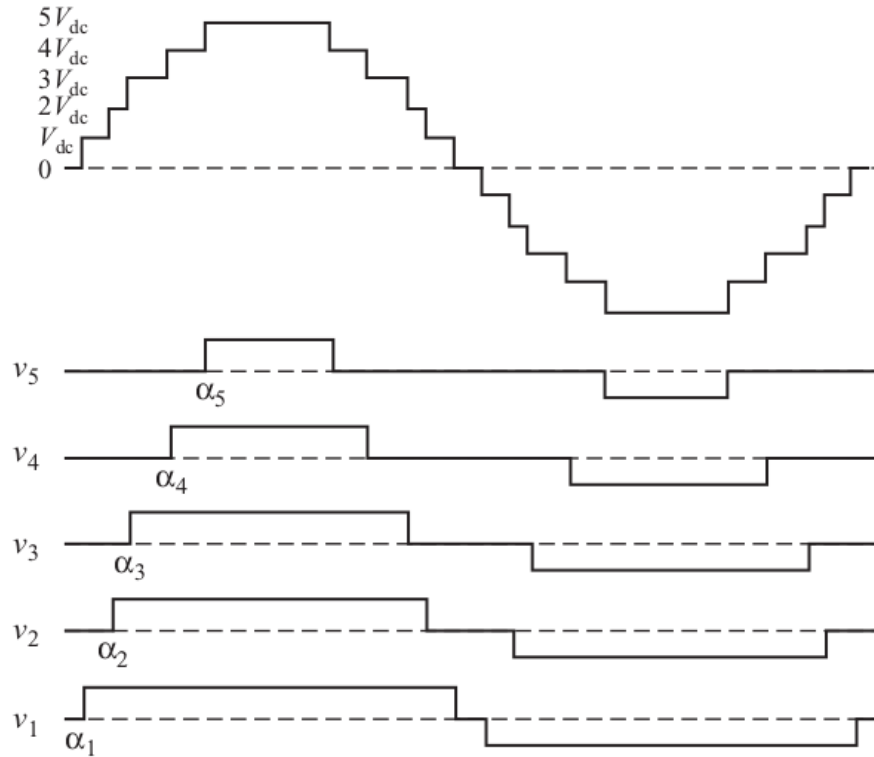

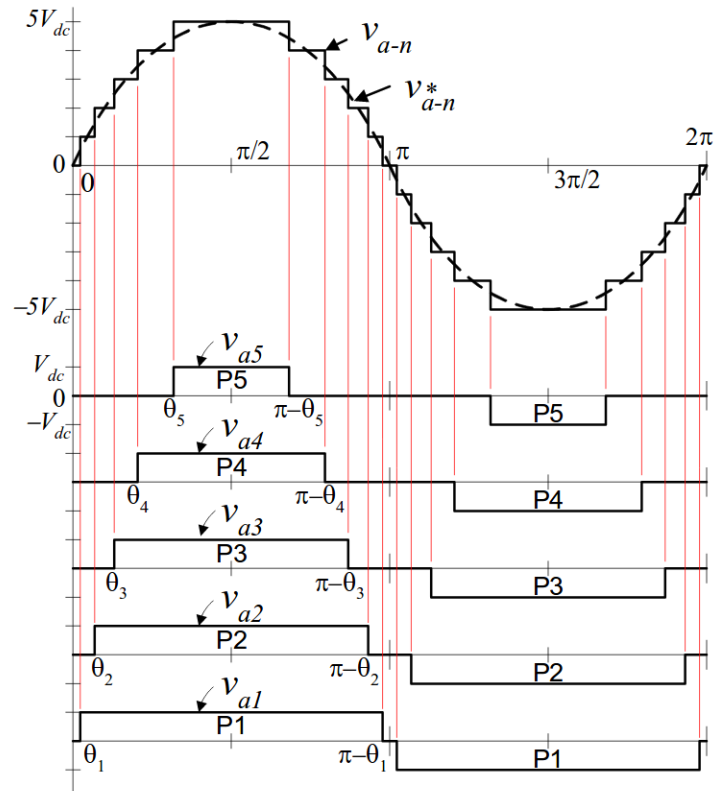11-Level Cascaded with Five Separate Sources




Alternate PWM Techniques

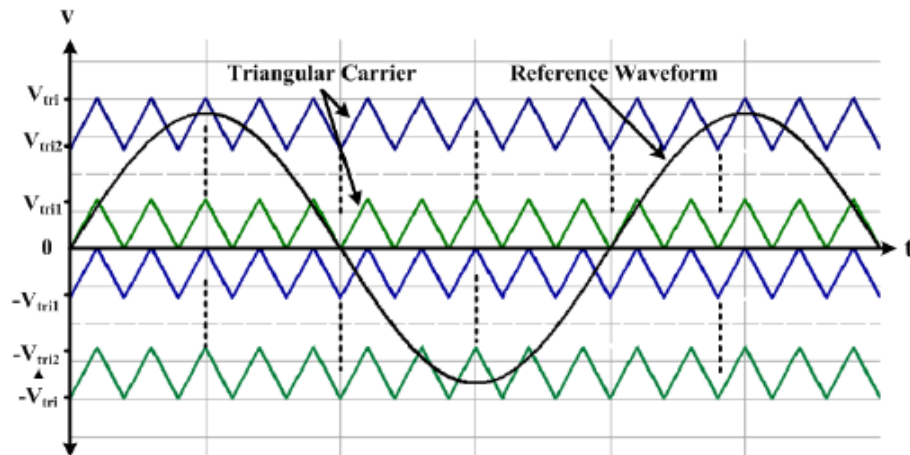


N-Level Cascaded H-Bridge Inverters

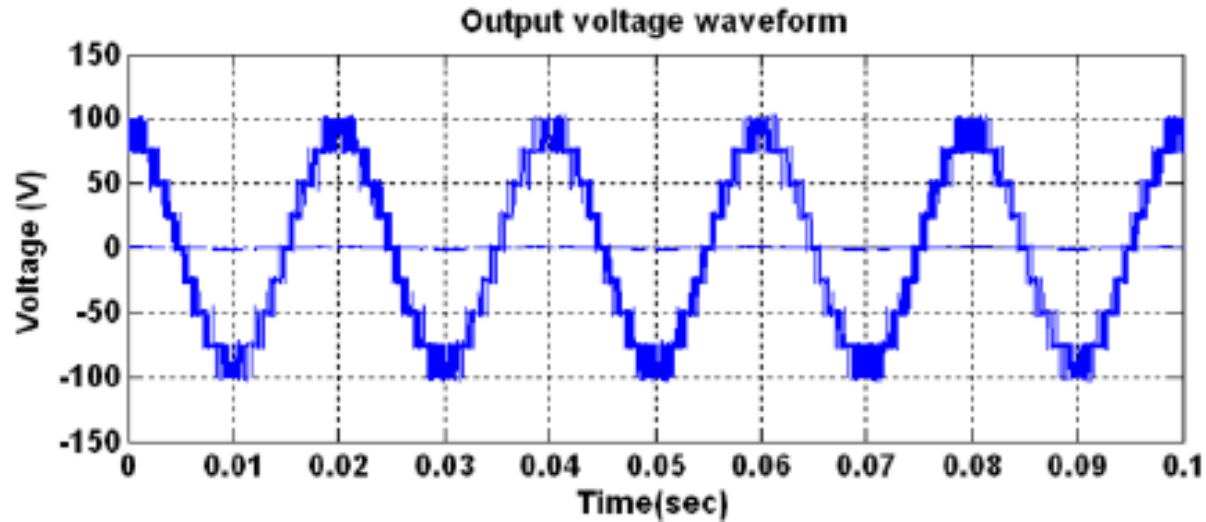Five-level Output Voltage Waveform ($f_c=3\text{kHz}$)




Multi-Level SVPWM

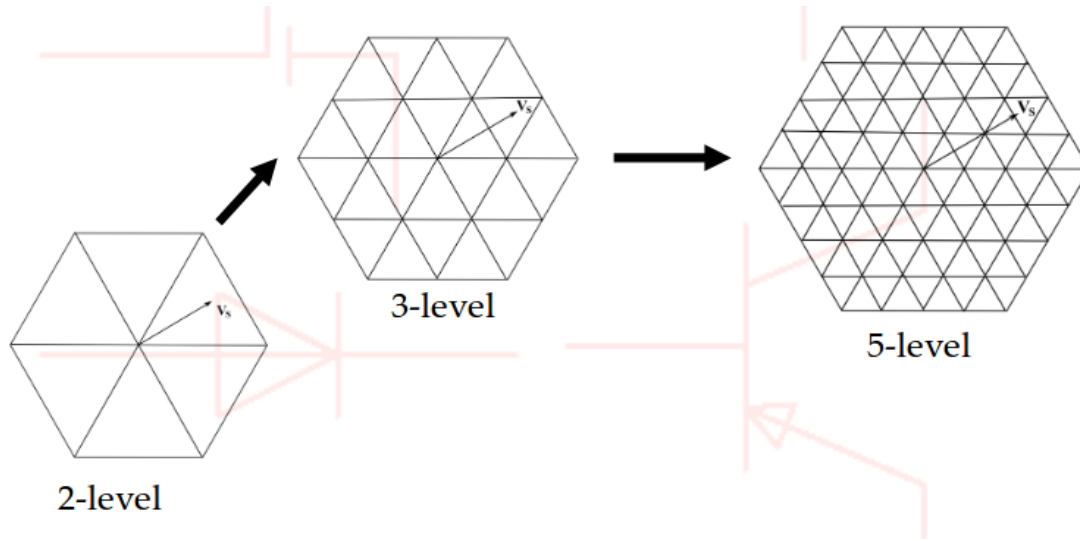


Multi-level SVPWM

3-Level

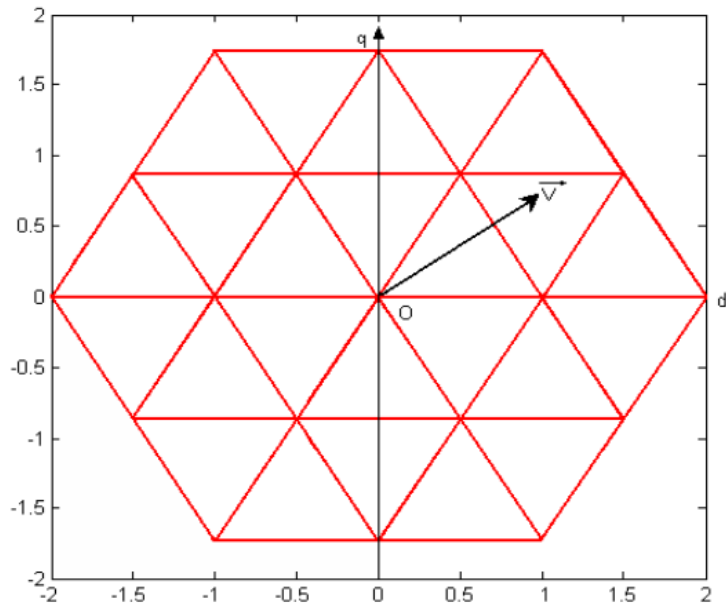


Multi-level SVPWM

5-Level

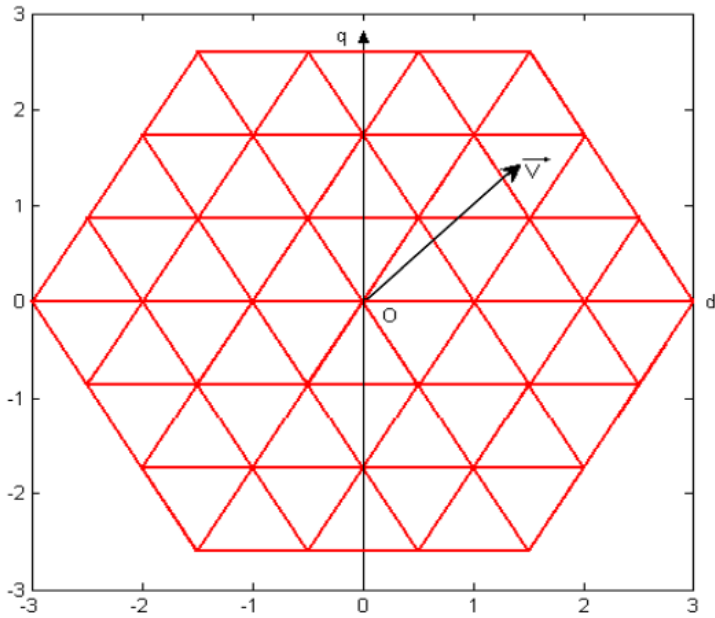


Multi-level SVPWM

Voltage Vectors of a 6-Level Inverter

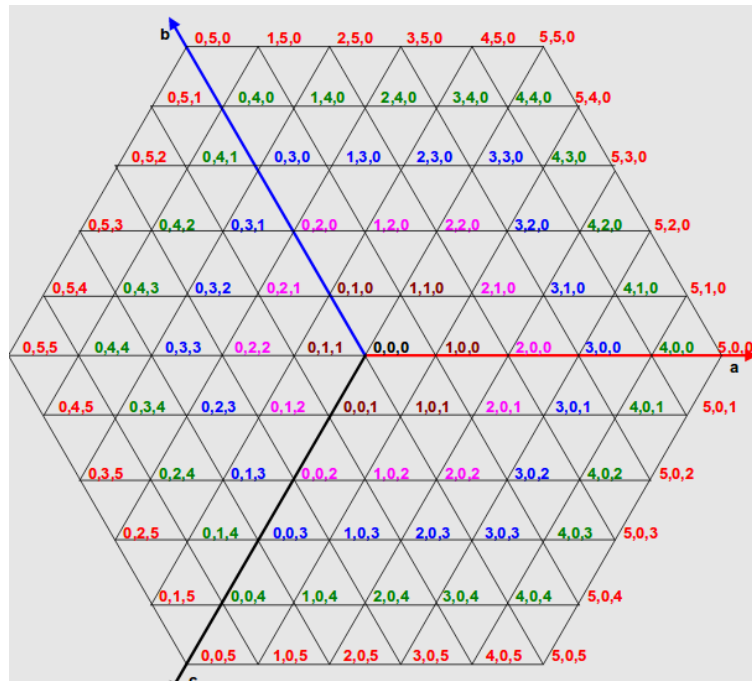

Diode Clamped Multi-level Inverters


Diode Clamped Multi-level Inverters

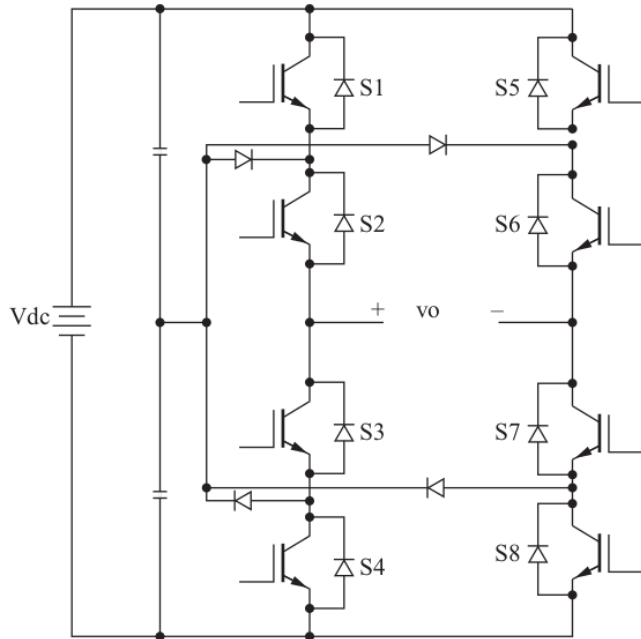

Five-level diode clamped inverter (Neutral Point Clamped (NPC))


Five-level diode clamped inverter

Voltage Levels: V_{dc}

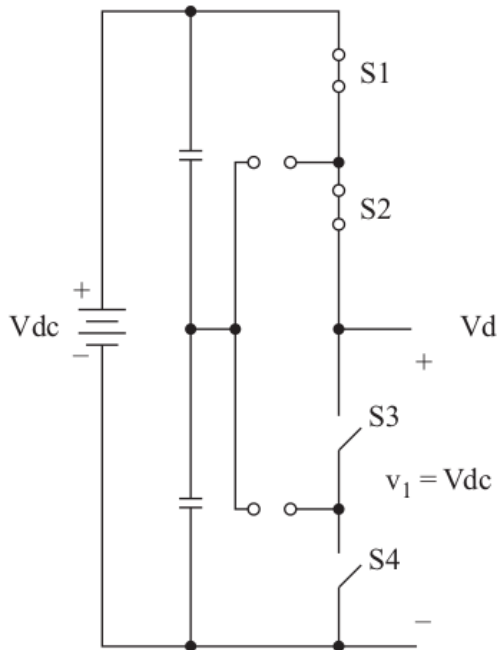


Five voltage-level diode clamped inverter

Voltage Levels: 0

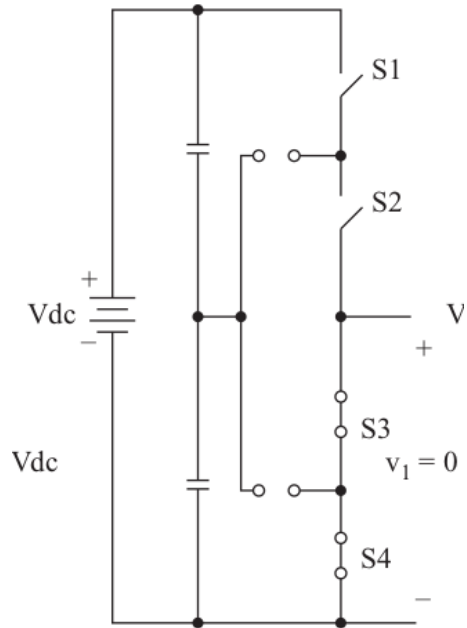

Five voltage-level diode clamped inverter


Voltage Levels: $V_{dc}/2$

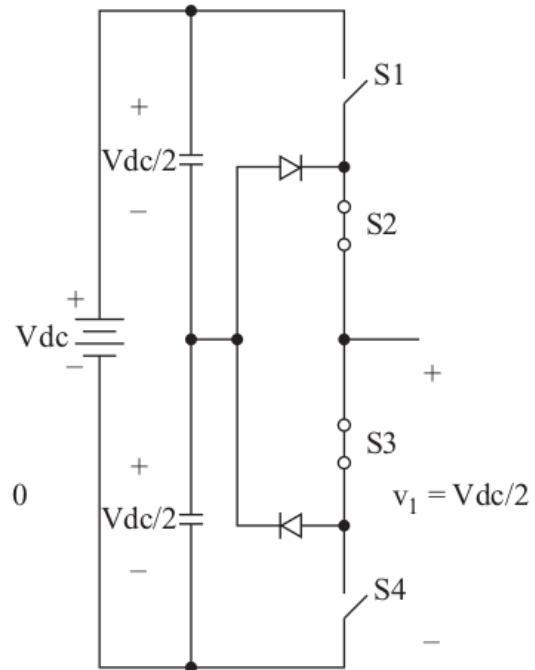

Even Higher Voltage Levels


Even Higher Voltage Levels

3 voltage sources cascaded

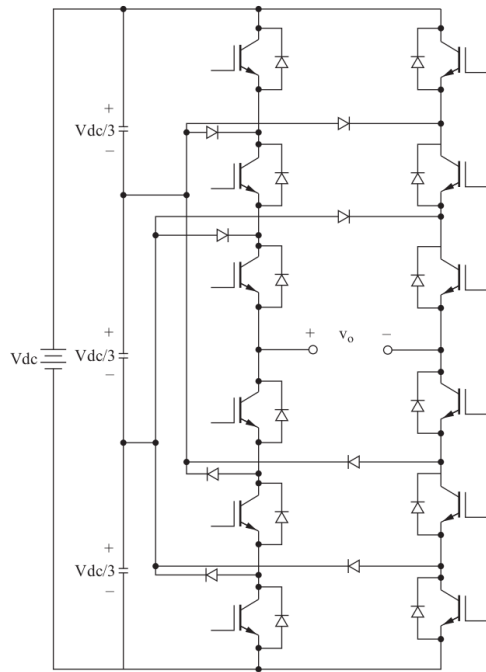

Even Higher Voltage Levels

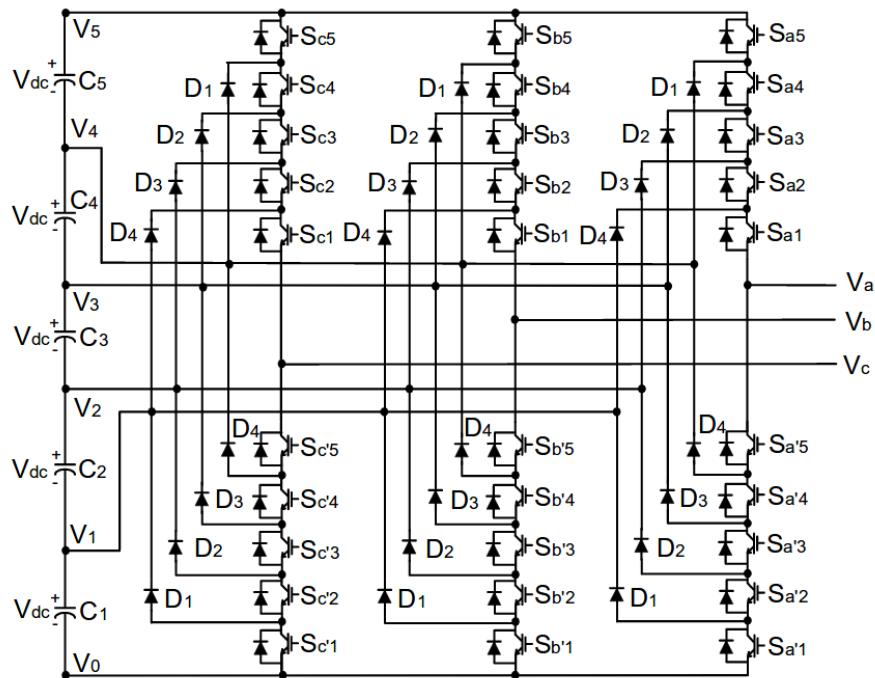5-Photovoltaic panels connected in series



Even Higher Voltage Levels

Switching States: Can you find the pattern?

Even Higher Voltage Levels


Switching States: Can you find the pattern?

Voltage V_{a0}	Switch State									
	S_{a5}	S_{a4}	S_{a3}	S_{a2}	S_{a1}	$S_{a'5}$	$S_{a'4}$	$S_{a'3}$	$S_{a'2}$	$S_{a'1}$
$V_5 = 5V_{dc}$	1	1	1	1	1	0	0	0	0	0
$V_4 = 4V_{dc}$	0	1	1	1	1	1	0	0	0	0
$V_3 = 3V_{dc}$	0	0	1	1	1	1	1	0	0	0
$V_2 = 2V_{dc}$	0	0	0	1	1	1	1	1	0	0
$V_1 = V_{dc}$	0	0	0	0	1	1	1	1	1	0
$V_0 = 0$	0	0	0	0	0	1	1	1	1	1

A set of five switches is on at any time

Even Higher Voltage Levels

Line-to-line voltage

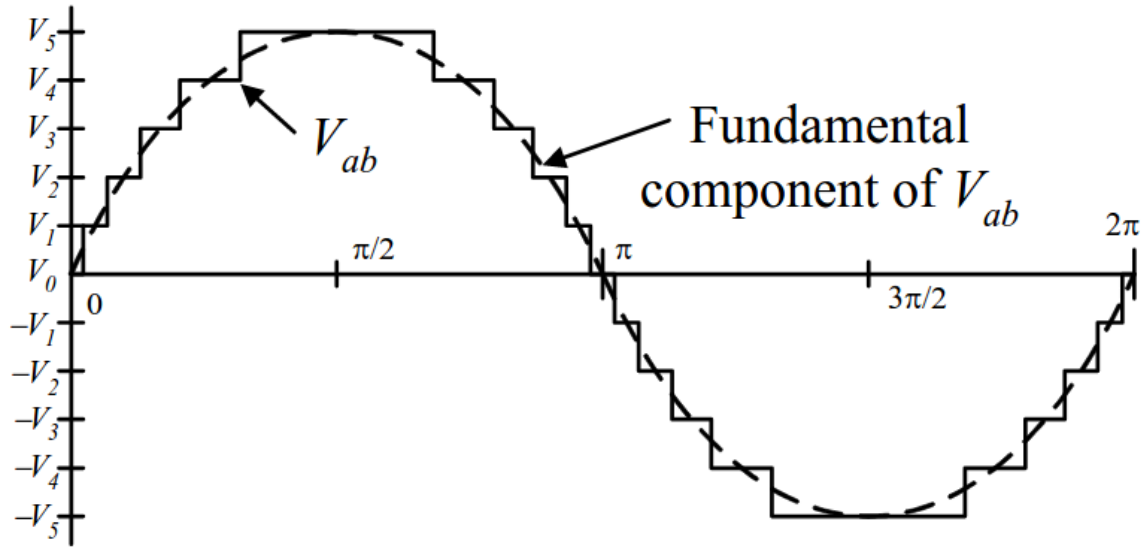

Further Reading

- [Multilevel Inverter – Types & Advantages](#)
- [Introduction to MultiLevel Inverters](#)
- [Multilevel Inverters](#)
- [Multilevel Inverters: A Survey of Topologies, Controls, and Applications](#)
- [Multilevel Power Converters](#)

You can download this presentation from:
keysan.me/ee464