

EE-463 STATIC POWER CONVERSION-I

3-Phase Diode Rectifiers

Ozan Keysan

keysan.me

Office: C-113 • Tel: 210 7586


3-Phase Half Wave Rectifier

3-Phase Half Wave Rectifier

N-Phase Generalized Form


3-Phase Half Wave Rectifier

N-Phase Generalized Form

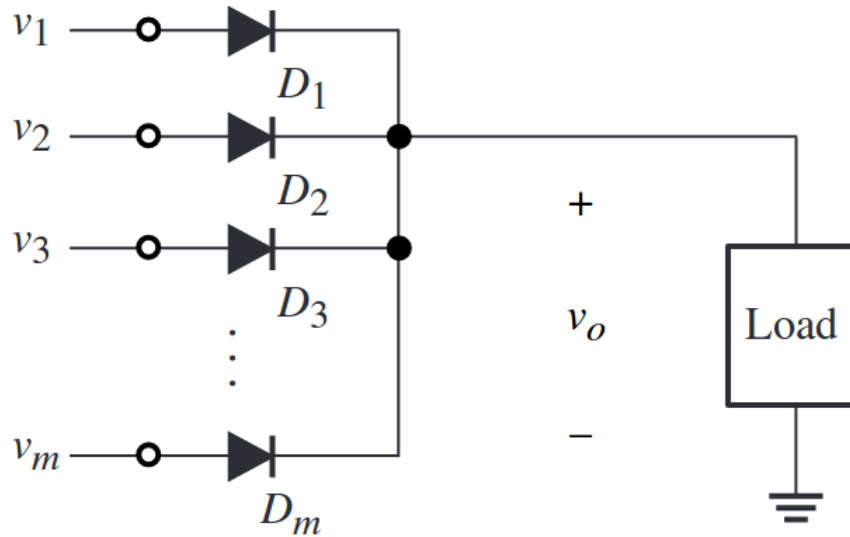


3-Phase Half Wave Rectifier

Voltage Waveforms

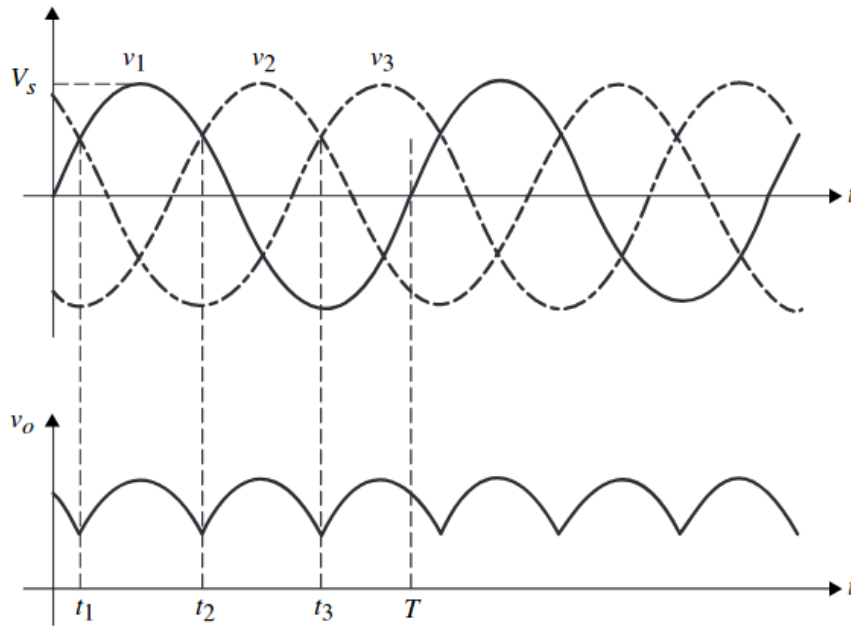

3-Phase Half Wave Rectifier

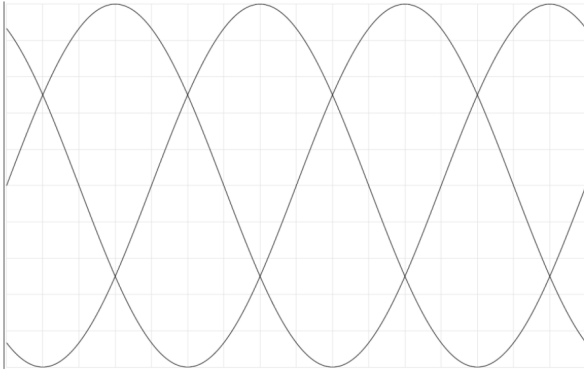

3-Phase Half Wave Rectifier

Average Voltage?

$$V_{dc} = \frac{3\sqrt{6}}{2\pi} V_{rms}$$

3-Phase Half Wave Rectifier

Average Voltage?

$$V_{dc} = \frac{3\sqrt{6}}{2\pi} V_{rms}$$


Comparison with the single phase rectifier?

3-Phase Full Wave (Bridge) Rectifier



3-Phase Full Wave (Bridge) Rectifier

3-Phase Full Wave (Bridge) Rectifier

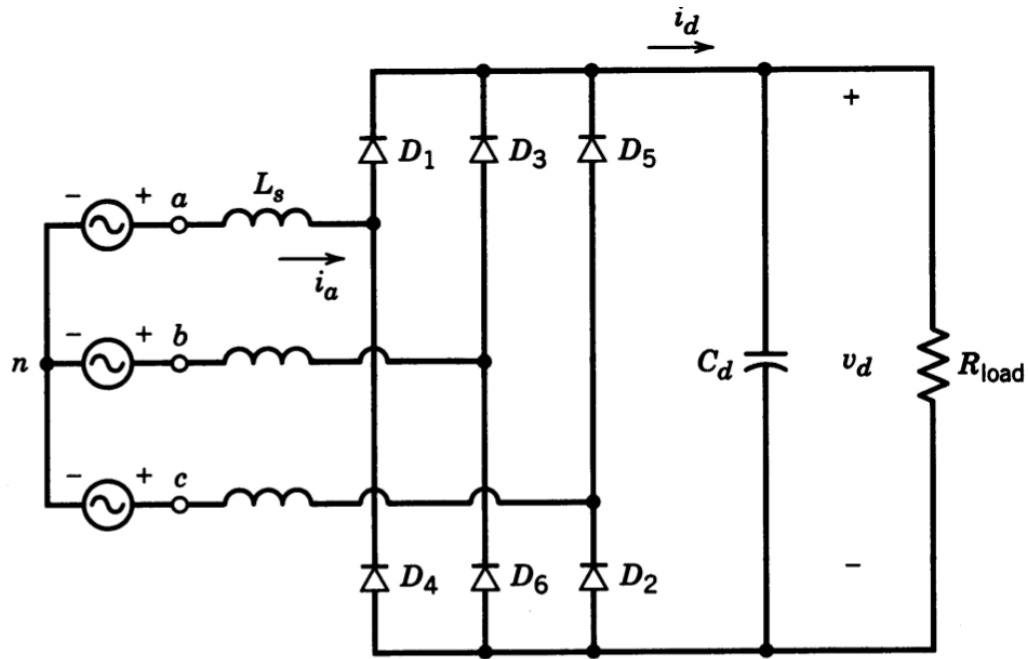


3-Phase Full Wave (Bridge) Rectifier

Ignore Ls and redraw

3-Phase Full Wave (Bridge) Rectifier

Ignore L_s and redraw

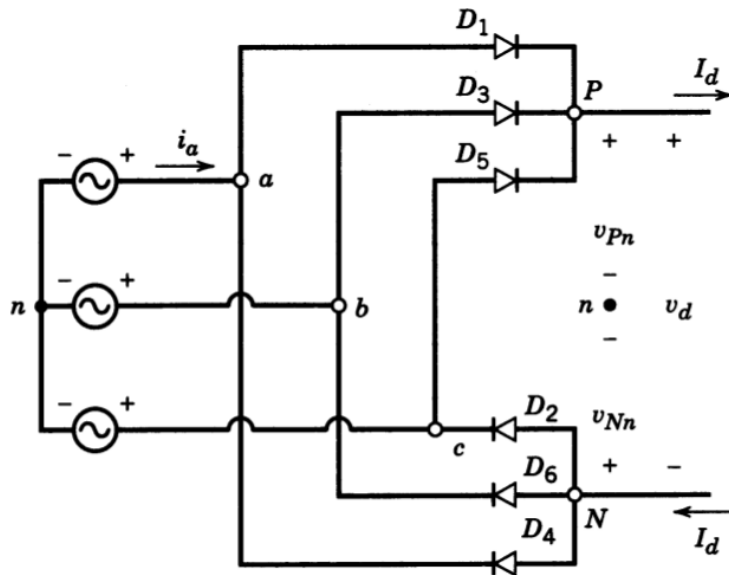


3-Phase Full Wave (Bridge) Rectifier

Can you draw the voltage and current waveforms?


3-Phase Full Wave (Bridge) Rectifier

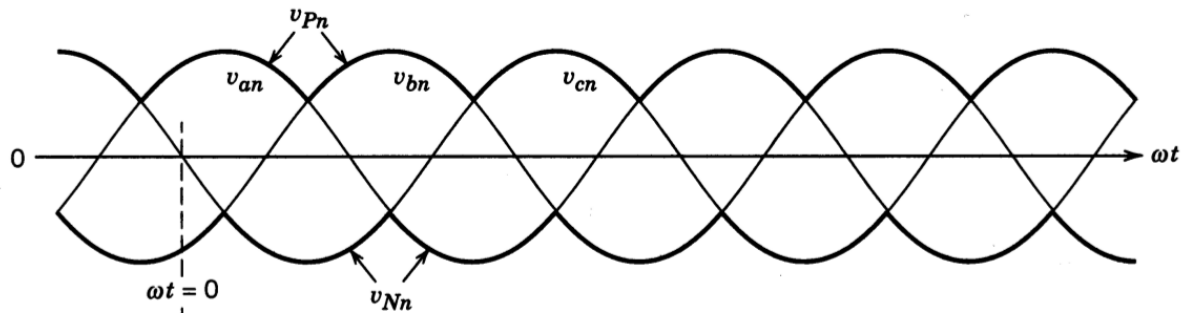Can you draw the voltage and current waveforms?



3-Phase Full Wave (Bridge) Rectifier

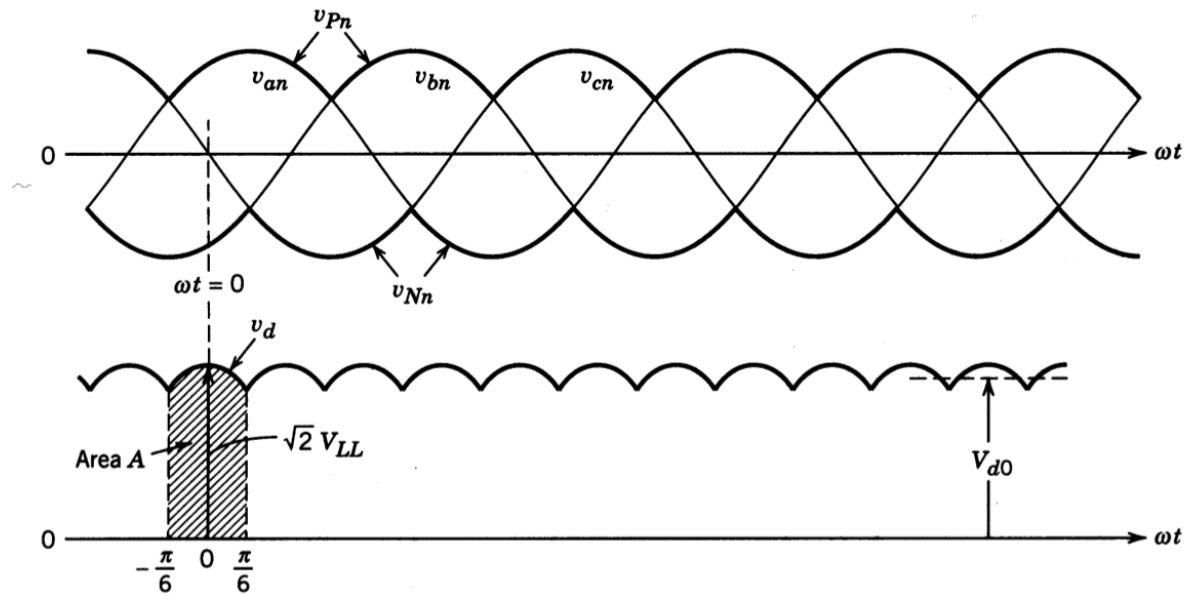Can you draw the voltage and current waveforms?



3-Phase Full Wave (Bridge) Rectifier

Average voltage?

3-Phase Full Wave (Bridge) Rectifier

Average voltage?: Twice of the half wave rectifier

$$V_{dc} = \frac{3\sqrt{6}}{\pi} V_{ph}$$

or

3-Phase Full Wave (Bridge) Rectifier

Average voltage?: Twice of the half wave rectifier

$$V_{dc} = \frac{3\sqrt{6}}{\pi} V_{ph}$$


or

$$V_{dc} = \frac{3\sqrt{2}}{\pi} V_{l-l} = 1.35 V_{l-l}$$

=540 Vdc for a 400 V grid

3-Phase Full Wave (Bridge) Rectifier

Output voltage waveforms

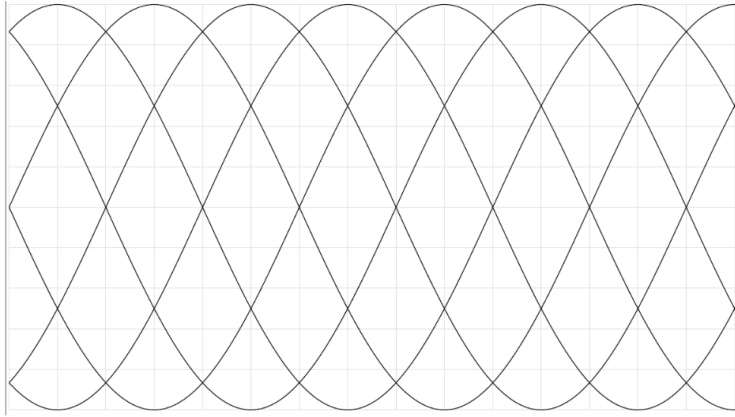


3-Phase Full Wave (Bridge) Rectifier

Output voltage waveforms

What about the current waveforms?

What about the current waveforms?


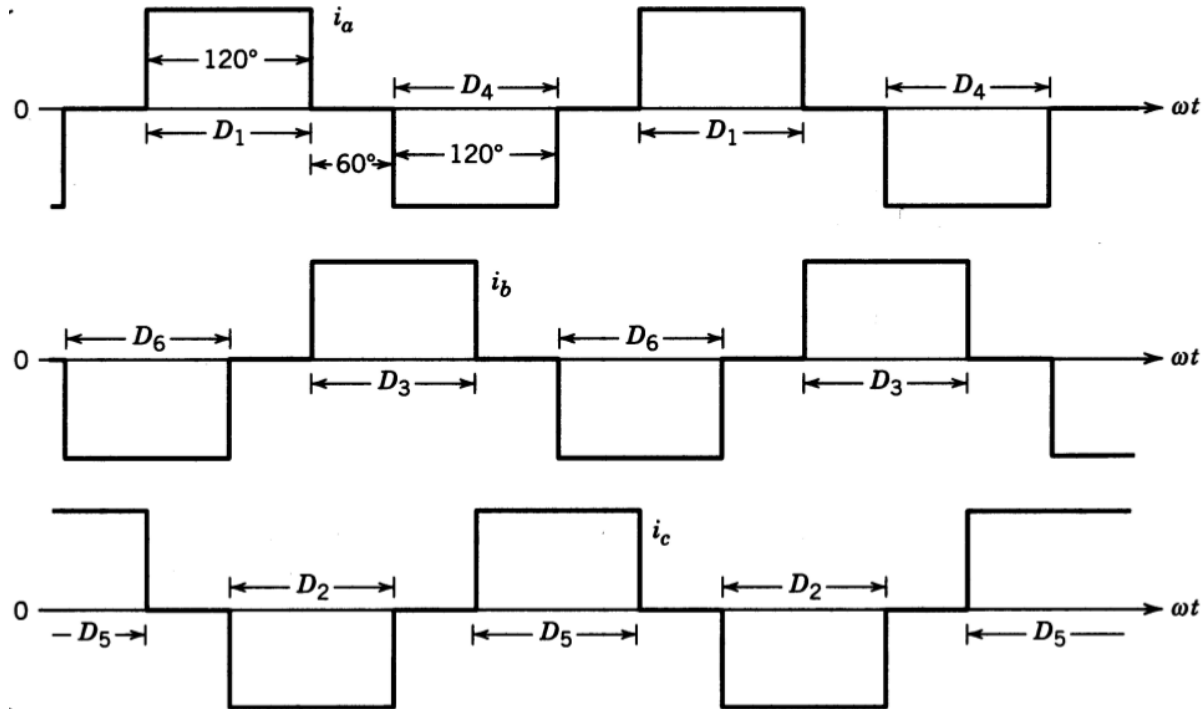


What about the current waveforms?

What are the differences wrt single phase?

What about the current waveforms?

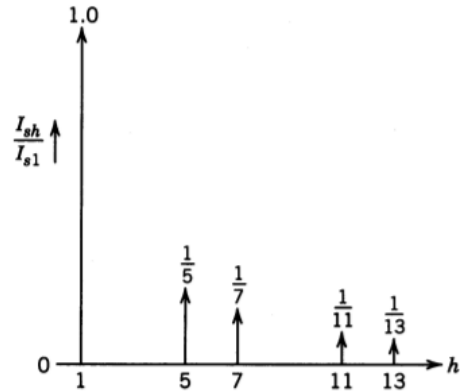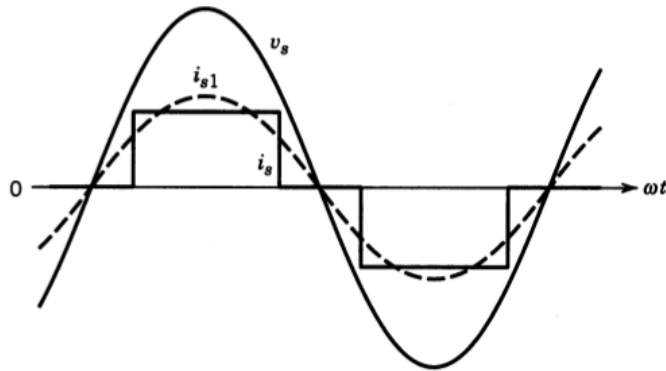What are the differences wrt single phase?




No 3rd order harmonics!

Comparison of Rectifiers



Type	Vout	ΔV_{out}	f_{ripple}
Single Phase	$\frac{2\sqrt{2}}{\pi} V_{ph} = 207 \text{ V}$	$\sqrt{2} V_{ph} = 325 \text{ V}$	100 Hz
3-phase Half Bridge	$\frac{3\sqrt{2}}{2\pi} V_{l-l} = 270 \text{ V}$	$\frac{\sqrt{2}}{2} V_{ph} = 162.5 \text{ V}$	150 Hz
3-phase Full Bridge	$\frac{3\sqrt{2}}{\pi} V_{l-l} = 540 \text{ V}$	$(1 - \frac{\sqrt{3}}{2}) \sqrt{2} V_{l-l} = 75.8 \text{ V}$	300 Hz

Commutation in 3-Phase Rectifiers

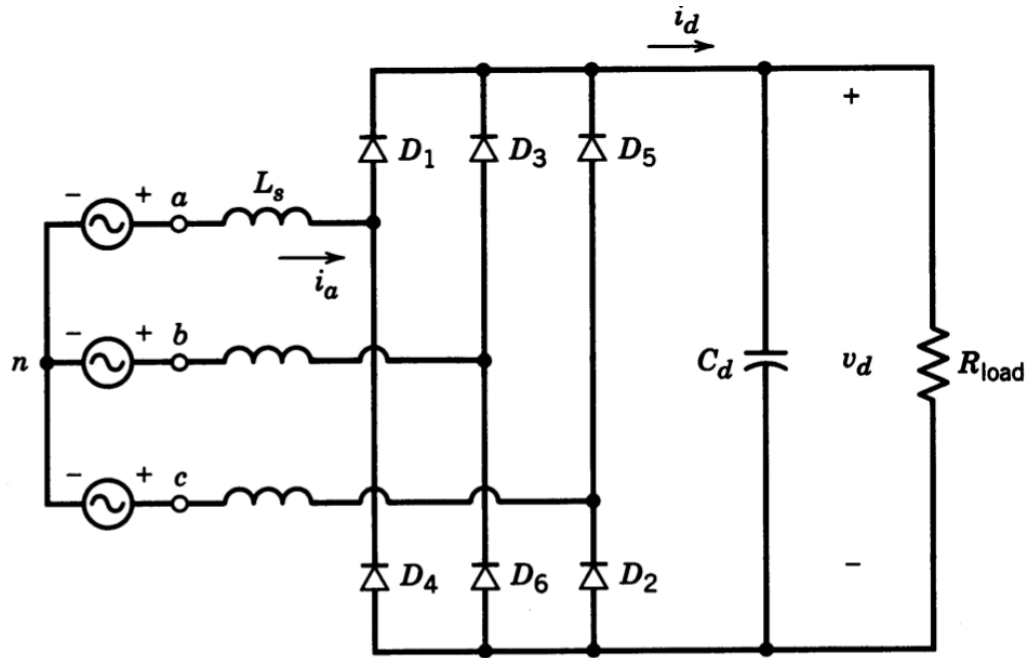


Commutation in 3-Phase Rectifiers

Commutation in 3-Phase Rectifiers

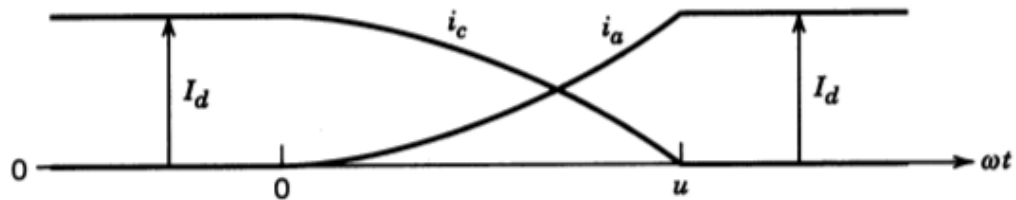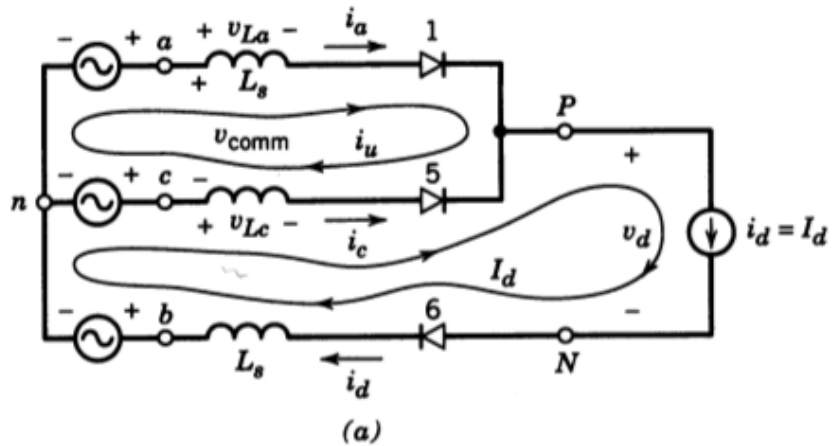

Commutation in 3-Phase Rectifiers

Commutation in 3-Phase Rectifiers

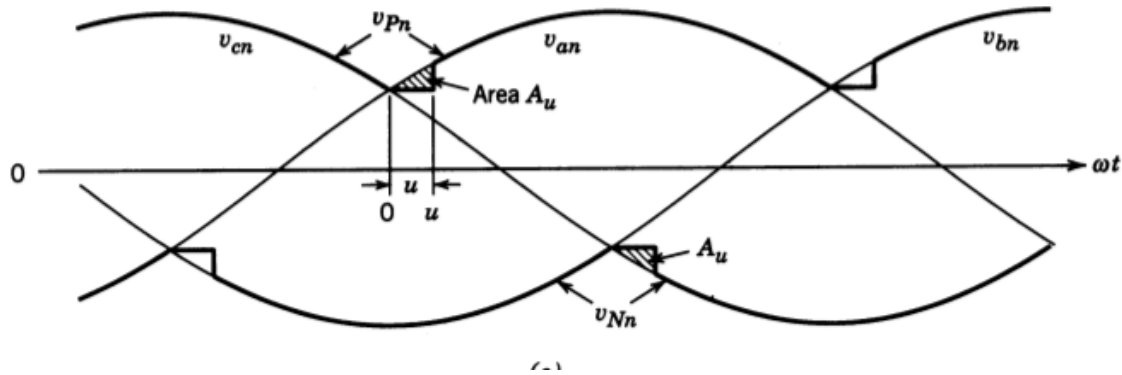

Average Voltage

Without Commutation

$$V_{dc} = \frac{3\sqrt{2}}{\pi} V_{l-l} = 1.35 V_{l-l}$$

Average Voltage

Without Commutation

$$V_{dc} = \frac{3\sqrt{2}}{\pi} V_{l-l} = 1.35 V_{l-l}$$

With Commutation

$$V_{dc} = \frac{3\sqrt{2}}{\pi} V_{l-l} - \frac{3}{\pi} \omega L_s I_d$$

[More info](#)

[Commutation Simulation](#), [MultiSim Simulation Examples](#)

You can download this presentation from:
keysan.me/ee463.