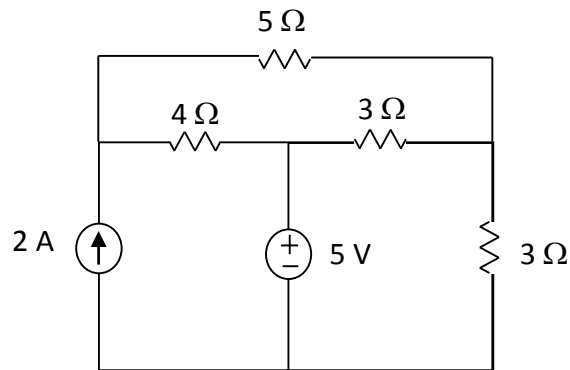


## HOMEWORK II


**Question 1** Consider the circuit below.



- Obtain the node equation in matrix form.
- Solve the node equation, and determine the branch voltages and currents.
- Obtain the mesh equation in matrix form.
- Solve the mesh equation, and determine the branch currents and voltages.
- Determine the powers delivered to/supplied by the branches. Verify that the power is conserved.
- Suppose that only the current through the 5 V battery is required. Transform the upper  $\Delta$  connected resistors to the equivalent Y connected resistors, solve the simple circuit (just one node equation), and determine the required current.

*Answer Part (f) 2/3 A.*

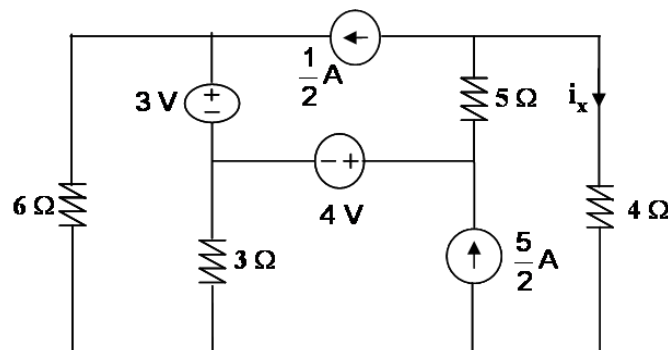**Question 2** Consider the circuit below.




- Obtain the node equation in matrix form.
- Solve the node equation, and determine the branch voltages and currents.
- Obtain the mesh equation in matrix form.

- d) Solve the mesh equation, and determine the branch currents and voltages.
- e) Determine the powers delivered to/supplied by the branches.  
Verify that the power is conserved.
- f) Find the current  $i_x$  by superposition.


Answer Part (f)  $i_x = 0.5 \text{ A}$ .

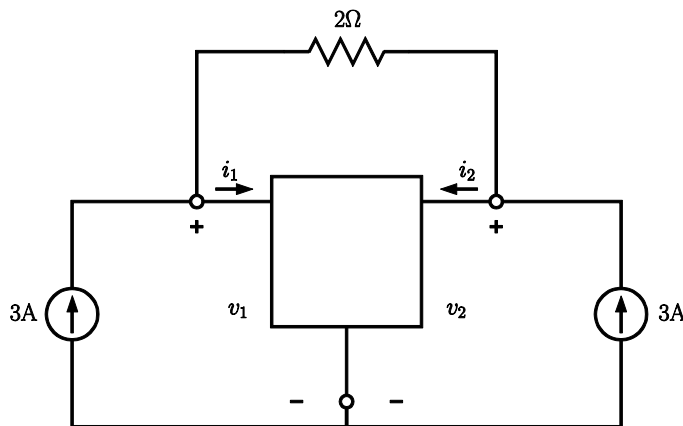**Question 3** For the following circuit, find the powers delivered to/supplied by the elements. Is the 3-T two-port passive or active? Explain.




$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 2 & 4 \\ -4 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

**Question 4** The circuit element AVG is introduced in Figure 1. For the circuit given in Figure 2, find the node voltages, the current  $i$ , and the powers delivered to/supplied by the elements.

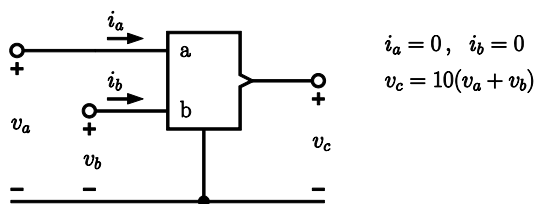

**Figure 1** The circuit element AVG.

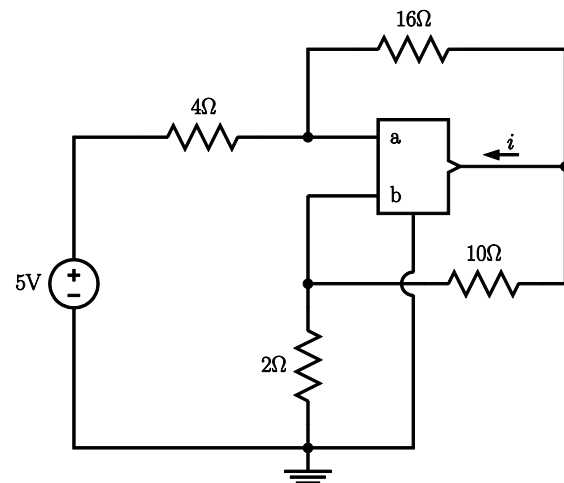

**Figure 2** The circuit for Question 4.

Answer  $i = 2.25 \text{ A}$ .