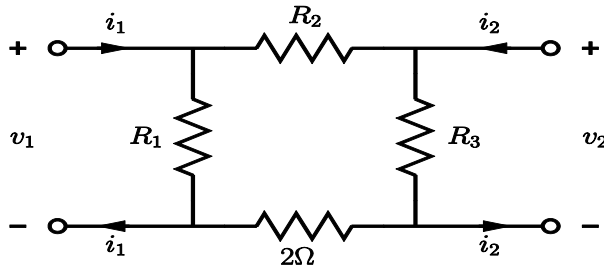


HOMEWORK IV

Question 1 For the following two port, the hybrid parameters are given as:


$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 4 & 1/2 \\ \alpha & 1/8 \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$




- a) Find α .
- b) Find $R_1, R_2,$ and R_3 .

Question 2

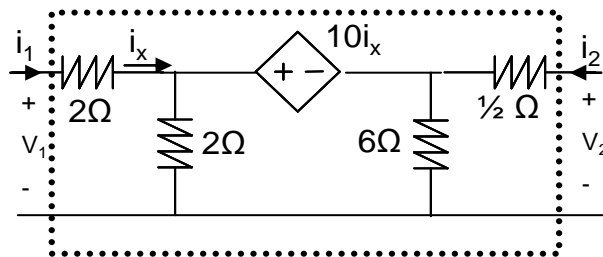- a) Obtain the resistance parameters for the following two-port circuit.



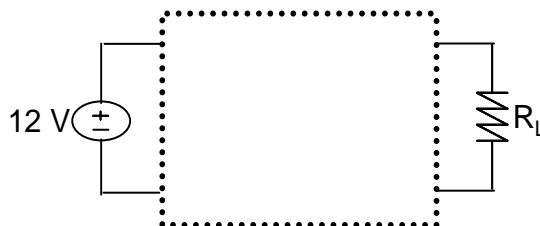
- b) The two port shown in Part (a) is used in the following configuration. Determine R_L so that the power absorbed by R_L has the maximum value. Also compute this power.



Answer (b) $R_L = 3.5\ \Omega, P_L = 72/7\ \text{W}$.

Question 3

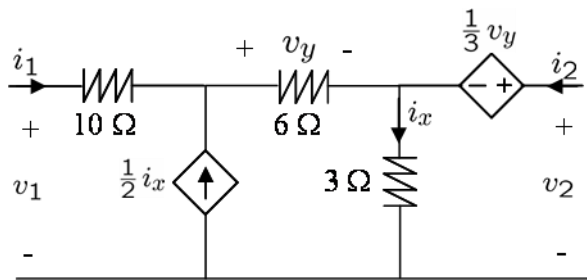- a) Obtain the hybrid parameters for the following two-port circuit.




$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

- b) Using the hybrid representation, find the power input to the two-port circuit given $v_1 = 8 \text{ V}$ and $i_2 = -4 \text{ A}$.
- c) Let $v_1 = 8 \text{ V}$ and $i_2 = -4 \text{ A}$. Solve the circuit, determine the powers supplied/absorbed by the elements, and verify the result of Part (b).


Answer (b) 64 W.

Question 4

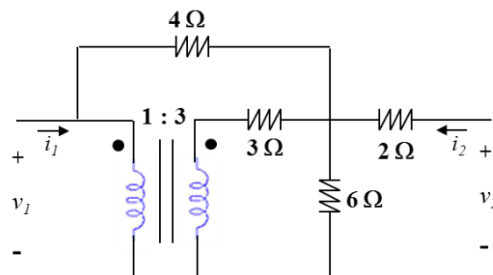- a) Obtain the conductance (short circuit) and transmission parameters for the following two-port circuit.



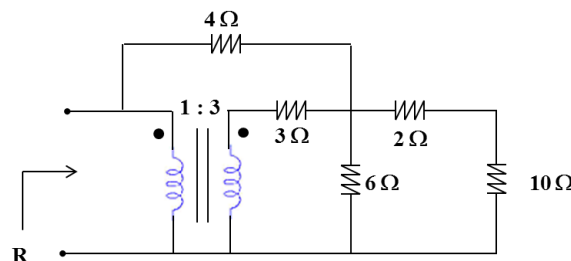
- b) The secondary port is terminated with a 10 ohm resistor as shown below. Find the input resistance R by driving the port terminals with a test source.



- c) Find R using the short circuit representation of the two-port circuit.
- d) Find R using the transmission representation of the two-port circuit.

Answer (b) $R = 8/11 \Omega$.

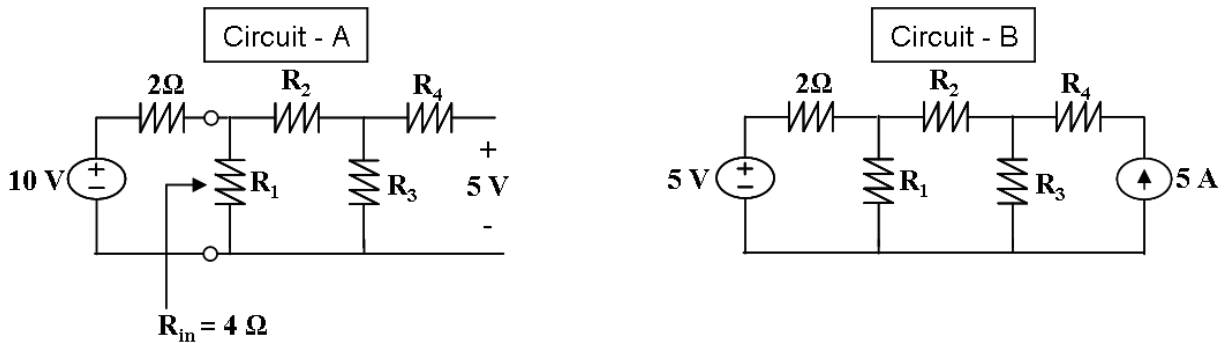
Question 5 Consider the circuits A and B given below.



Find the power supplied/absorbed by the 5 V source in Circuit - B.

Answer $25/3$ W, absorbed.

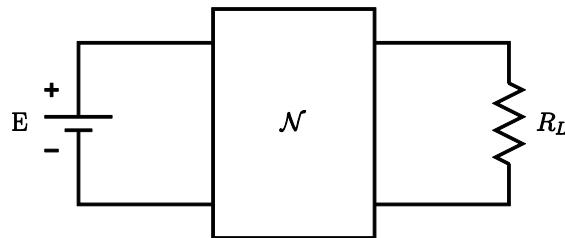Question 6 Consider the following circuit where the two-port circuit \mathcal{N} contains only passive LTI resistors and ideal transformers. R_L is a passive load resistor. The power supplied by the source is denoted by P_s , and the power delivered to the load is denoted by P_L .





The measurement results of two experiments are given in the table below.

	R_L	P_s	P_L
Exp. #1	3Ω	16 W	P_o
Exp. #2	12Ω	14 W	P_o


- Find P_o . (Hint: Tellegen's theorem.)
- What is the value of R_L that maximizes P_L ?
- Suppose that a third experiment with the R_L value found in Part (b) is performed. What will P_L and P_s be in this case?
- Obtain the short circuit parameters for \mathcal{N} in terms of E . Determine a set of suitable E values. Assign a value to E and design \mathcal{N} .

Answer (a) $P_o = 4/3$ W, (b) $R_L = 6 \Omega$, (c) $P_L = 1.5$ W, $P_s = 15$ W.

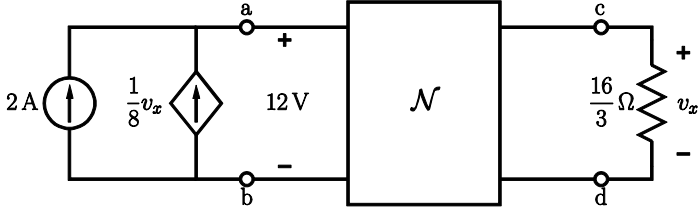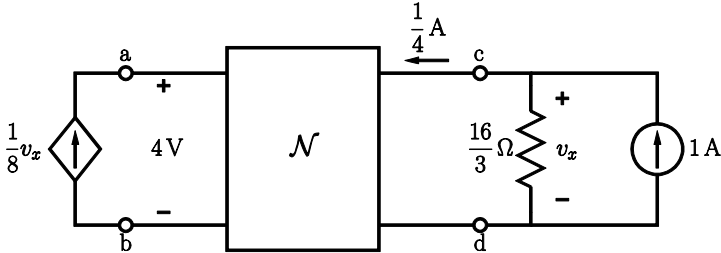Question 7 Consider the circuits below where the two-port \mathcal{N} contains only LTI resistors and ideal transformers.



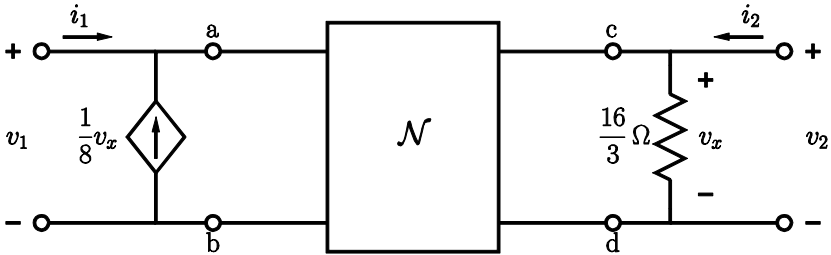- a) Find the value of v_x in the circuit that is driven by the 2A current source.
- b) Obtain the resistance parameters for the below two-port circuit.



$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

- c) Given $i_1 = -2 \text{ A}$ and $i_2 = 4 \text{ A}$, find the power input to the two-port \mathcal{N} .
- d) Obtain the resistance parameters for the two-port \mathcal{N} .

Answer (a) $v_x = 4 \text{ V}$, (c) 19 W .