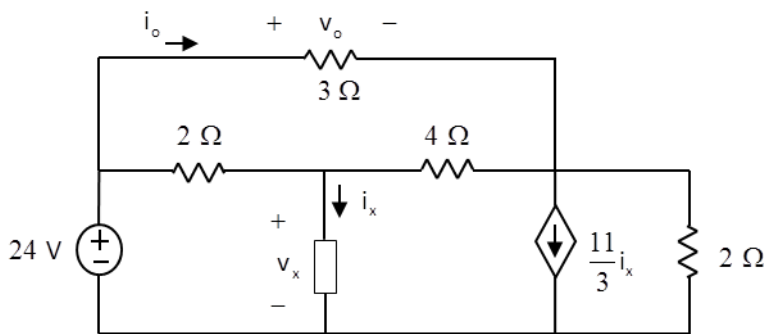


HOMWORK V



Question 1 Find the current i_o in the circuit below.



$$i_x = \begin{cases} \frac{3}{8}v_x^2, & v_x \geq 0 \\ 0, & v_x < 0 \end{cases}$$


Answer $i_o = 12 \text{ A}$.

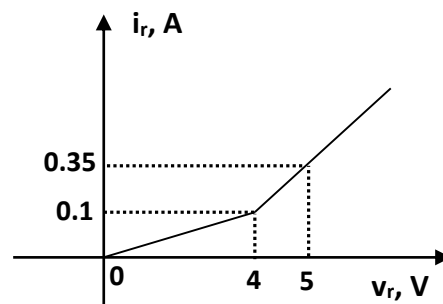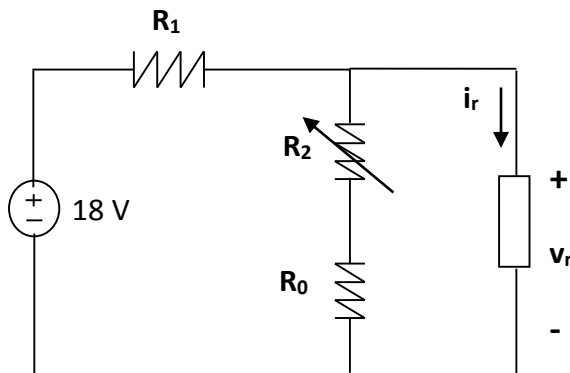Question 2 In the circuit given below, the resistor R_2 can take any value in the range $[0, +\infty]$. Determine the R_1 and R_0 values so that the current through the nonlinear element is limited to the range $100 \text{ mA} \leq i_r \leq 600 \text{ mA}$ whatever the R_2 value is.



Answer $R_1 = 20 \Omega$, $R_0 = 20/3 \Omega$.

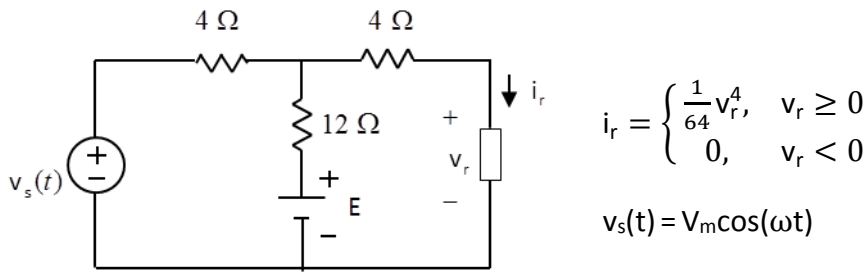
Question 3 Consider the circuit given below.




Given $v_r(t) \cong 2 + 0.15 \cos(\omega t)$ V, find E and V_m .

Answer $E = 15$ V, $V_m = 0.9$ V.

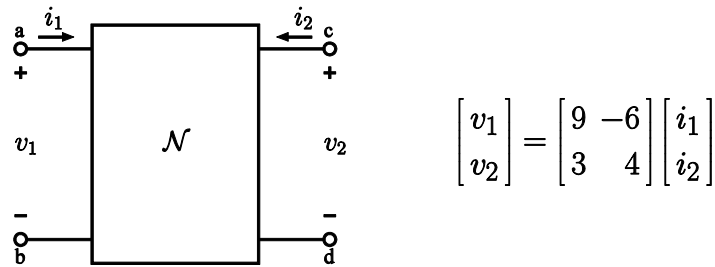Question 4 Consider the following two-port circuit.




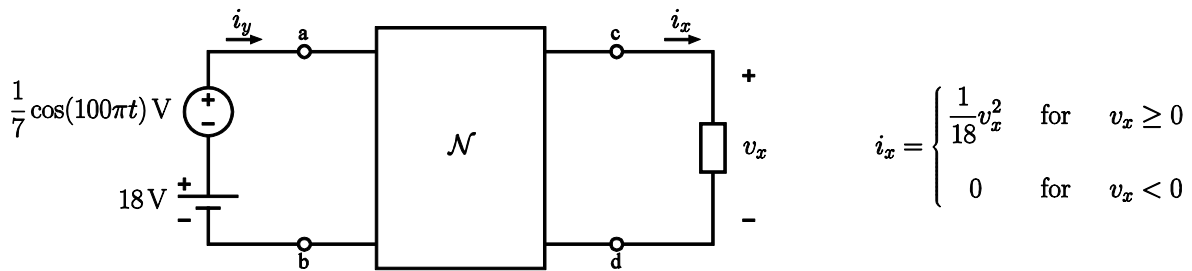Find (approximately) the current $i_y(t)$ in the below circuit.




Answer $i_y(t) \cong (5/3) + (1/81) \cos(100\pi t)$ A.

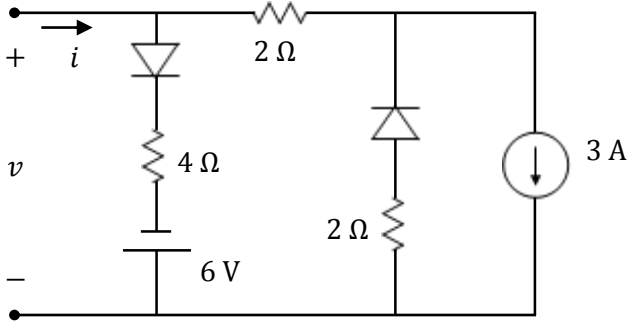
Question 5 Given the following one-port circuit with ideal diodes, obtain and sketch the port, i.e. the i - v , characteristic.



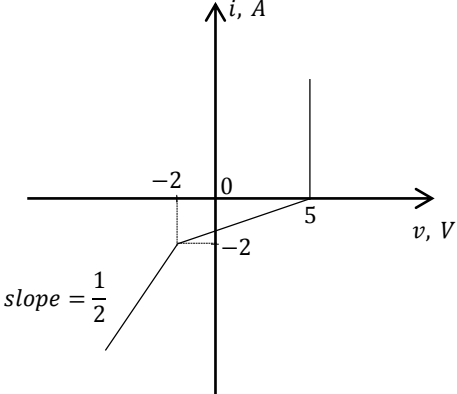Question 6 Design one-port circuits realizing the given i - v characteristics. The available elements are LTI passive resistors, constant independent sources, and ideal diodes.



(a)

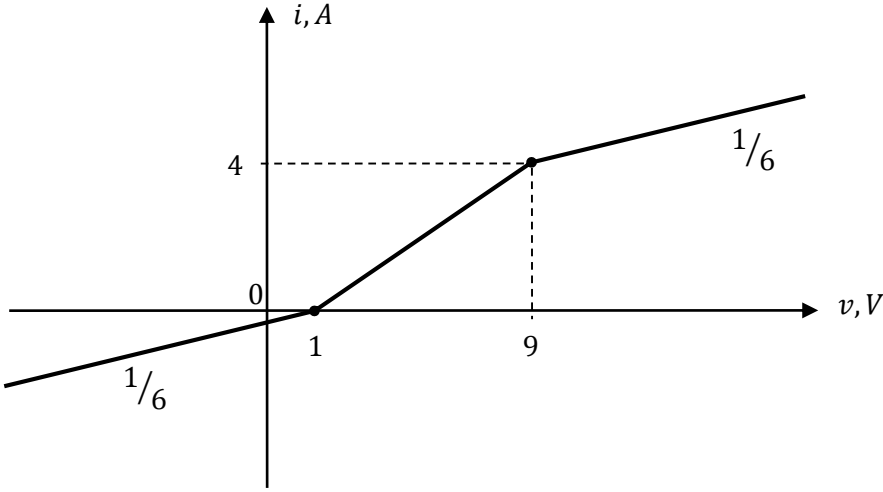

(b)