

HOMEWORK II


Question 1. Given the state equation of an LTI dynamic circuit,

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \\ \dot{x}_3(t) \end{bmatrix} = \begin{bmatrix} 1 & -1 & 0 \\ 2 & 4 & 5 \\ -2 & -2 & -3 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \\ x_3(t) \end{bmatrix}$$

- a) Find the natural frequencies of the circuit.
- b) Determine real initial values $x_1(0), x_2(0),$ and $x_3(0)$ so that $x_1(t), x_2(t),$ and $x_3(t)$ are bounded for $t \geq 0$.
- c) For the initial values determined above, find $x_1(t), x_2(t),$ and $x_3(t)$ for $t \geq 0$.

Ans: (a) $s_1 = 2, s_2 = j, s_3 = -j$.
 (b) (i) $x_1(0) = a/2, x_2(0) = a, x_3(0) = -a; a \in R$;
 (ii) $x_1(0) = b/2, x_2(0) = 0, x_3(0) = 0; b \in R$;
 The answer is any vector that can be expressed as a linear combination vectors shown in parts (i) and (ii), that is $x_1(0) = (a + b)/2, x_2(0) = a, x_3(0) = -a; a \in R, b \in R$.


Question 2. Consider the circuit below.

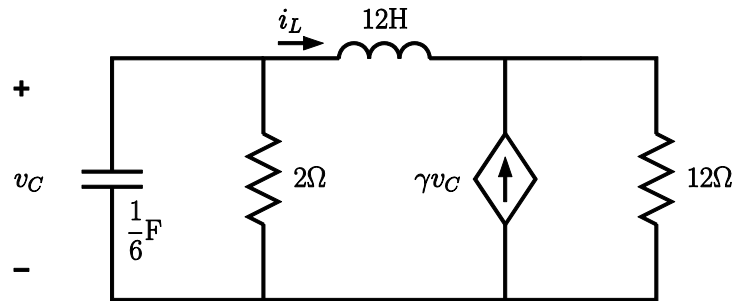

- a) Obtain the state equation.
- b) Given $v_C(t) = (K_1 + K_2 t)e^{\lambda t}$, find λ and γ .
- c) Let $\gamma = \frac{17}{12}$ mho.
 - i. Find the natural frequencies of the circuit.
 - ii. Find suitable initial conditions $i_L(0)$ and $v_C(0)$ such that the energy delivered to the 2Ω resistor over the time interval $[0, \infty)$ is 5 J.

Ans: (b) $\lambda = -2, \gamma = -1/12$ mhos.
 (c) (i) $s_1 = 1, s_2 = -5$.
 (ii) $v_C(0) = 10 V, i_L(0) = 10/3 A$; or $v_C(0) = -10 V, i_L(0) = -10/3 A$.


Question 3. Consider the circuit below.

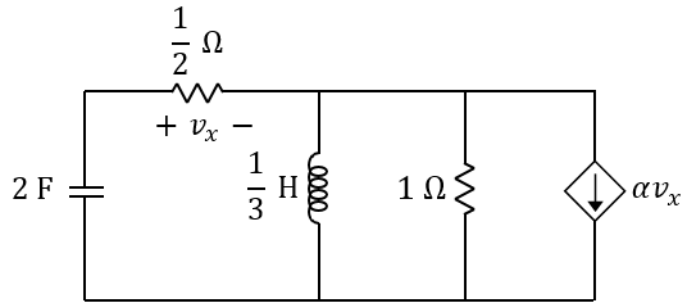

- Let $\alpha \neq 3$. Obtain the state equation.
- Find α if one of the natural frequencies is at -3 . Find the other natural frequency.
- Find the range of α values to guarantee the stability of the circuit.
- What happens if $\alpha = 3$?

Ans: (b) $\alpha = 2 \text{ mhos}$, $s_2 = -1$.
 (c) $\alpha < 3 \text{ mhos}$.
 (d) Single state variable, $v_C = -i_L$.

Question 4. Consider the circuit below.

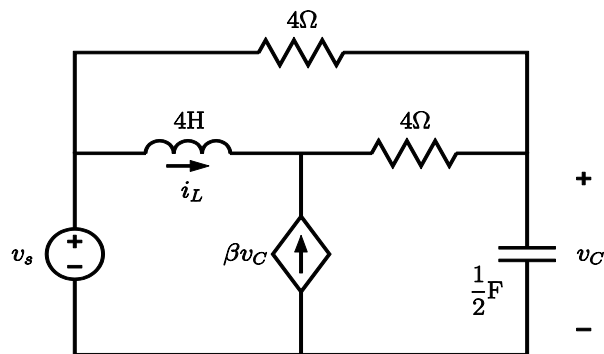


- Obtain the state equation.

For the following parts, take $v_s(t) = 0$.

- Let $\beta = 2 \text{ mho}$ and $v_C(0) = 4 \text{ V}$. Find $i_L(0)$ so that only a single mode is excited.
- Given $v_C(t) = \cos(\omega t) \text{ V}$, determine β and ω and find $i_L(t)$.

Ans: (b) $i_L(0) = -6 \text{ A}$ or $i_L(0) = -3 \text{ A}$.
 (c) $\beta = 0.75 \text{ mhos}$, $\omega = 1 \text{ rad/sec}$.


Question 5. Consider the circuit below.

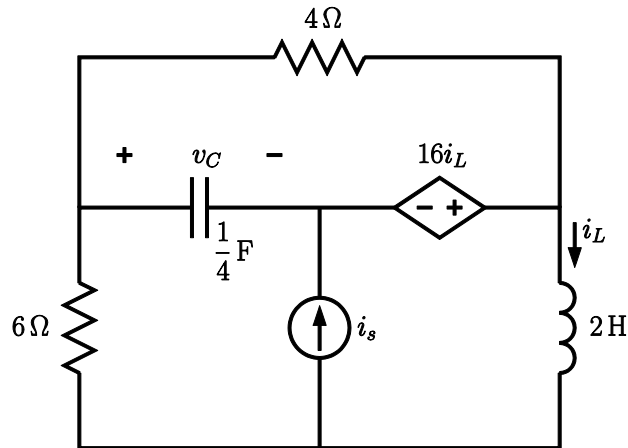

- Obtain the state equation.
- Find the natural frequencies of the circuit.
- Obtain the state transition matrix.
- Given $i_s(t) = 10e^{-t}$ A, find the particular solutions for $v_C(t)$ and $i_L(t)$.

Ans: (b) $s_{1,2} = 2 \pm j$.
 (d) $i_{Lp}(t) = 2e^{-t}$ A.


Question 6. Consider the circuit below.

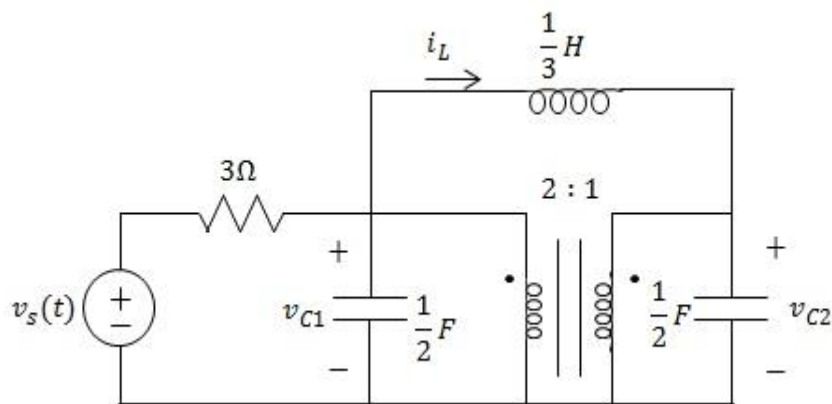

- Obtain the state equation.
- Find the natural frequencies of the circuit.
- Given $v_s(t) = 18$ V, find the particular solutions for $v_{C1}(t)$, $v_{C2}(t)$, and $i_L(t)$.
- Solve part (c) by studying the DC steady-state of the system. Does steady-state exist?

Ans: (b) $s_{1,2} = -4/15 \pm j\sqrt{254}/15$.
 (c) $v_{C1p}(t) = 0$, $i_{Lp}(t) = 12$ A.


Question 7. Consider the circuit below.

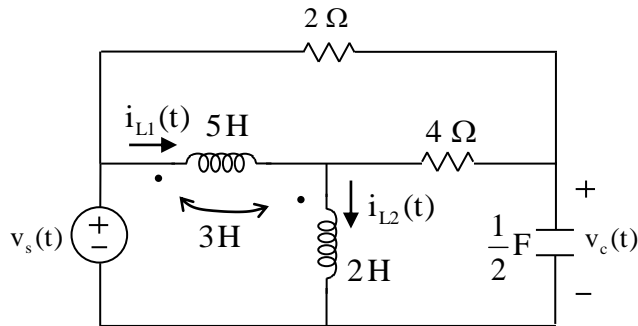

- Obtain the state equation.
- Find the natural frequencies of the circuit.
- What are the observed natural frequencies of the circuit for the branch variables $v_c(t)$, $i_{L1}(t)$, and $i_{L2}(t)$?

Ans: (b) $s_1 = 0$, $s_{2,3} = -53/2 \pm \sqrt{2497}/2$.
 (c) v_c : s_2, s_3 ; i_{L1} , i_{L2} : s_1, s_2, s_3 .


Question 8. Consider the circuit below.

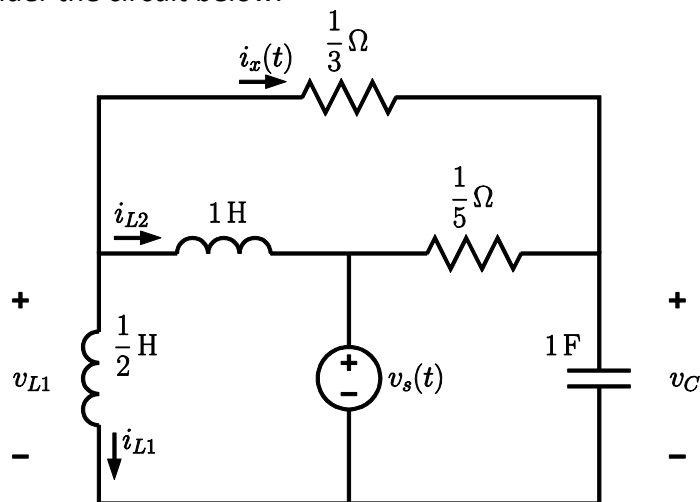

- Obtain the state equation.
- Find the natural frequencies of the circuit.
- Let the initial values of dynamic elements be specified. Write the forms of the zero-input solutions (do not determine the coefficients) for $v_c(t)$, $i_{L2}(t)$, $v_{L1}(t)$, and $i_x(t)$.
- Given $v_s(t) = 9e^{-t}$ V, find the particular solutions for $v_c(t)$, $i_{L1}(t)$, $i_{L2}(t)$, $v_{L1}(t)$, and $i_x(t)$.

Ans: (b) $s_1 = 0$, $s_2 = -2$, $s_3 = -4$.
 (d) $i_{x_p}(t) = -33e^{-t}$ A

Question 9. Consider the circuit below.

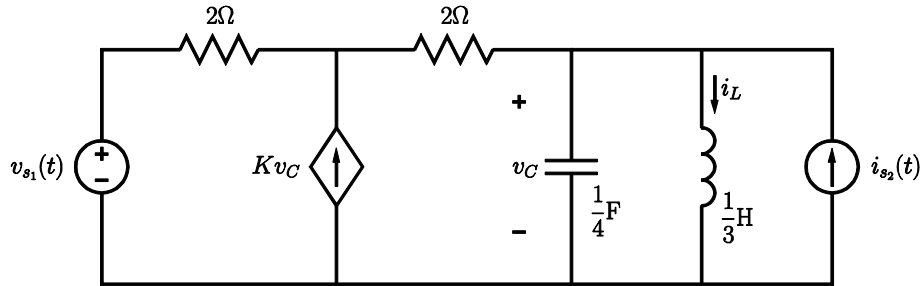

- a) Obtain the state equation.
- b) Express the natural frequencies in terms of K .
- c) Determine the value of K so that the natural frequencies are purely imaginary. For this value of K , obtain the state transition matrix.
For the following parts, take $K = 4$.
- d) Find the natural frequencies of the circuit.
- e) Obtain the state transition matrix.
- f) Find the zero-input solution given $v_C(0) = 7 \text{ V}$, $i_L(0) = 4 \text{ A}$.
- g) Given $v_{s1}(t) = 8 \text{ V}$ and $i_{s2}(t) = 3e^{6t} \text{ A}$,
 - i. Find the particular solution, $\underline{x}_p(t)$.
 - ii. Find the zero-state solution.
 - iii. Determine the initial state $\underline{x}(0)$ so that $\underline{x}(t) = \underline{x}_p(t)$ for $t \geq 0$.
- h) Given $v_{s1}(t) = 0$ and $i_{s2}(t) = e^{4t} \text{ A}$, find the zero-state solution.

Ans: (c) $K = 0.5 \text{ mhos}$.

(d) $s_1 = 4$, $s_2 = 3$.

(f) $v_{C_{zi}}(t) = 12e^{4t} - 5e^{3t} \text{ V}, t \geq 0$.

(g) (i) $i_{L_p}(t) = 2 + 6e^{6t} \text{ A}$.

(ii) $i_{L_{zs}}(t) = -12e^{4t} + 4e^{3t} + 2 + 6e^{6t} \text{ A}$.

(iii) $v_C(0) = 12 \text{ V}$, $i_L(0) = 8 \text{ A}$.

(h) $v_{C_{zs}}(t) = -12e^{4t} + 16te^{4t} + 12e^{3t} \text{ V}, t \geq 0$.