

EE-464 STATIC POWER CONVERSION-II

DC/DC Converters Continued

Ozan Keysan

keysan.me

Office: C-113 • Tel: 210 7586







Slobodan Ćuk

[Linked-in profile](#)

Ćuk converter

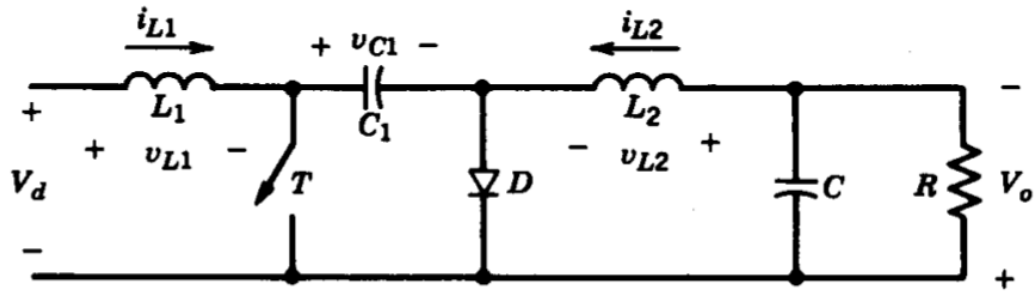


Cuk converter

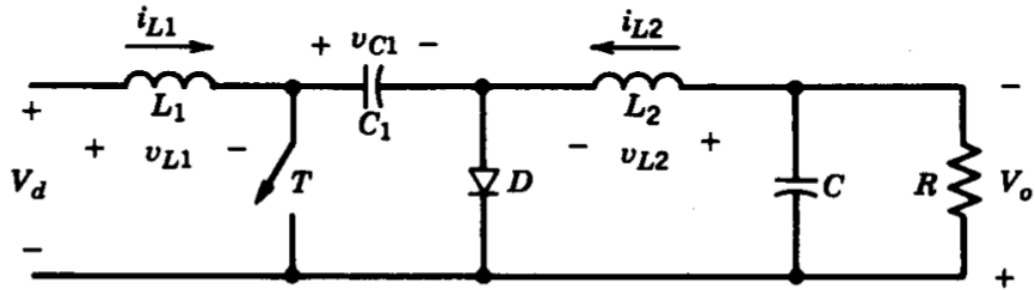

Supplies a negative voltage


Cuk converter

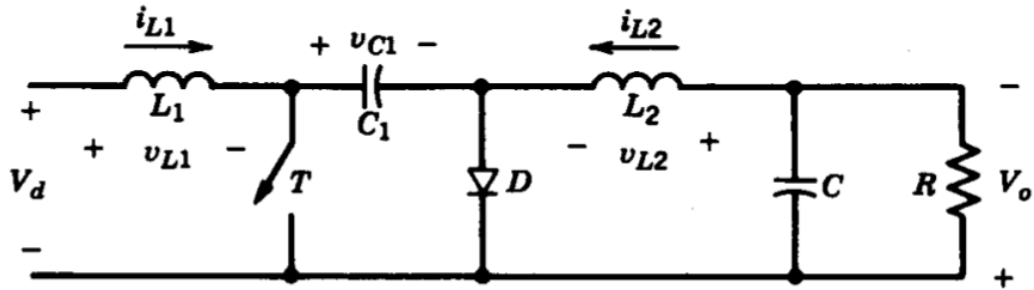

Supplies a negative voltage

Reduced EMI and bi-directional power flow

Cuk converter

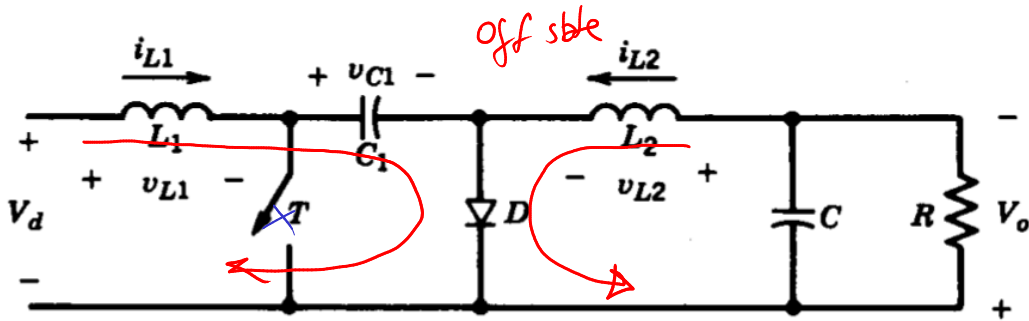


Supplies a negative voltage

Reduced EMI and bi-directional power flow

C_1 is the primary energy storage element (should be large)

Cuk converter

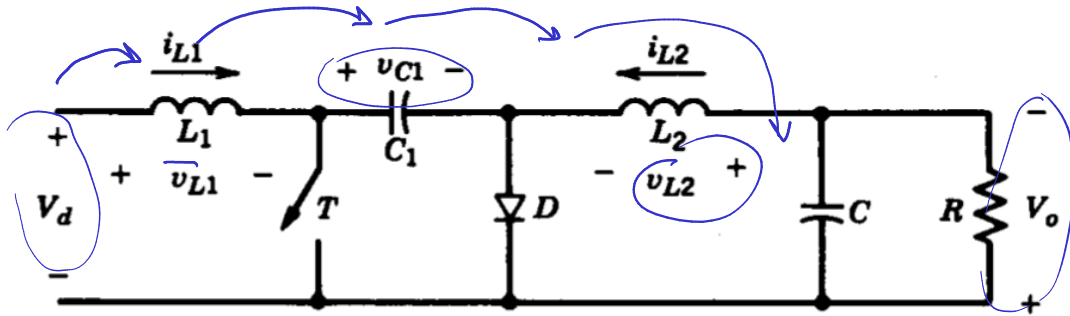


Can you plot the on & off states?

on average $\Rightarrow V_{L1} = 0$, $V_{L2} = 0$

$$V_{C1} = V_d - (-V_o) \Rightarrow \boxed{V_{C1} = V_d + V_o}$$

$$V_{C1} > V_d$$
$$V_{C1} > V_o$$

ON State

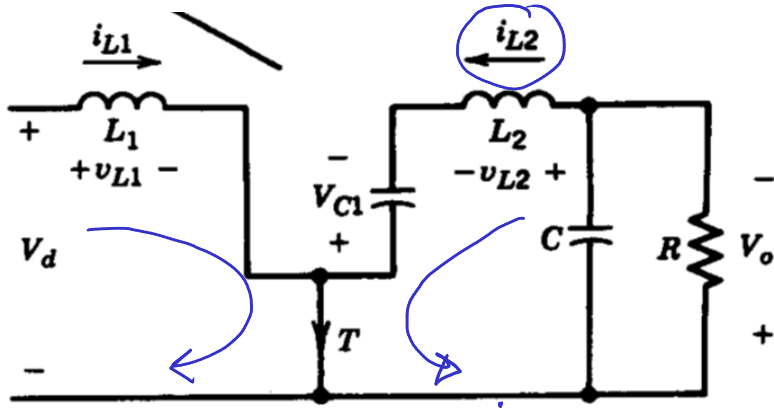


L_1 is charging with V_d

$L_2 \Rightarrow V_{C1} + V_o$




ON State

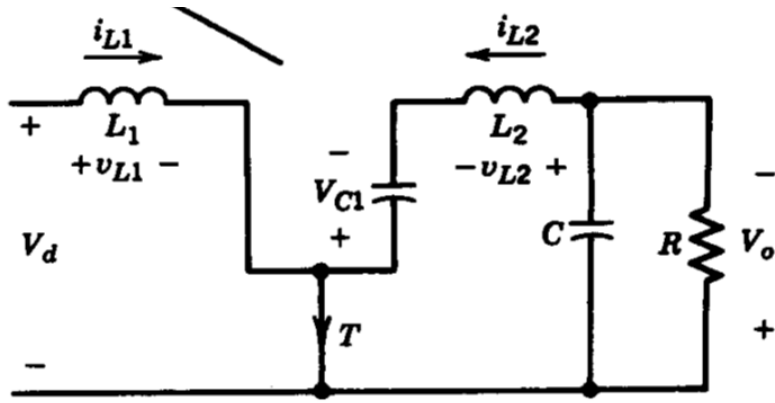

Diode off (reverse biased by C_1)


ON State

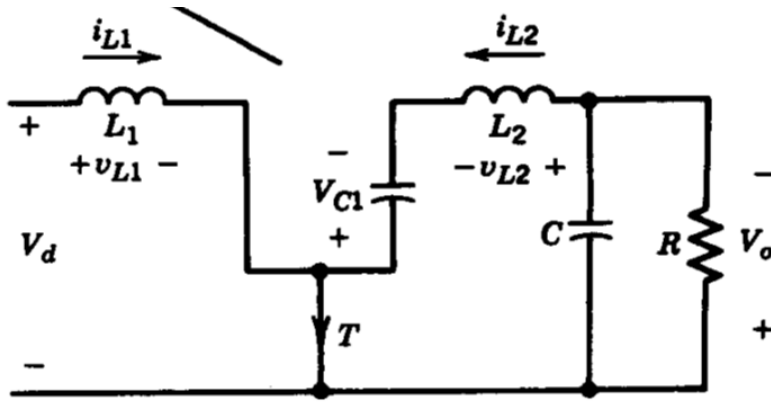

Diode off (reverse biased by C_1)

i_{L1} and i_{L2} passes through T_1

ON State

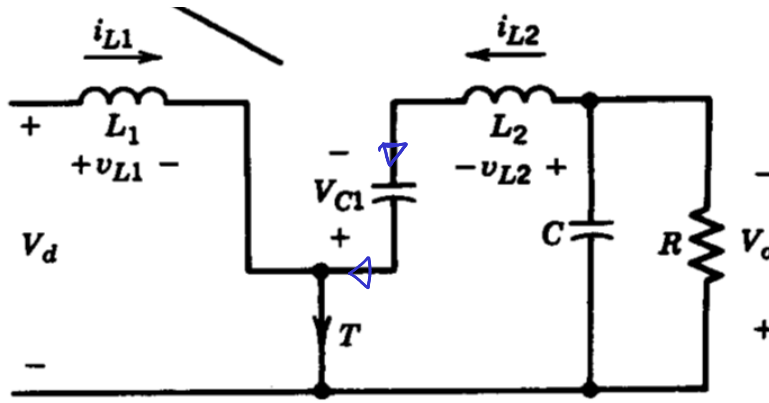


Diode off (reverse biased by C_1)

i_{L1} and i_{L2} passes through T_1

C_1 discharges through T_1 (V_{C1} $>$ V_o)


OFF State

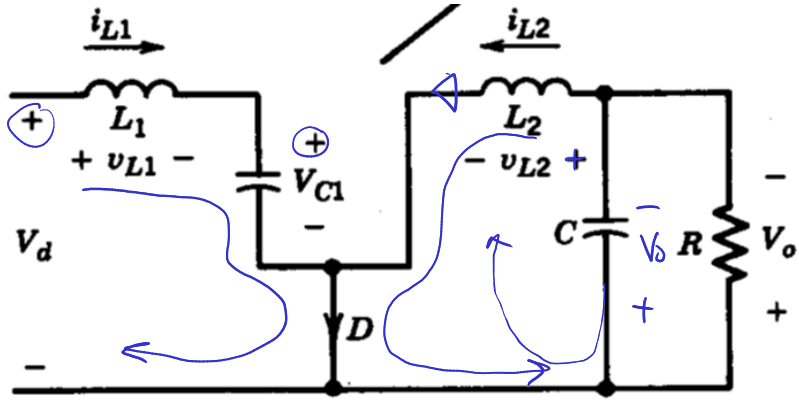


$V_{c1} > V_d$

$V_{L1} = V_d - V_{c1}$
 negative


i_{L1} decreases

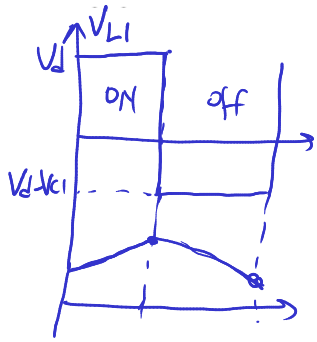

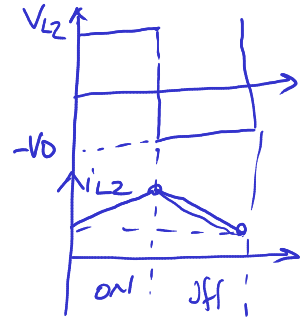$V_{L2} = -V_o \Rightarrow i_{L2}$ is decreasing




OFF State

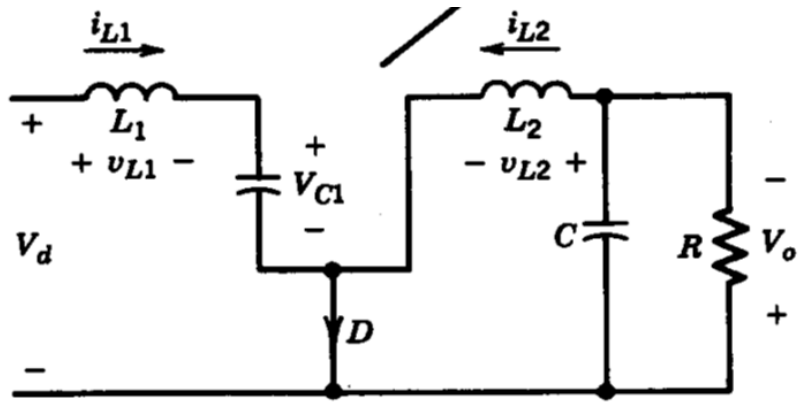

Diode on


OFF State

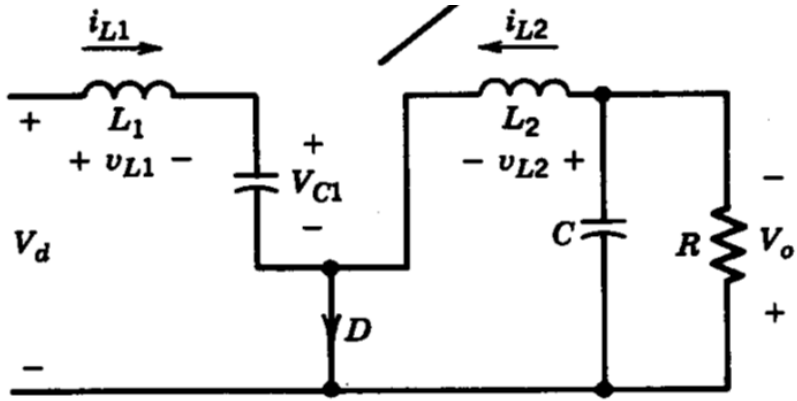

Diode on

i_{L1} decreases ($V_{C1} > V_d$)

OFF State


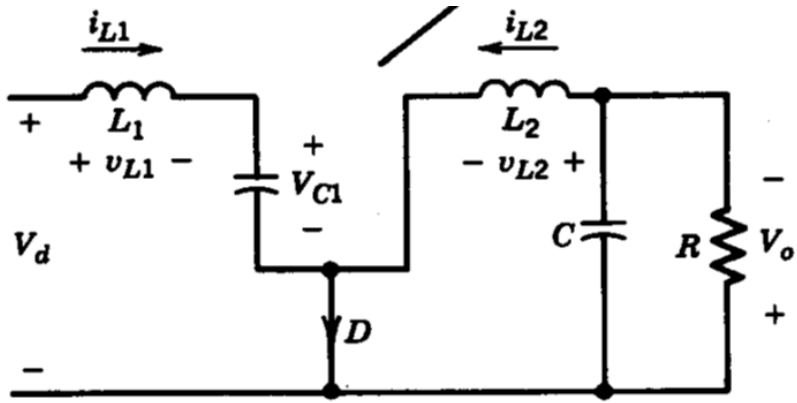


Diode on

i_{L1} decreases ($V_{C1} > V_d$)

$C1$ charges through $D1$ (from input and $L1$)

Operating States

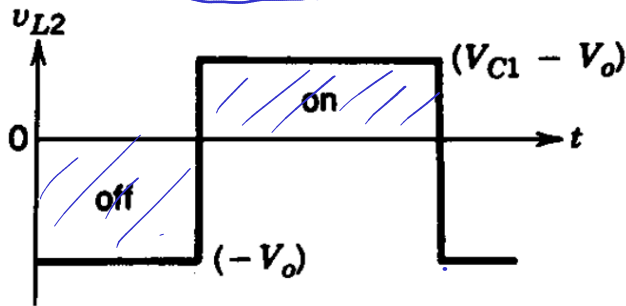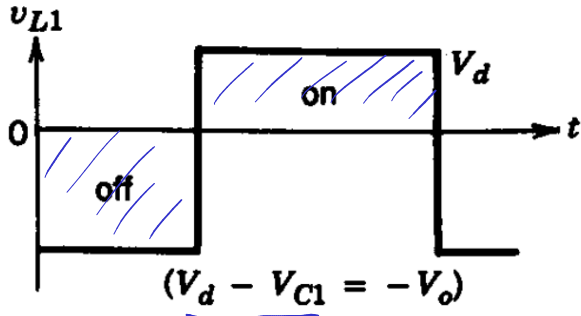

$$V_{C1} > V_o$$

$$\frac{L_1}{s} \left[V_d \cdot D \cdot \frac{1}{s} + (V_d - V_{C1}) \cdot (1-D) \cdot \frac{1}{s} \right] = 0$$

$$V_d \cdot D \cdot \frac{1}{s} + V_d - V_{C1} - D \cdot V_d + D \cdot V_{C1} = 0$$

$$V_{C1} = \frac{V_d}{1-D}$$

L_2 :

$$(V_{C1} - V_o) \cdot D \cdot \frac{1}{s} + (-V_o) \cdot (1-D) \cdot \frac{1}{s} = 0$$

$$V_{C1} \cdot D - V_o \cdot D - V_o + V_o \cdot D = 0$$


$$V_{C1} = \frac{V_o}{D}$$

Buck-boost converter

$$\frac{V_d}{1-D} = \frac{V_o}{D} \Rightarrow$$

$$V_o = \left(\frac{D}{1-D} \right) \cdot V_d$$

Operating States

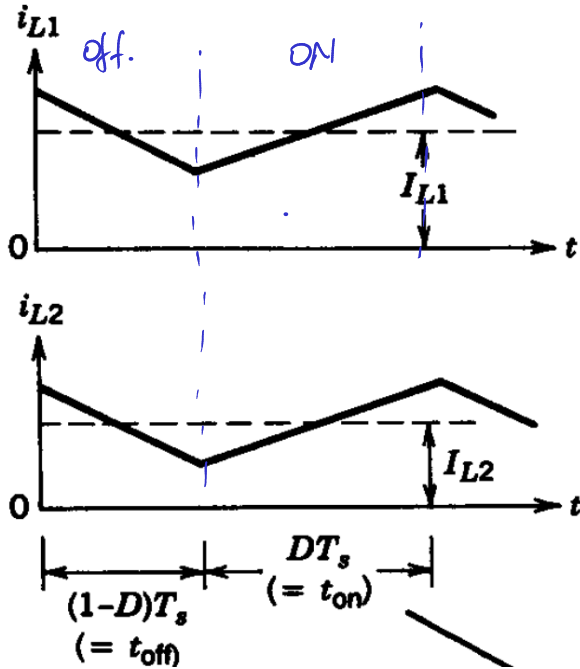


Cuk converter


$$V_o = \frac{D}{(1 - D)} V_d$$

It is a buck-boost converter!


Input/Output Ripple?

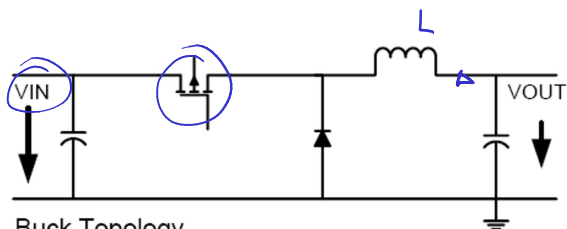




Buck Topology

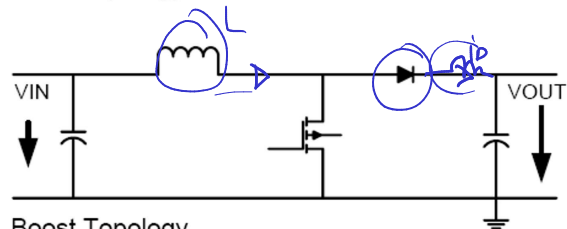


Boost Topology

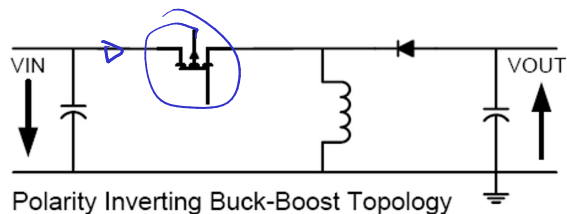


Polarity Inverting Buck-Boost Topology

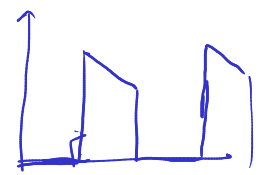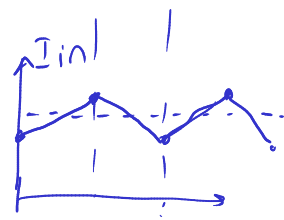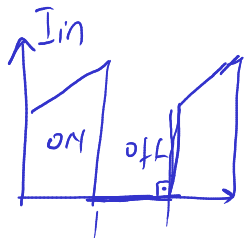

Cuk converter

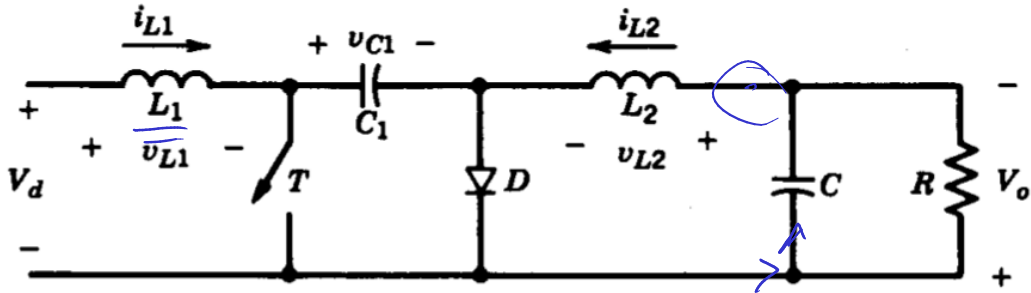

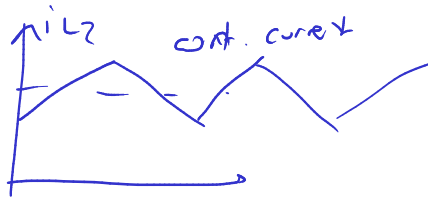Double ended: Inductors placed at both the input and the output



Cuk converter

Advantages:

- Both input and output currents are ripple free (fed through inductors)

Ćuk converter

Advantages:

- Both input and output currents are ripple free (fed through inductors)
- Lower filtering requirements

Ćuk converter

Advantages:

- . Both input and output currents are ripple free (fed through inductors)
- . Lower filtering requirements
- . Constant source current

Ćuk converter

Disadvantages:

Ćuk converter

Disadvantages:

- Capacitor(C_1) is quite bulky

Cuk converter

Disadvantages:

- Capacitor (C_1) is quite bulky
- Capacitor (C_1) should have a large ripple current rating


Ćuk converter

Disadvantages:

- Capacitor (C_1) is quite bulky
- Capacitor (C_1) should have a large ripple current rating
- Complex circuit


For curious students: [Power Electronics Manifesto](#) by Slobodan Ćuk

Practical Product: LM2611

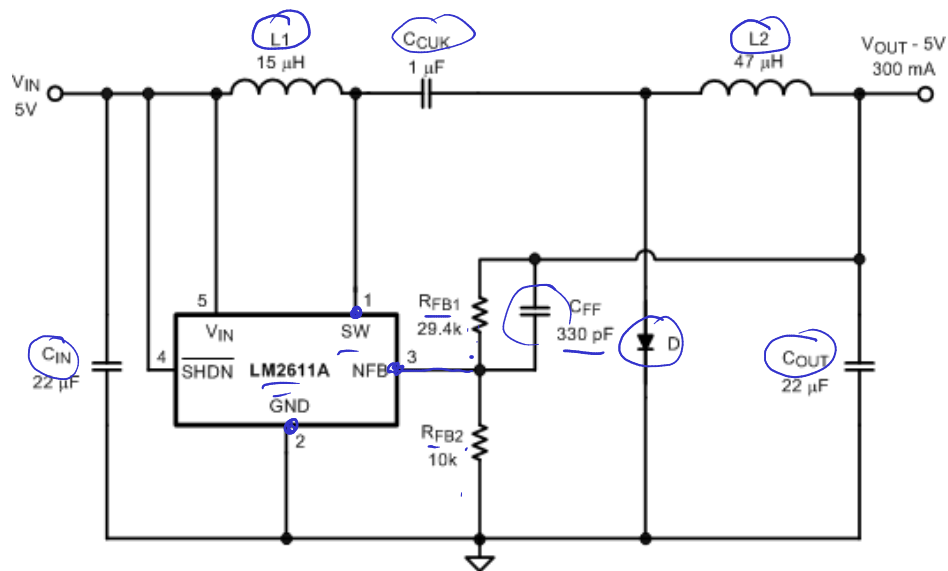

C_{IN} : TAIYO YUDEN X5R JMK325BJ226MM
 C_{cUK} : TAIYO YUDEN X5R EMK316BJ105MF
 C_{OUT} : TAIYO YUDEN X5R JMK325BJ226MM
D: ON SEMICONDUCTOR MBR0520
L1: SUMIDA CR32-150
L2: SUMIDA CR32-470

Practical Product: [LM2611](#)

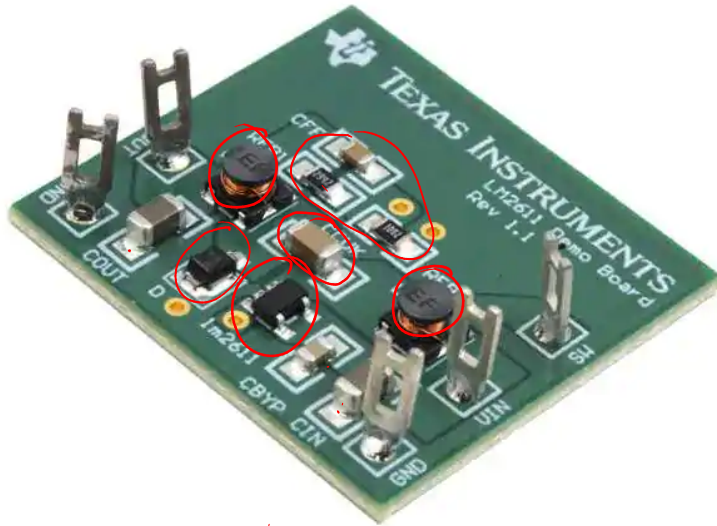

Example

Mohan Exercise 7-3


SEPIC Converter

SEPIC Converter

Single Ended Primary Inductor Converter


SEPIC Converter

Single Ended Primary Inductor Converter

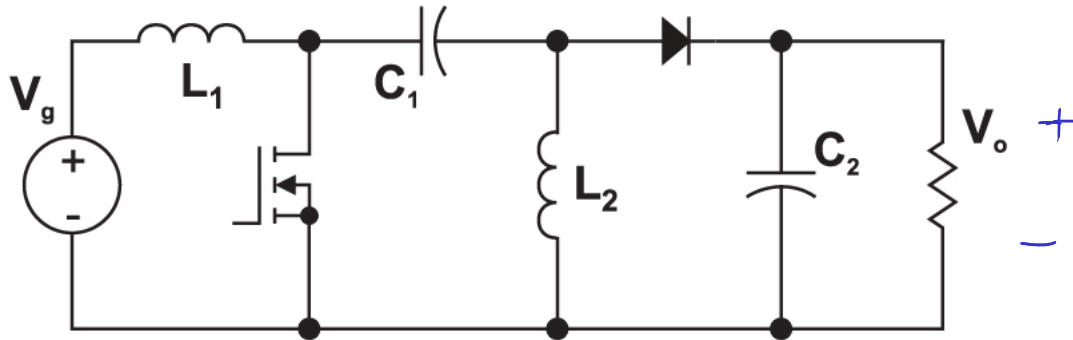


SEPIC Converter

Single Ended Primary Inductor Converter

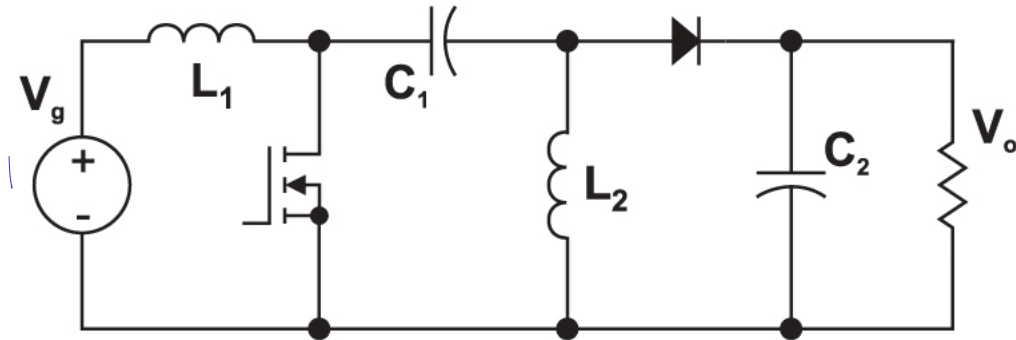


Essentially a boost converter cascaded with a buck-boost converter

SEPIC Converter

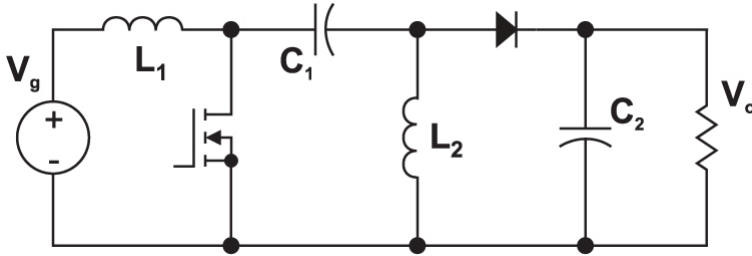

Popular in battery powered systems (voltage level can be adjusted according to charge level)


SEPIC Converter

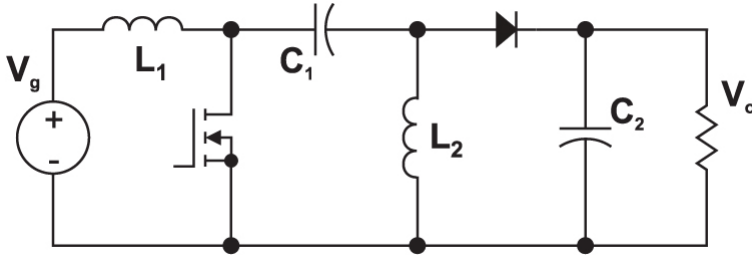

Popular in battery powered systems (voltage level can be adjusted according to charge level)

Possible to shutdown completely (when the switch is off)


Operating Modes:

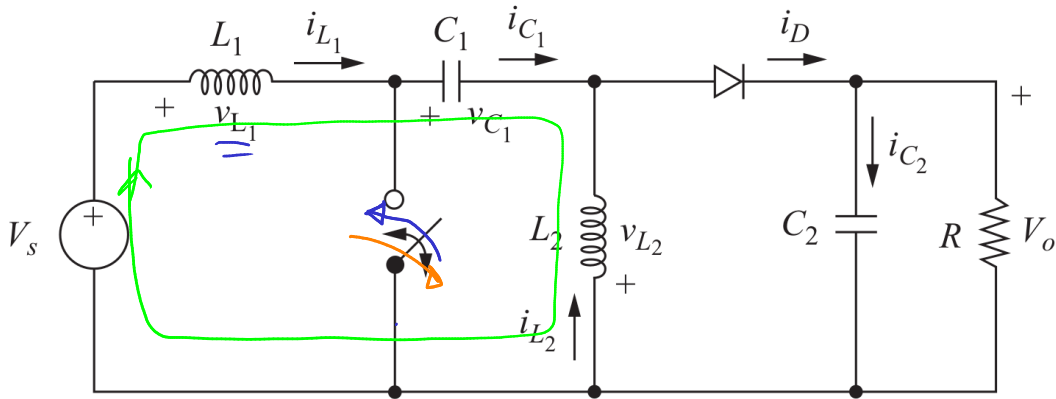

$-V_s + V_{L1} + V_{C1} - V_{L2} = 0$ } for inst. and average voltages
in the steady state $\Rightarrow V_{L1} = 0, V_{L2} = 0$ (average values)
 C_1 is large enough $\Rightarrow V_{C1} \Rightarrow$ is constant

$$V_{C1} = V_s$$


Operating Modes: ON State

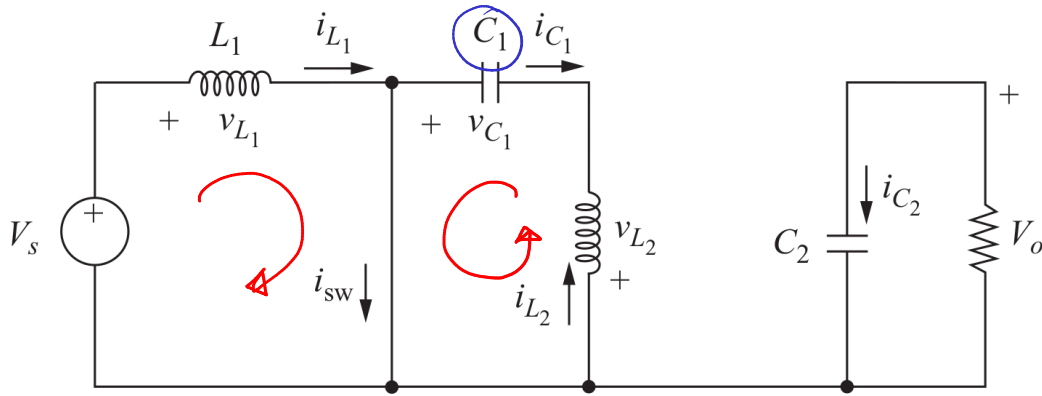

$$v_{L1} = V_s$$

$$v_{L2} = \underline{V_{C1}} = V_s$$


Operating Modes: OFF State

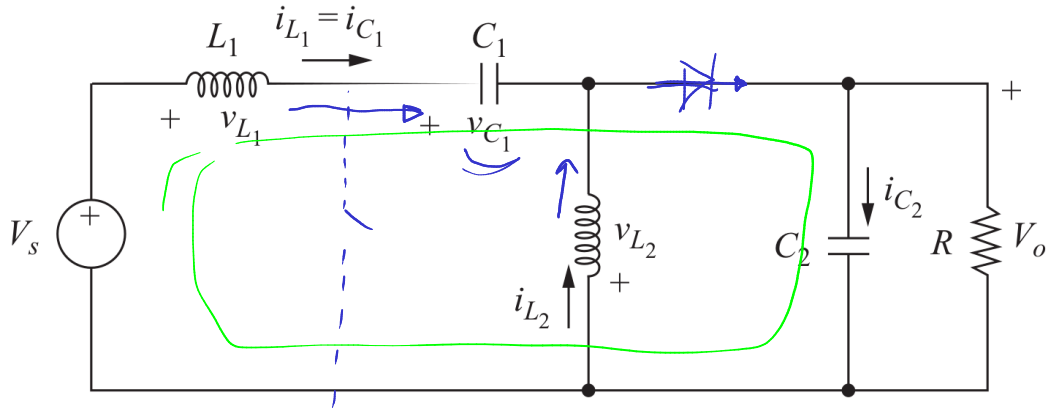

$$-V_s + v_{L_1} + v_{C_1} + V_o = 0$$

$$\underline{\underline{v_{L_1} = -V_o}}$$

Operating Modes: OFF State

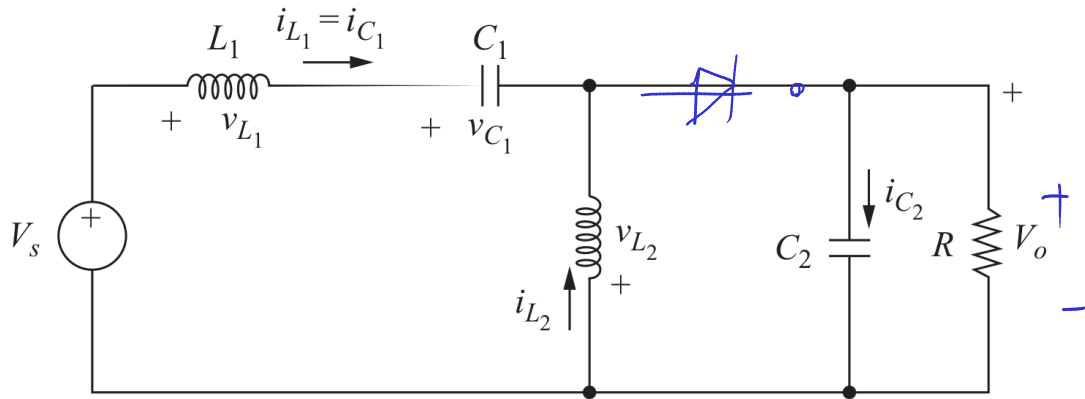

$$-V_s + v_{L1} + v_{C1} + V_o = 0$$

$$\text{If } v_{C1} = V_s \text{ then } v_{L1} = -V_o$$

Use voltage second before


$$V_s \cdot D / T_s +$$
$$-V_o(1-D) / T_s = 0$$

$$V_o = V_s \cdot \left(\frac{D}{1-D} \right)$$

21 / 31


↳ buck-boost converter

Operating Modes: Currents

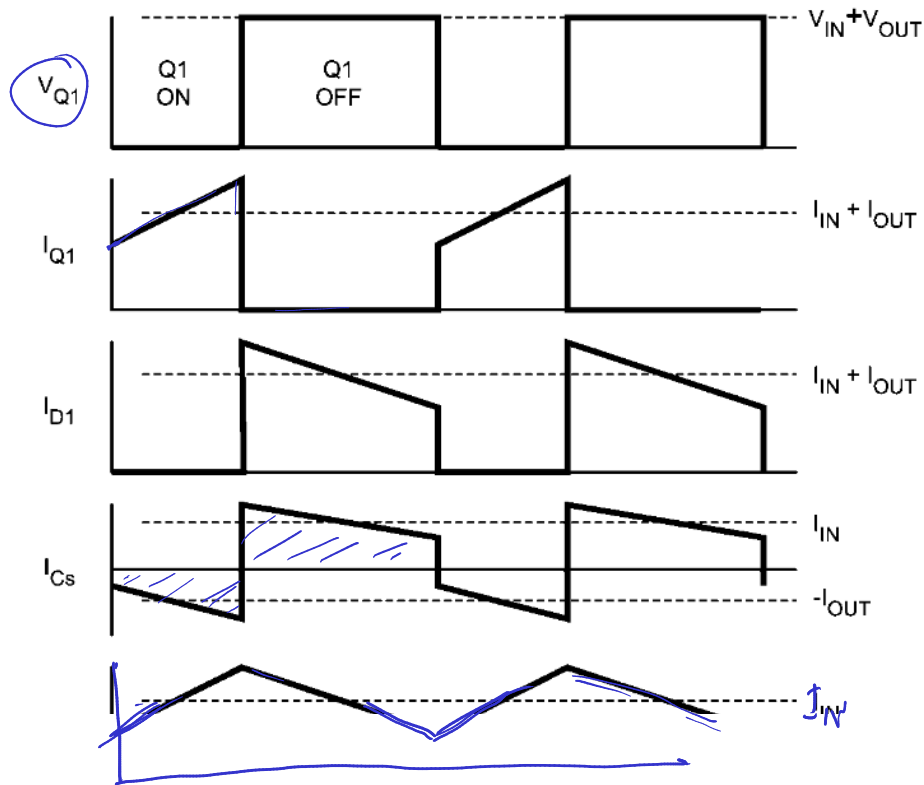

Example (Handout)

SEPIC With Mutually Coupled Inductors

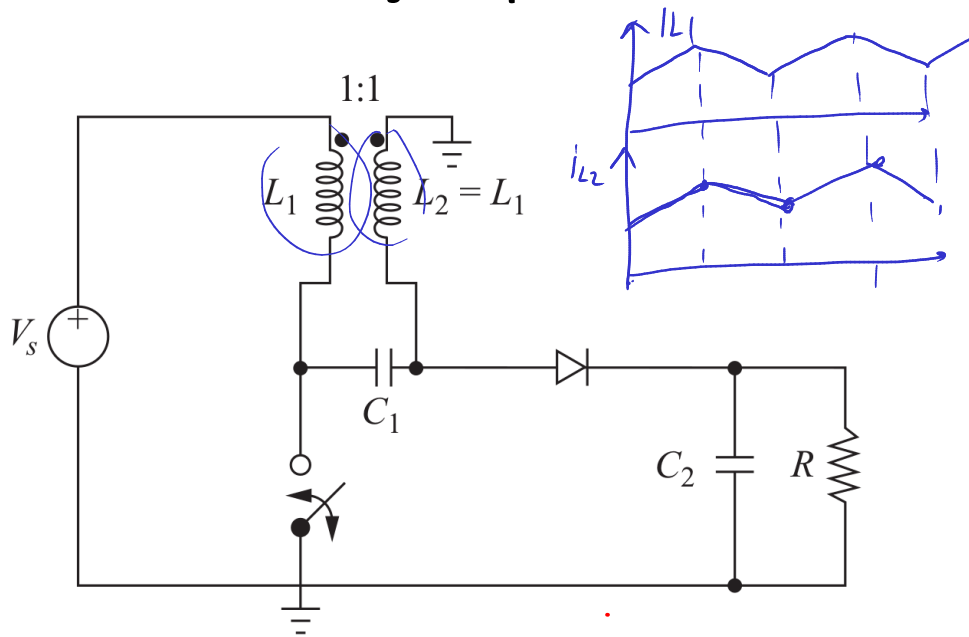

SEPIC Converter

SEPIC Converter

Advantages:

- Non-inverting buck-boost converter

SEPIC Converter

Advantages:

- Non-inverting buck-boost converter
 - Energy Efficient (can be completely turned-off)
-

Disadvantages:

- Pulsating output current

SEPIC Converter

Advantages:

- Non-inverting buck-boost converter
 - Energy Efficient (can be completely turned-off)
-

Disadvantages:

- Pulsating output current
- Large capacitance (and large ripple current rating)

SEPIC Converter

Advantages:

- Non-inverting buck-boost converter
 - Energy Efficient (can be completely turned-off)
-

Disadvantages:

- Pulsating output current
- Large capacitance (and large ripple current rating)
- Fourth order transfer function, difficult to control

SEPIC Converter

SEPIC Converter

Inductors can be combined in a single core (coupled inductors)

Lower required inductance, and size

Minimize oscillation in the circuit (more on that later)


Interleaved Converters

Interleaved Converters

Interleaved Buck Converter


Interleaved Converters

Interleaved Buck Converter

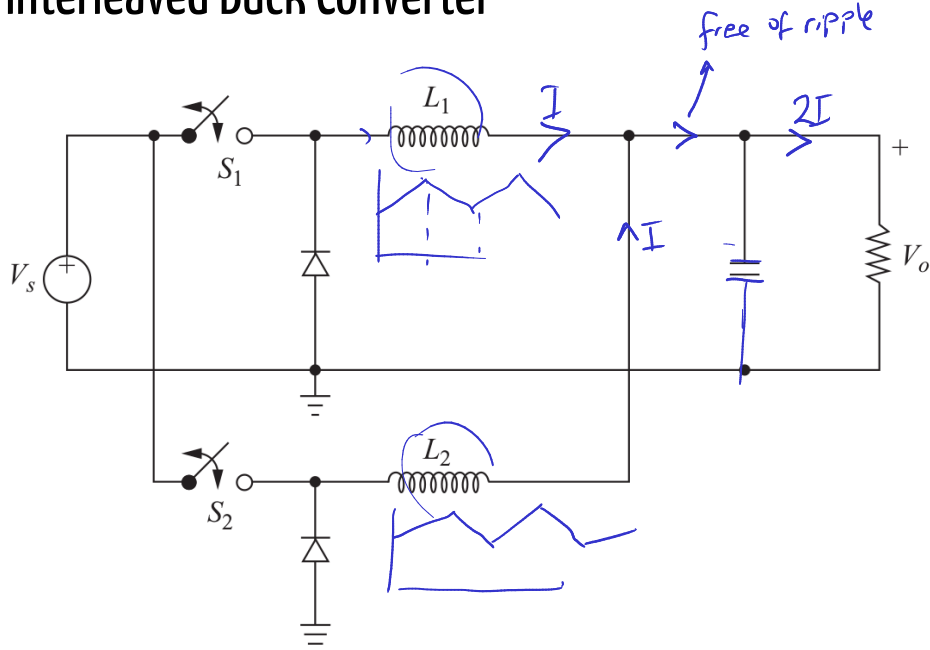


Interleaved Converters

Interleaved Buck Converter

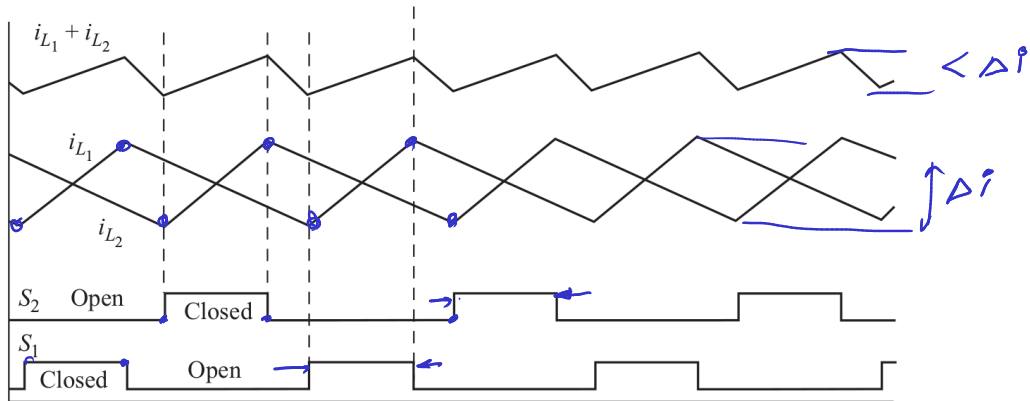

Interleaved Converters

Interleaved Boost Converter

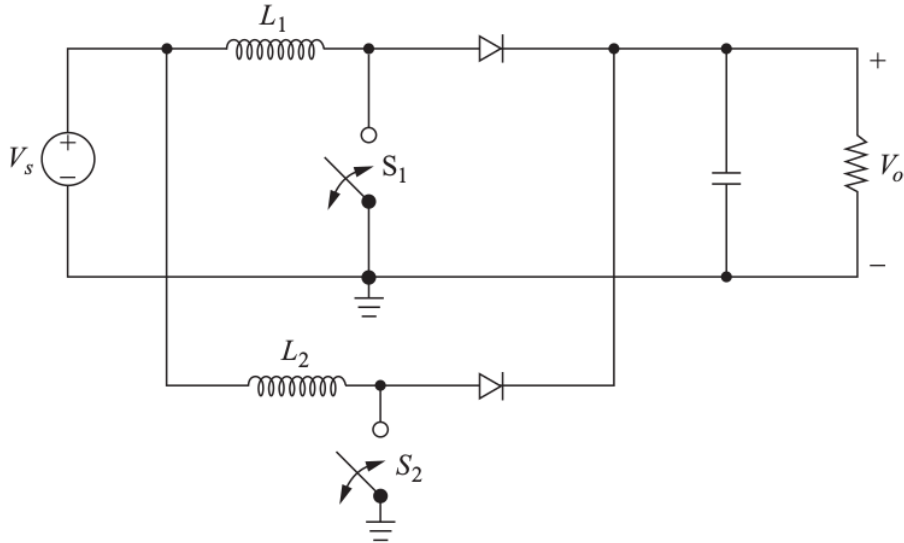

Reading Assignments

- [TI Training Videos](#)
- [MATLAB Topology Comparison](#)
- [Application Note: Designing A SEPIC Converter](#)
- [Sepic and Cuk Converters](#)
- [Sepic Converter Basics](#)
- [Power supply topology: SEPIC vs Flyback](#)

You can download this presentation from:
keysan.me/ee464