

8th HOMEWORK

Due May 8, 2008

- In the following equations, solve for A and ϕ in terms of the other constants using phasor diagrams
 - $A \cos(\omega t - \phi) + 3A \sin(\omega t - \phi) = \sin(\omega t)$
 - $\sqrt{2} \cos(\omega t - \phi) - A \sin(\omega t - \phi) = \cos(\omega t)$
 - $\pi \cos(\omega t - \phi) + \sqrt{3}A \sin(\omega t - \phi) = 2 \sin(\omega t)$
- A sheet of aluminum is being pushed between the poles of a horseshoe magnet. Describe the direction of flow of the induced current, or eddy currents, in the sheet. Explain why there is a strong friction force that opposes the motion of the sheet.
- A circuit consists of a resistor connected in series to a battery; the resistance is 5Ω and the emf of the battery is $12 V$. The wire (of negligible resistance) connecting these circuit elements are laid out along a square of $20 \text{ cm} \times 20 \text{ cm}$. The entire circuit is placed face on in an oscillating magnetic field. The instantaneous value of the magnetic field is

$$B = B_0 \sin \omega t \tag{1}$$

with $B_0 = 0.15 T$ and $\omega = 360 \text{radian/s}$.

- Find the instantaneous current in the resistor.
 - Find the average power dissipated in the resistor
- What is the natural frequency for an LC circuit consisting of a $2.2 \times 10^{-6} F$ capacitor and a $8.0 \times 10^{-2} H$ inductor?
 - Consider an RC circuit consisting of a capacitor and a resistor in series. The capacitor is initially charged
 - Show that Kirchhoff's rule leads to the following equation for this system:

$$R \frac{dQ}{dt} + \frac{1}{C} Q = 0 \tag{2}$$

- (b) Verify that the solution of this equation is

$$Q = Q_0 e^{-t/RC} \quad (3)$$

where Q_0 is the initial charge at time $t = 0$.

- (c) Show that the current is

$$I = -\frac{Q_0}{RC} e^{-t/RC} \quad (4)$$

- (d) Suppose that the resistance is 3.0Ω . Suppose that the capacitance of the capacitor is $1.0 \times 10^{-4} F$ and that the initial voltage across its terminals is $3.0 V$. For this special case, plot the current as a function of time. What is the current at the initial instant? After how many seconds will the current have dropped to one-half of its initial value.

6. An LCR series circuit has $L = 0.5 H$, $C = 2.0 \times 10^{-5} F$, and $R = 10 \Omega$. At time $t = 0$, the capacitor is fully charged with a voltage at $20 V$ across its plates.

- (a) What is the initial energy in the circuit?
- (b) What is the percentage loss of energy per period?
- (c) At what time after $t = 0$ will the energy in the circuit have fallen to one-half of its initial value? One-tenth of its initial value?
- (d) Plot the energy as a function time for the time interval $0 s \leq t \leq 0.1 s$